



Electrolytic capacitor

'blue top' resistors

PASCO USB hub (voltmeter in this case) Discharge circuit switch



Electrolytic capacitor Take care to connect **positive** to the **positive** voltage terminal!





About 6V DC power supply for charging circuit

	1.710 101	Ω and a
	2.2 kn	22 kil 47 k0
	1 kn	- 100 kn
	330 D	- 330 kn /
	100 0 3.3 M	NN IMA
- 1		1
		and the second

Multiple resistors, with a selector dial. (Measure accurately with a multimeter).

INSTRUCTIONS

1. Set up the equipment. **TAKE CARE THAT THE CAPACITOR IS WIRED THE CORRECT WAY ROUND**. A reverse bias (i.e. where the negative (black) capacitor terminal is connected to the +ve power supply terminal) on an electrolytic capacitor may cause them to be damaged irreparably. **Check with your teacher before switching on!**

Don't use the ammeter. The PASCO datalogger ammeters don't work so well at μ A levels, and may introduce noise (and possibly oscillations) in the circuit.

 Experiment using the datalogger and Capstone software and charge then discharge. Determine the optimal resistor value to charge and discharge in about ten seconds.
Set the datalogger voltmeter data rate to be 20Hz.



4. Plot: (i) charging V vs t; (ii) discharging V vs t and (iii) ln V vs t. Use the latter to determine the **RC time** for the circuit.

5. Use a multimeter to determine R, and hence calculate the capacitance (in μ F).



Charging a capacitor using a DC source

1. Switch closed. Current flows through resistor and positive charge builds up on right capacitor plate. An equal amount of negative charge builds up on left plate.

2. *Electrical field* set up between capacitor plates as no current can flow between them. Voltage V between the plates is V = Q/C where Q is the total charge

the plates is V = Q/C where Q is the total charge deposited and C is the *capacitance* ('charge per unit volt')

3. As charge builds up on right plate, potential difference between capacitor and source reduces. This reduces the current flowing onto the plate. Eventually the voltage V becomes V_0 and hence no more current can flow.

4. Note the amount of charge which can be deposited depends on the resulting *electrical field strength* between the plates. Above the breakdown field strength, current will flow between the plates.



Dielectric	Breakdown field strength /Vm ⁻¹
Air	3 x 10 ⁶
Mineral oil	15 x 10 ⁶
Neoprene	16 x 10 ⁶
Water	65 x 10 ⁶
Mica	118 x 10 ⁶



Discharging a capacitor

$$Q = CV$$
 $V = IR$

capacitor charge, voltage relationship

Ohm's law

 $\therefore I = \frac{V}{R} = -C\frac{dV}{dt}$

Note $V = V_0$ when t = 0



$$I = -\frac{dQ}{dt}$$

Definition of current, and negative since charge is discharged from plates

$$\frac{1}{RC} \int_0^t dt = -\int_{V_0}^V \frac{dV}{V}$$
$$\frac{t}{RC} = -\left[\ln|V|\right]_{V_0}^V$$
$$\frac{t}{RC} = -\ln\left(\frac{V}{V_0}\right)$$
$$V = V_0 e^{-\frac{t}{RC}}$$



Time, current and voltage data copied and pasted into Excel from Capstone.



Use a multimeter to determine a precise measurement of the resistor chosen. Write this into your spreadsheet!



Make sure your **disconnect** the resistor from the circuit first.

Resistance measurement from multimeter reading

1068

R /ohms

Plot charging and discharging voltage vs time curves using Excel





CAPACITOR CHARGE AND DISCHARGE

A. French. 20/9/2021

CHARGING

DISCHARGING





RC /s

C /microF

1.048

981

InV vs discharge time t

Extract just the discharge curve. Shift the time measurements so they start from zero.

For **discharge**:

$$V = V_0 e^{-\frac{t}{RC}}$$
$$\therefore \ln V = \ln V_0 - \frac{t}{RC}$$

So a graph of $\ln V$ vs tshould be a straight line graph, with gradient -1/RC

