



Capacitor charge &
discharge in 10ohm
increments

Dr Andrew French


Laptop running
PASCO
Capstone

8V DC
supply

Large analogue
voltmeter

PASCO
USB hub
(voltmeter,
ammeter

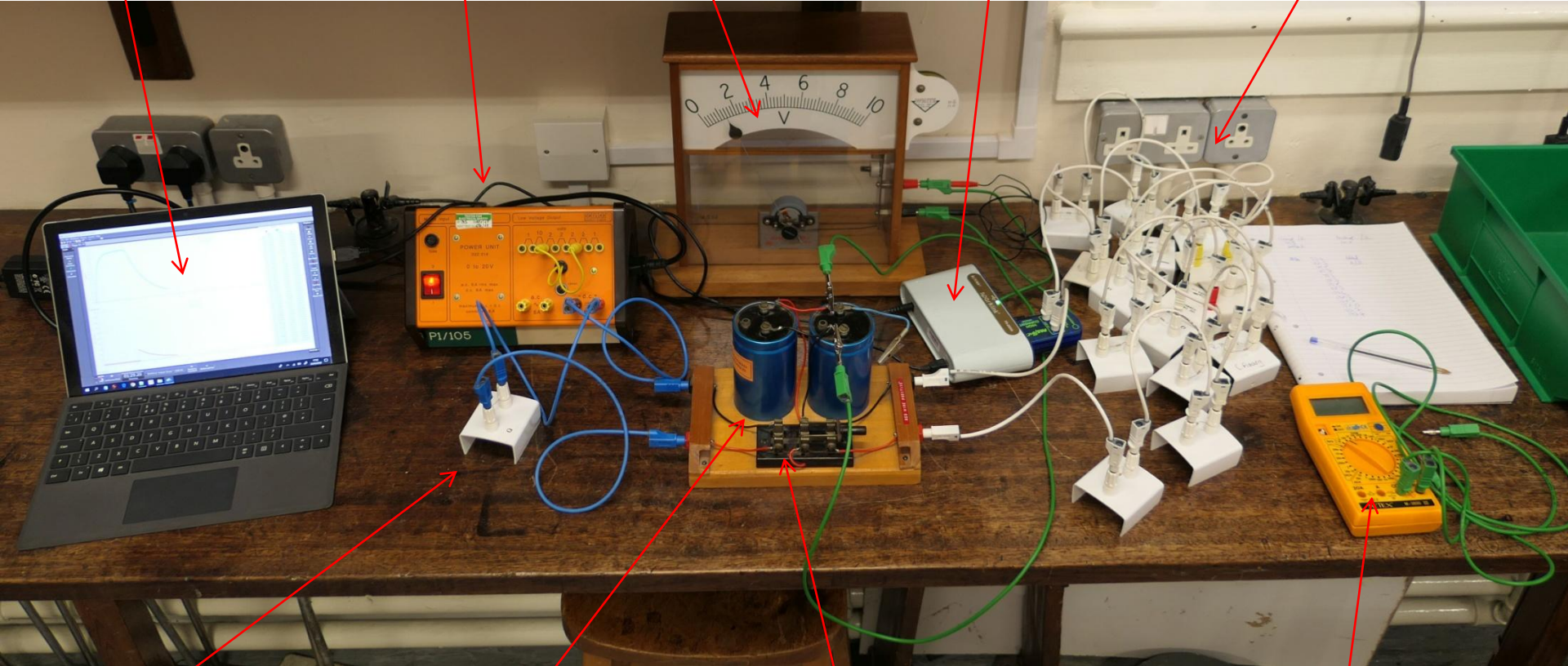10ohm resistors
mounted in
terminal blocks,
wired in series




40.8ohm charging
resistor in a
terminal block

Capacitors wired in
parallel to yield a
total capacitance
of about 0.1F


Charge
/discharge
switch

Multimeter for testing total
resistance of resistors
(unplug resistors from circuit
before testing)

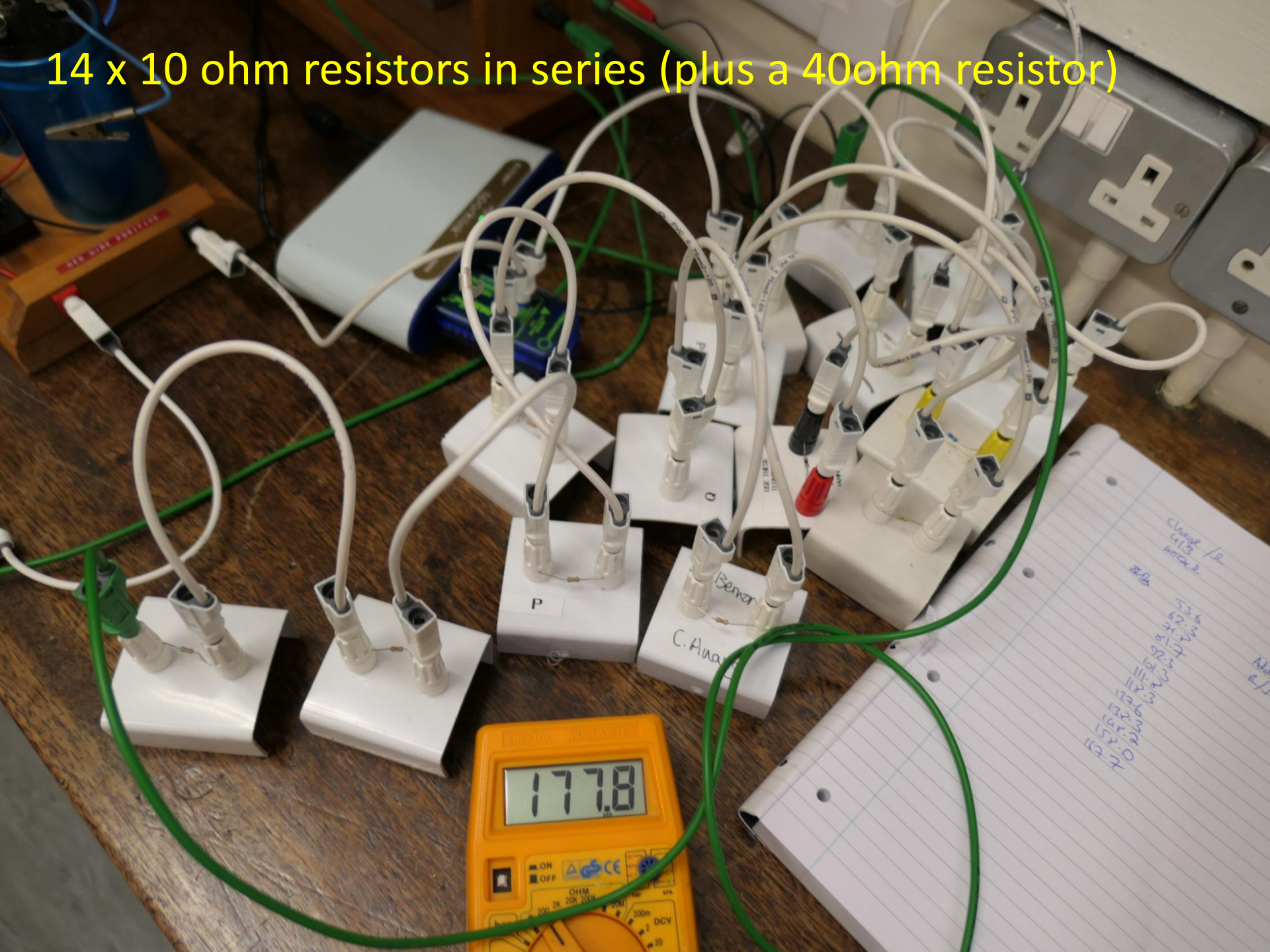14 x 10 ohm resistors in series (plus a 40ohm resistor)



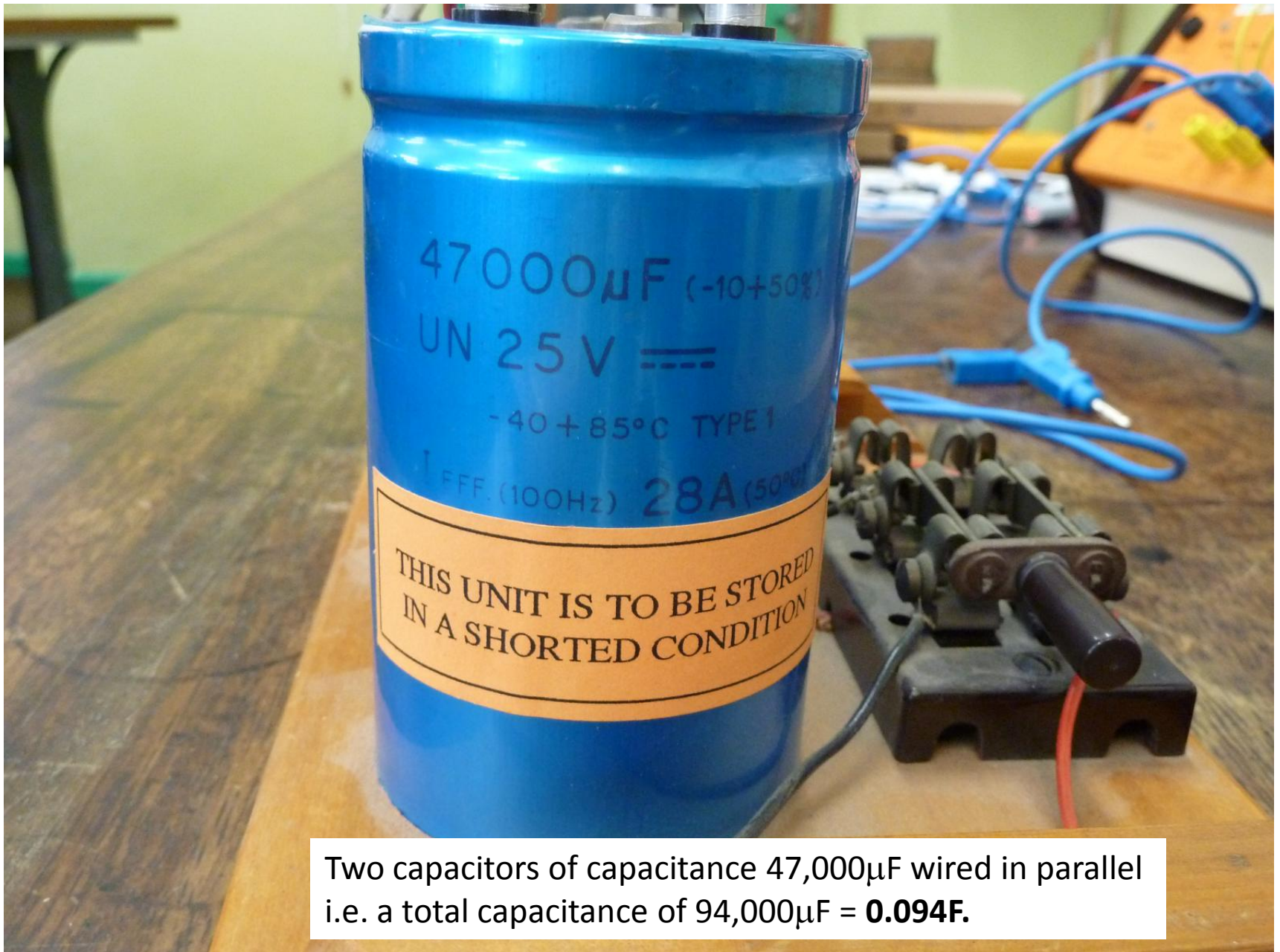
Change
413
total
222
53.6
62.3
71.2
81.7
92.3
102.9
113.5
124.1
134.7
145.3
155.9
166.5
177.1



Two capacitors of capacitance $47,000\mu\text{F}$ wired in parallel i.e. a total capacitance of $94,000\mu\text{F} = \mathbf{0.094\text{F}}$.

Charging a capacitor using a DC source

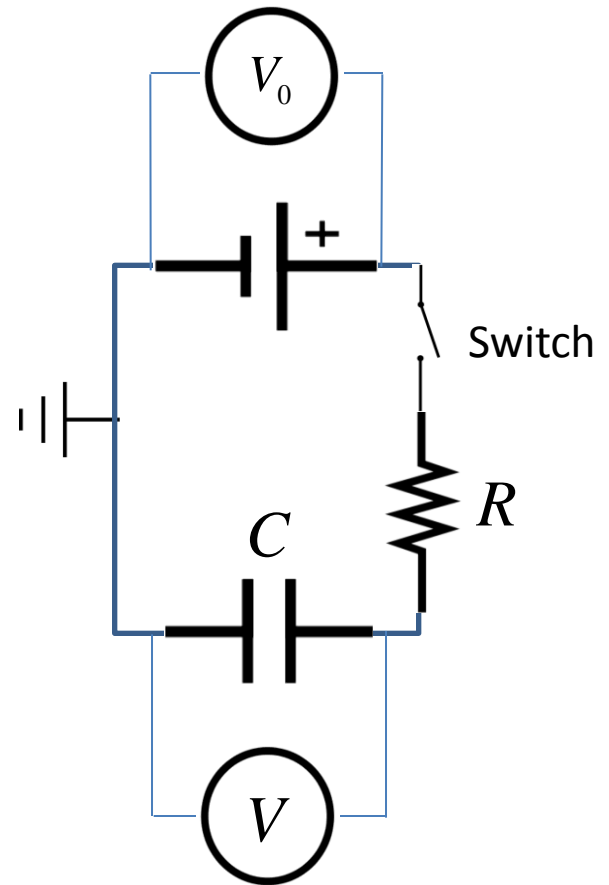1. Switch closed. Current flows through resistor and positive charge builds up on right capacitor plate. An equal amount of negative charge builds up on left plate.
2. *Electrical field* set up between capacitor plates as no current can flow. Voltage V between the plates is $V = Q/C$ where Q is the total charge deposited and C is the *capacitance* ('charge per unit volt')
3. As charge builds up on right plate, potential difference between capacitor and source reduces. This reduces the current flowing onto the plate. Eventually the voltage V becomes V_0 and hence no more current can flow.
4. Note the amount of charge which can be deposited depends on the resulting *electrical field strength* between the plates. Above the breakdown field strength, current will flow between the plates.



Dielectric	Breakdown field strength / Vm^{-1}
Air	3×10^6
Mineral oil	15×10^6
Neoprene	16×10^6
Water	65×10^6
Mica	118×10^6

Charging a capacitor using a DC source

$$Q = CV$$

capacitor charge, voltage relationship

$$V_{\infty} - V = IR$$

Ohm's law

$$I = \frac{dQ}{dt}$$

Definition of current



$$\therefore I = \frac{V_{\infty} - V}{R} = C \frac{dV}{dt}$$

$$\frac{1}{RC} \int_0^t dt = \int_0^V \frac{dV}{V_{\infty} - V} = - \int_0^V \frac{-dV}{V_{\infty} - V}$$

$$\frac{t}{RC} = - \left[\ln |V_{\infty} - V| \right]_0^V$$

$$-\frac{t}{RC} = \ln(V_{\infty} - V) - \ln(V_{\infty}) = \ln \left(\frac{V_{\infty} - V}{V_{\infty}} \right)$$
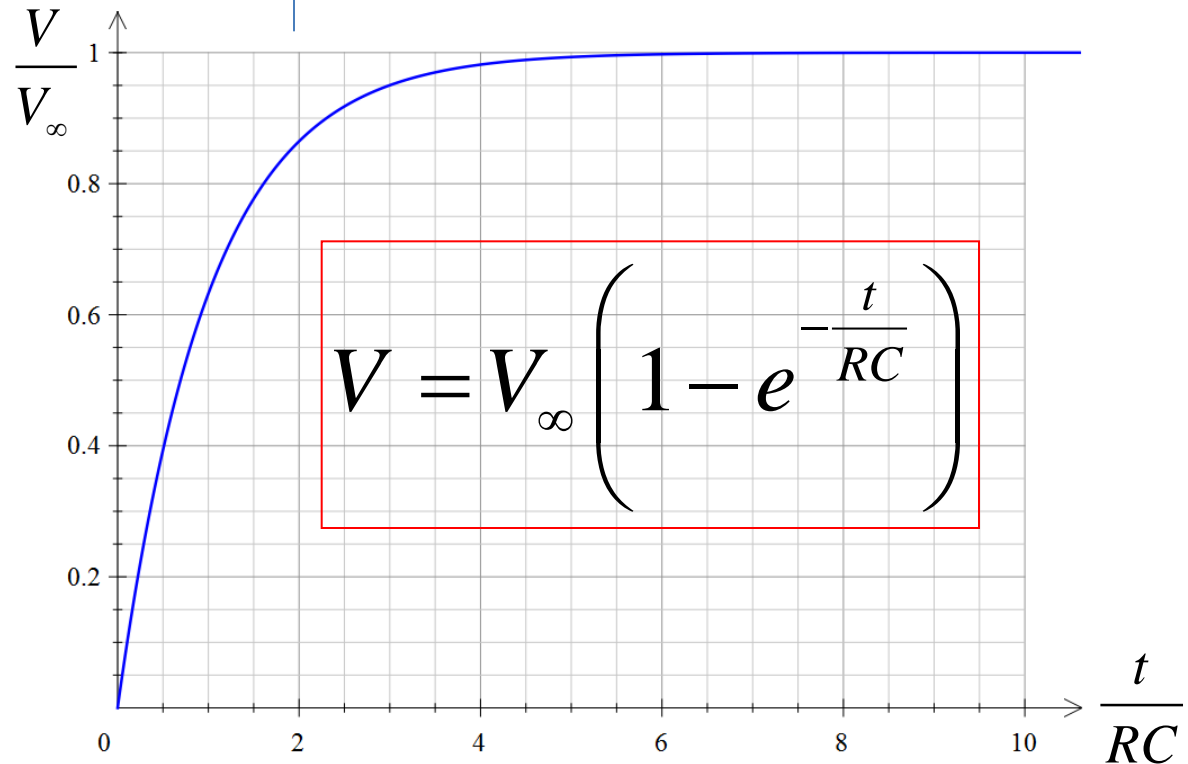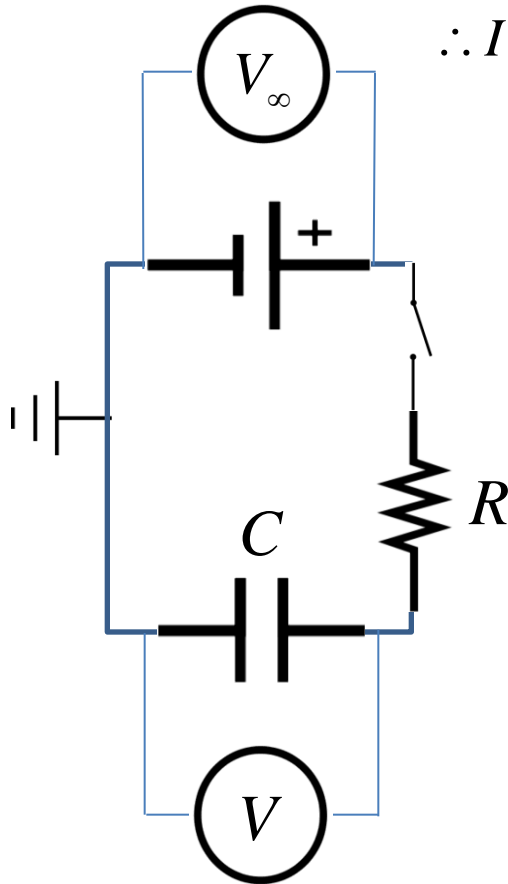
$$\frac{V_{\infty} - V}{V_{\infty}} = e^{-\frac{t}{RC}}$$



Discharging a capacitor

$$Q = CV$$

capacitor
charge, voltage
relationship

$$V = IR$$

Ohm's law

$$\therefore I = \frac{V}{R} = -C \frac{dV}{dt}$$

$$I = -\frac{dQ}{dt}$$

Definition of
current, and
negative since
charge is
discharged from
plates



$$\frac{1}{RC} \int_0^t dt = -\int_{V_0}^V \frac{dV}{V}$$


$$\frac{t}{RC} = -\left[\ln|V|\right]_{V_0}^V$$

$$\frac{t}{RC} = -\ln\left(\frac{V}{V_0}\right)$$

$$V = V_0 e^{-\frac{t}{RC}}$$


Note $V = V_0$ when $t = 0$

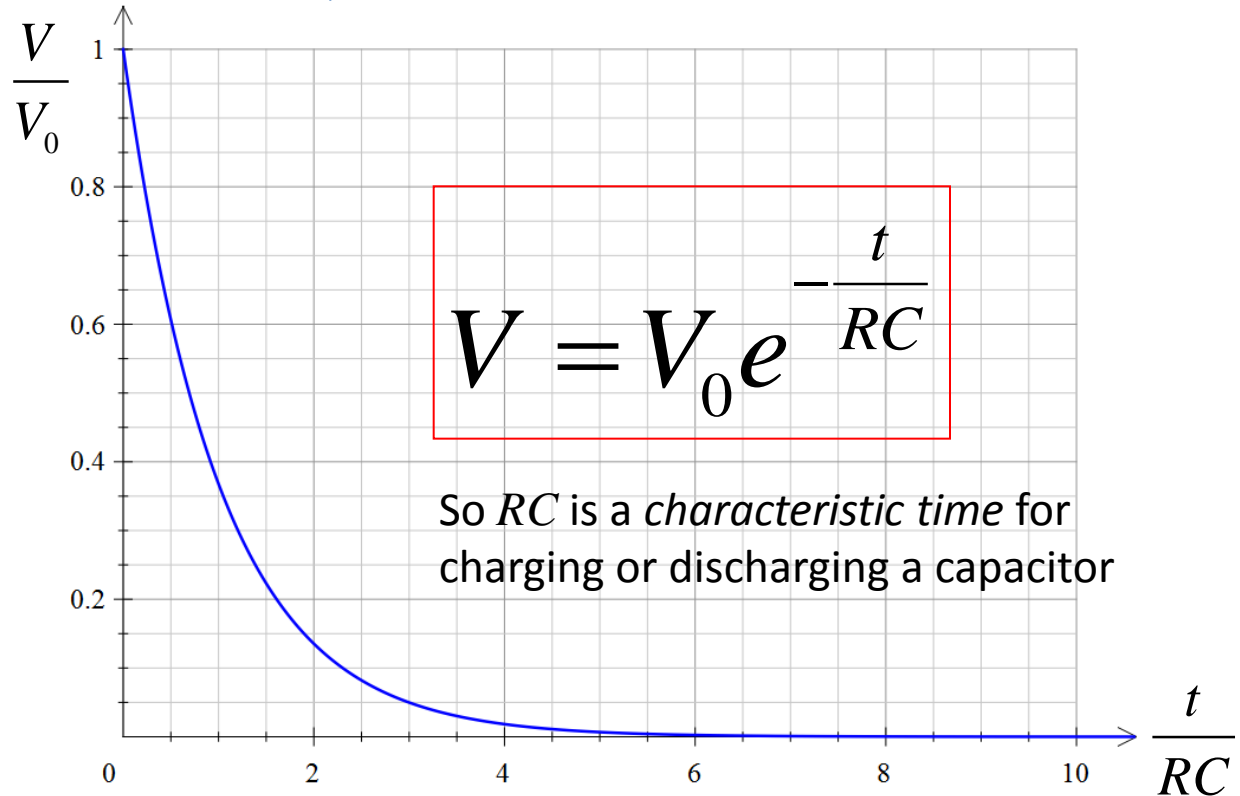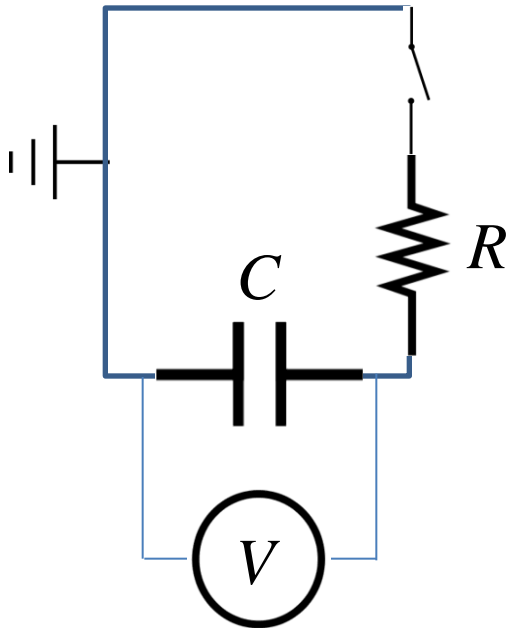

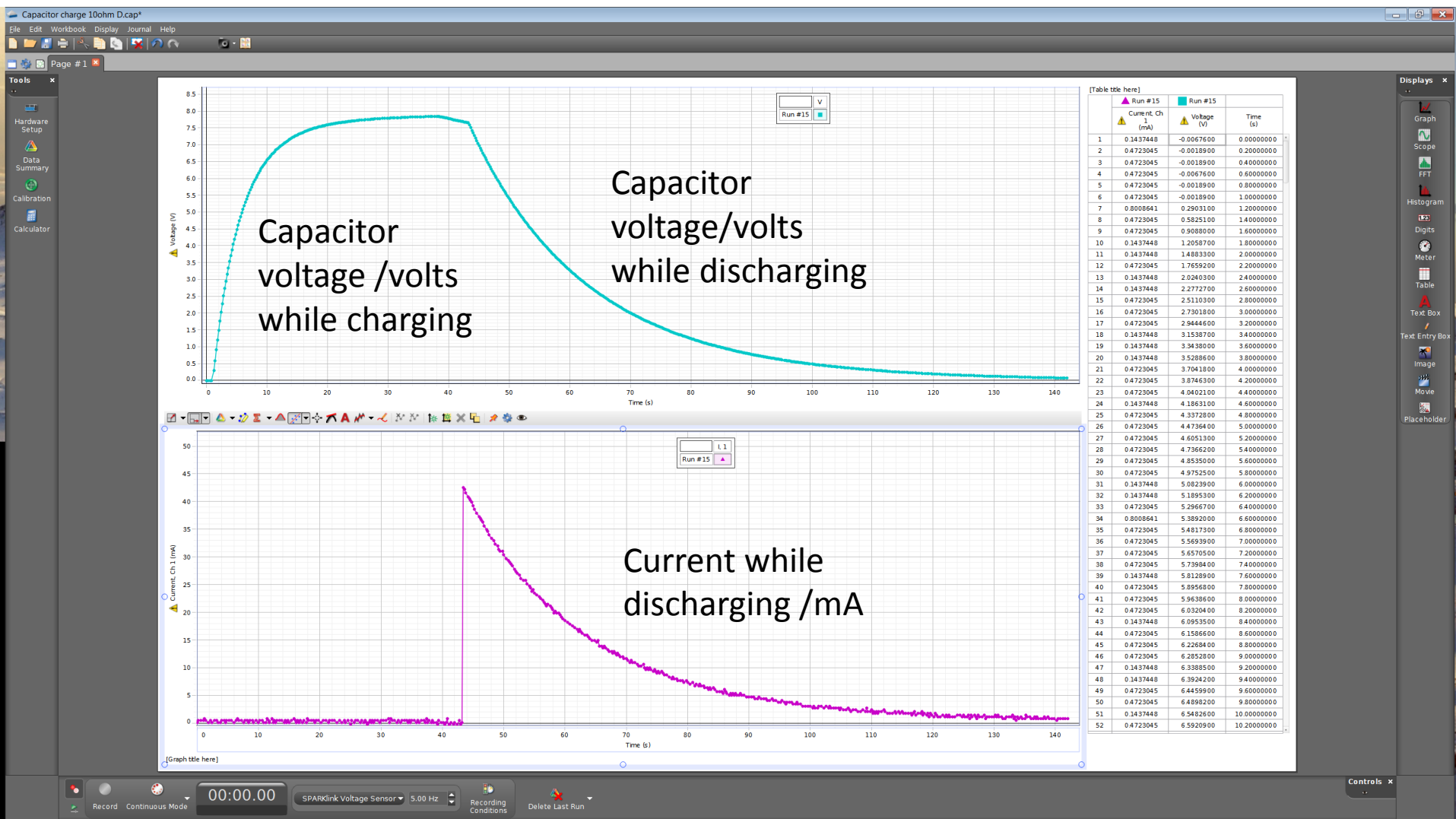

Charge and discharge recorded using Capstone software, interfacing via USB to the PASCO datalogger hub. Note Ammeter is in series with discharge loop, so no current recorded during charging.

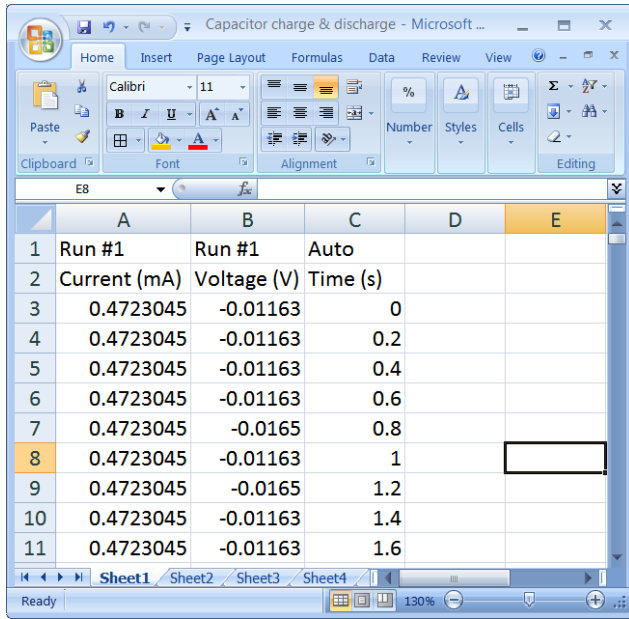Capstone → Copy and paste data to text files (one per discharge resistance)



	A	B	C	D	E
1	Run #1	Run #1	Auto		
2	Current (mA)	Voltage (V)	Time (s)		
3	0.4723045	-0.01163	0		
4	0.4723045	-0.01163	0.2		
5	0.4723045	-0.01163	0.4		
6	0.4723045	-0.01163	0.6		
7	0.4723045	-0.0165	0.8		
8	0.4723045	-0.01163	1		
9	0.4723045	-0.0165	1.2		
10	0.4723045	-0.01163	1.4		
11	0.4723045	-0.01163	1.6		

```

%Import Capacitor charge & discharge data
% LAST UPDATED by Andy French Mar 2020

function import_data
disp(' '); disp(' Importing data from Excel... ')


%Import resistances /ohms
[num,txt,row] = xlsread('Capacitor charge & discharge.xlsx',...
'Resistances');
R = num(:,2).';

%Import data from Excel
num_runs = 15;
for n=1:15
    [num,txt,row] = xlsread('Capacitor charge & discharge.xlsx',...
['Sheet',num2str(n)]);
    data(n).I_mA = num(:,1);
    data(n).V_volts = num(:,2);
    data(n).t_s = num(:,3);
    data(n).R_ohms = R(n);
end

%Save data to a .mat file
save('capacitor data','data','R');
disp(' Data saved to file capacitor_data.mat. ');

%End of code
    
```

MATLAB

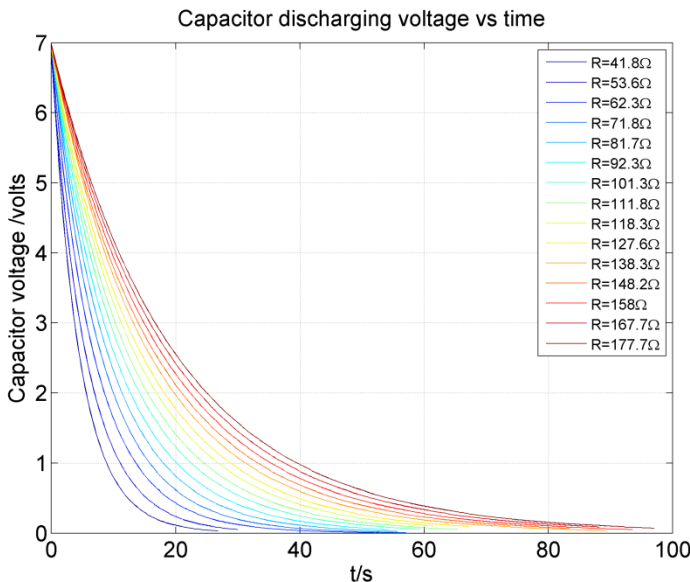

```

%Process Capacitor charge & discharge data
% LAST UPDATED by Andy French Mar 2020
function process_data


%FontSize for graphs
fsize = 16;

%Load imported data
load('capacitor data')


%Initialize charge, discharge and line of best fit curves
fig_Vcharge = figure; ax_V_charge = axes('nextplot','add'); grid on; set(gca,'f
xlabel('t/s','fontsize',fsize); ylabel('Capacitor voltage /volts','fontsize',fs
title('Capacitor charging voltage vs time','fontsize',fsize)
fig_Vdischarge = figure; ax_V_discharge = axes('nextplot','add'); grid on; set(
xlabel('t/s','fontsize',fsize); ylabel('Capacitor voltage /volts','fontsize',fs
title('Capacitor discharging voltage vs time','fontsize',fsize)
fig_Idischarge = figure; ax_I_discharge = axes('nextplot','add'); grid on; set(
xlabel('t/s','fontsize',fsize); ylabel('Current /mA','fontsize',fsize);
title('Capacitor discharging current vs time','fontsize',fsize)
fig_best_fit = figure; ax_best_fit = axes('nextplot','add'); grid on; set(gca,
xlabel('t/s','fontsize',fsize); ylabel('ln(V/volts)','fontsize',fsize);
title('ln(V) vs t line of best fit to find RC time','fontsize',fsize)
fig_V_over_I = figure; ax_V_over_I = axes('nextplot','add'); grid on; set(gca,
xlabel('t/s','fontsize',fsize); ylabel('R = V/I /\Omega','fontsize',fsize);
title('R = V/I for capacitor discharge','fontsize',fsize)

%Determine legend string
lgnd_str = {};
    
```


Capacitor charging voltage vs time

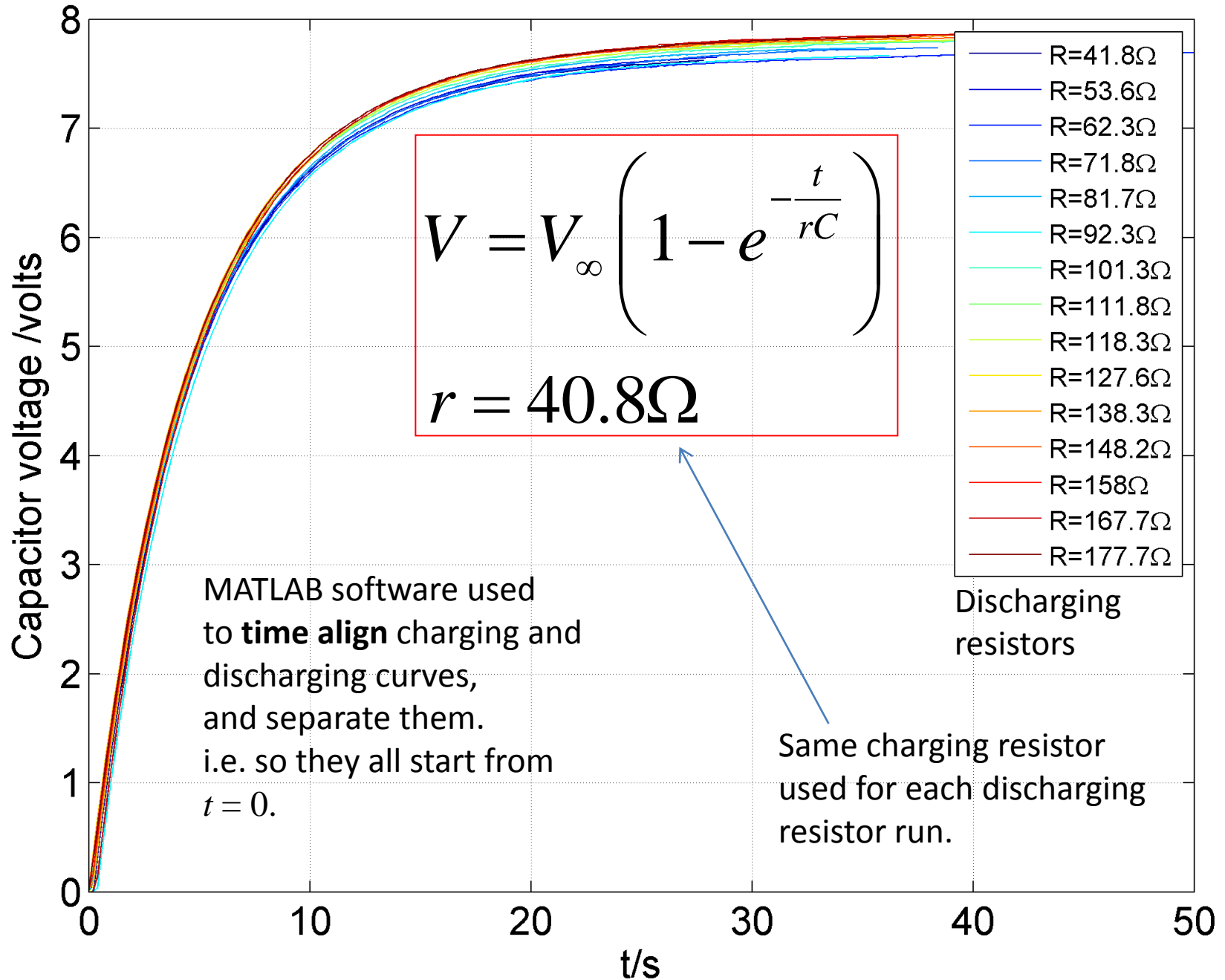


Capacitor discharging current vs time

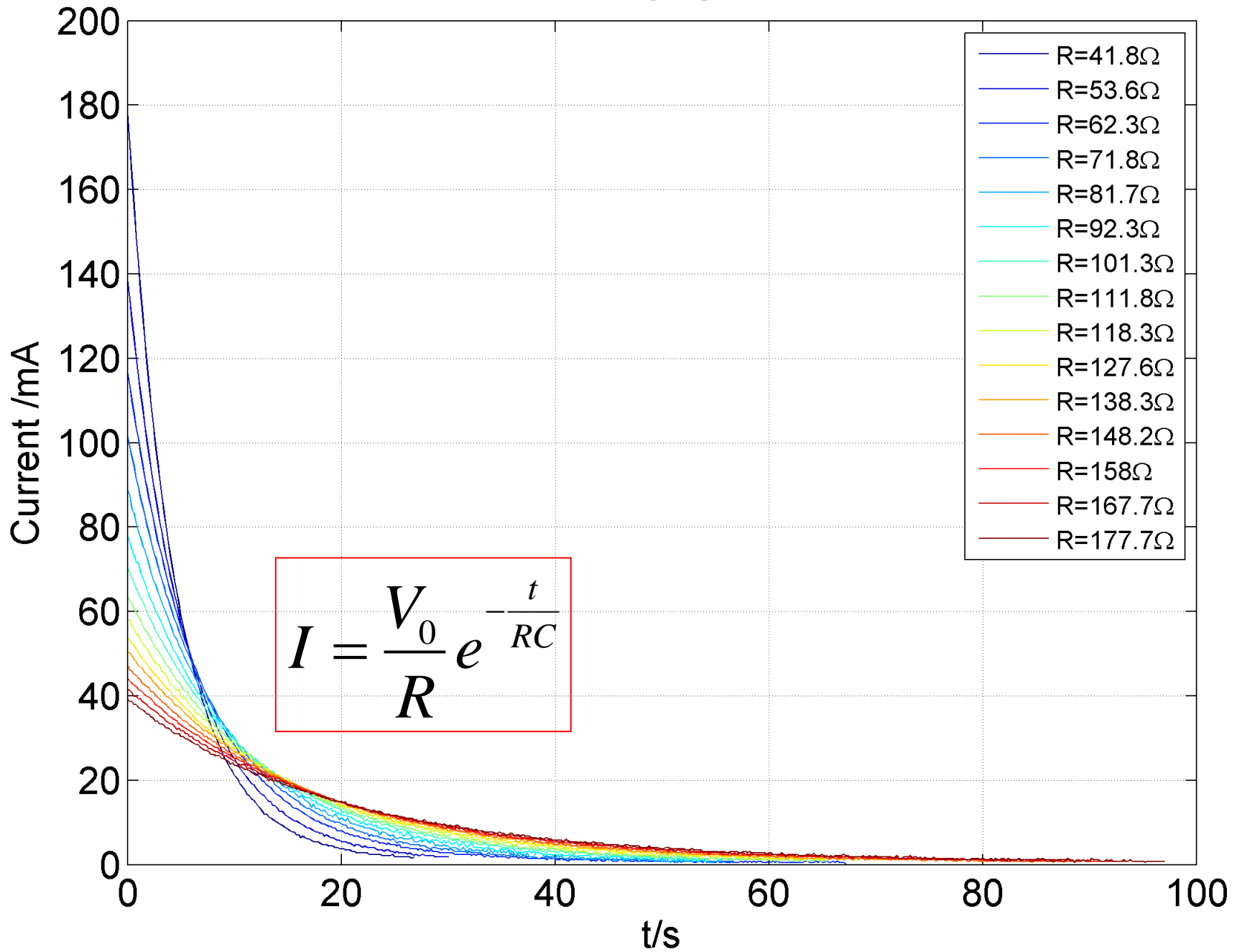


Capacitor discharging voltage vs time

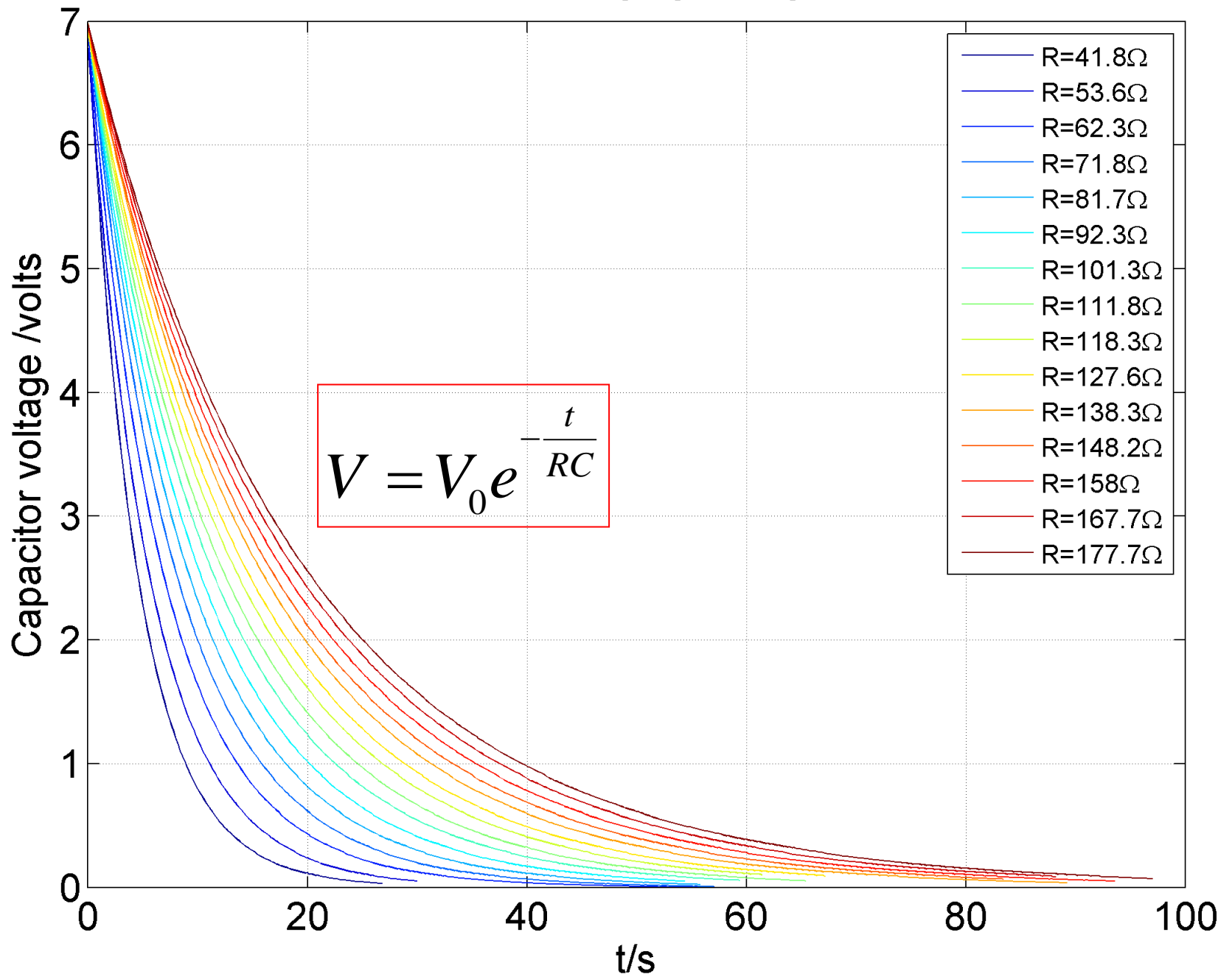

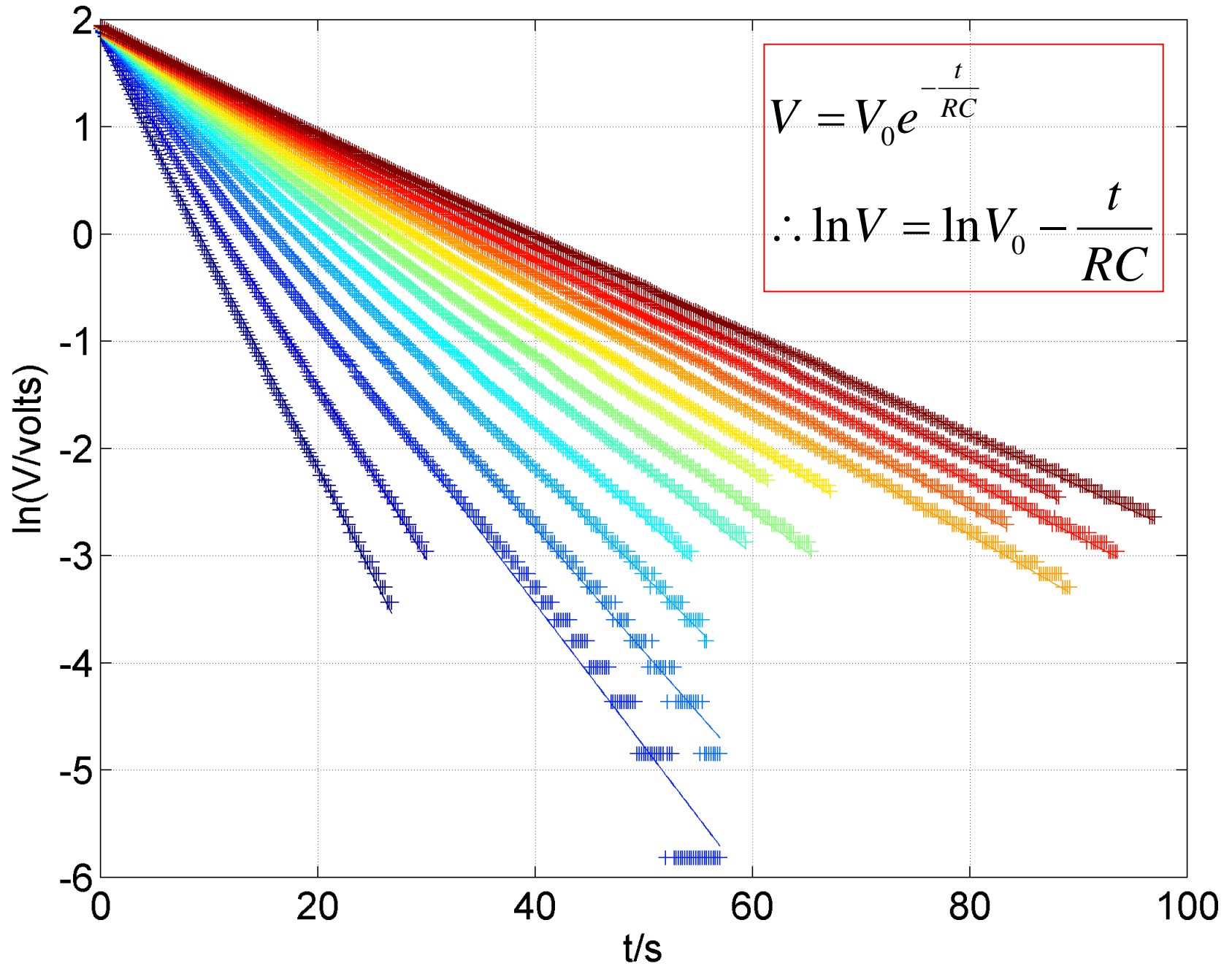ln(V) vs t line of best fit to find RC time


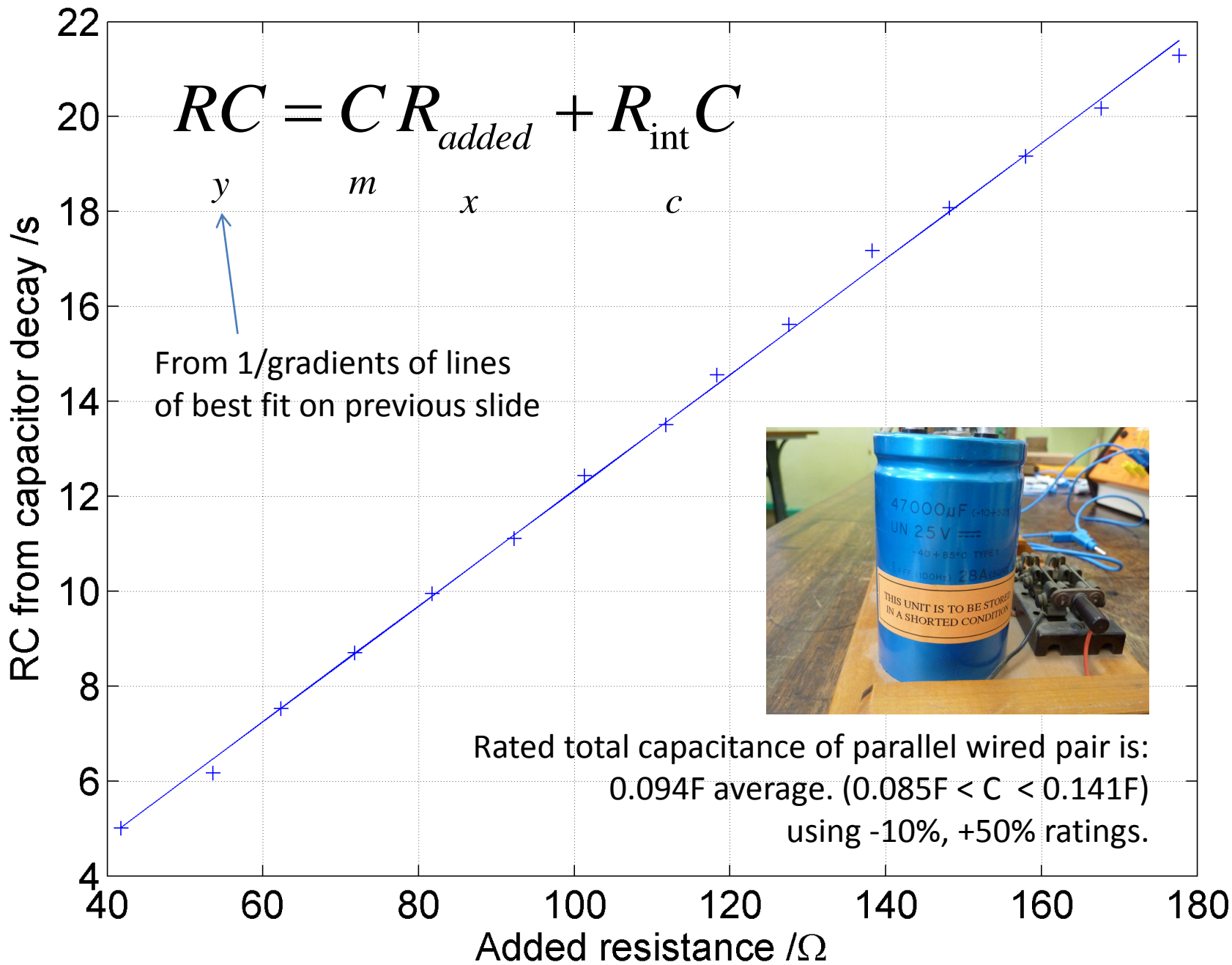
$$C = (0.1219 \pm 0.0012)F, R_{\text{int}} = (-0.575 \pm 1.14)\Omega.$$



Notice overall resistance of circuit appears *not* to be quite constant during full discharge.

$R = V/I$ for capacitor discharge

