

# Electric Circuits Basics



Dr Andrew French. December 2022

# Alternative *digital* voltmeters



Voltmeter

shunt

2V setting

**Most of the kit!**



Mains cable

Power supply

Fixed resistors

Filament lightbulbs


Diodes

Switch


LED

Light Emitting Diode

Ammeter

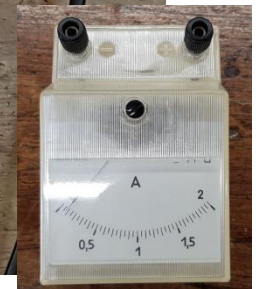

Alternative *analogue* ammeter

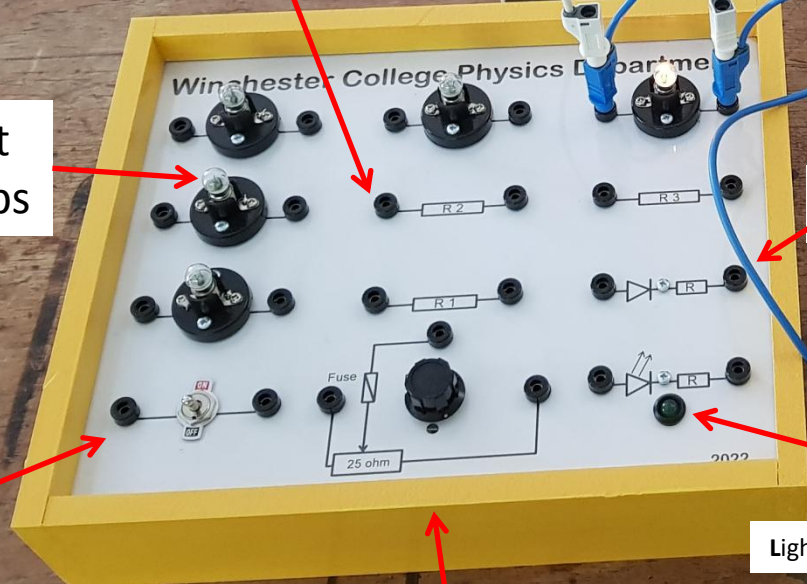

**Circuit board of electrical components**


Yours might be grey or green in colour

**\* ALWAYS SET UP A MULTIMETER BEFORE YOU WIRE IT INTO A CIRCUIT. AN AMMETER USED AS A VOLTMETER WILL CAUSE IT TO BLOW A FUSE \***



**Circuit #1 : One filament bulb in series** (this means a single circuit loop)

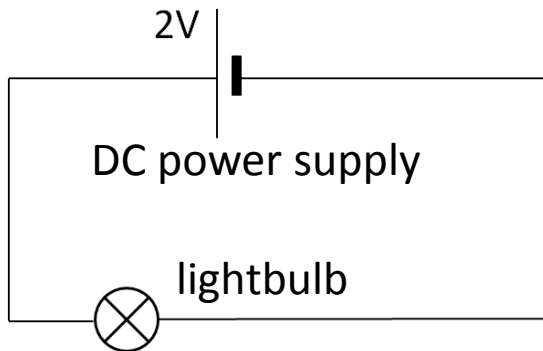1. Set the power supply to a 2V setting.
2. Connect up the 2V power supply to one of the light bulbs.




The drawing above is the equivalent **circuit diagram**.

**DC means Direct Current**  
i.e. a fixed voltage is applied to the circuit, which means a constant current flows



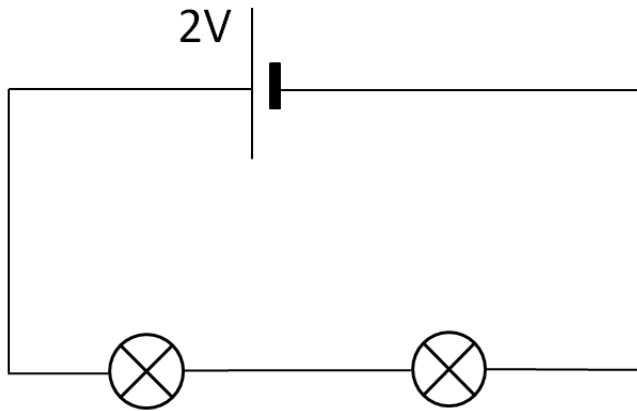
## Circuit #2 : Two filament bulbs in series

When a second bulb is added in series, what happens to the brightness of the bulbs?




The approximately 2V is now shared evenly between each bulb.

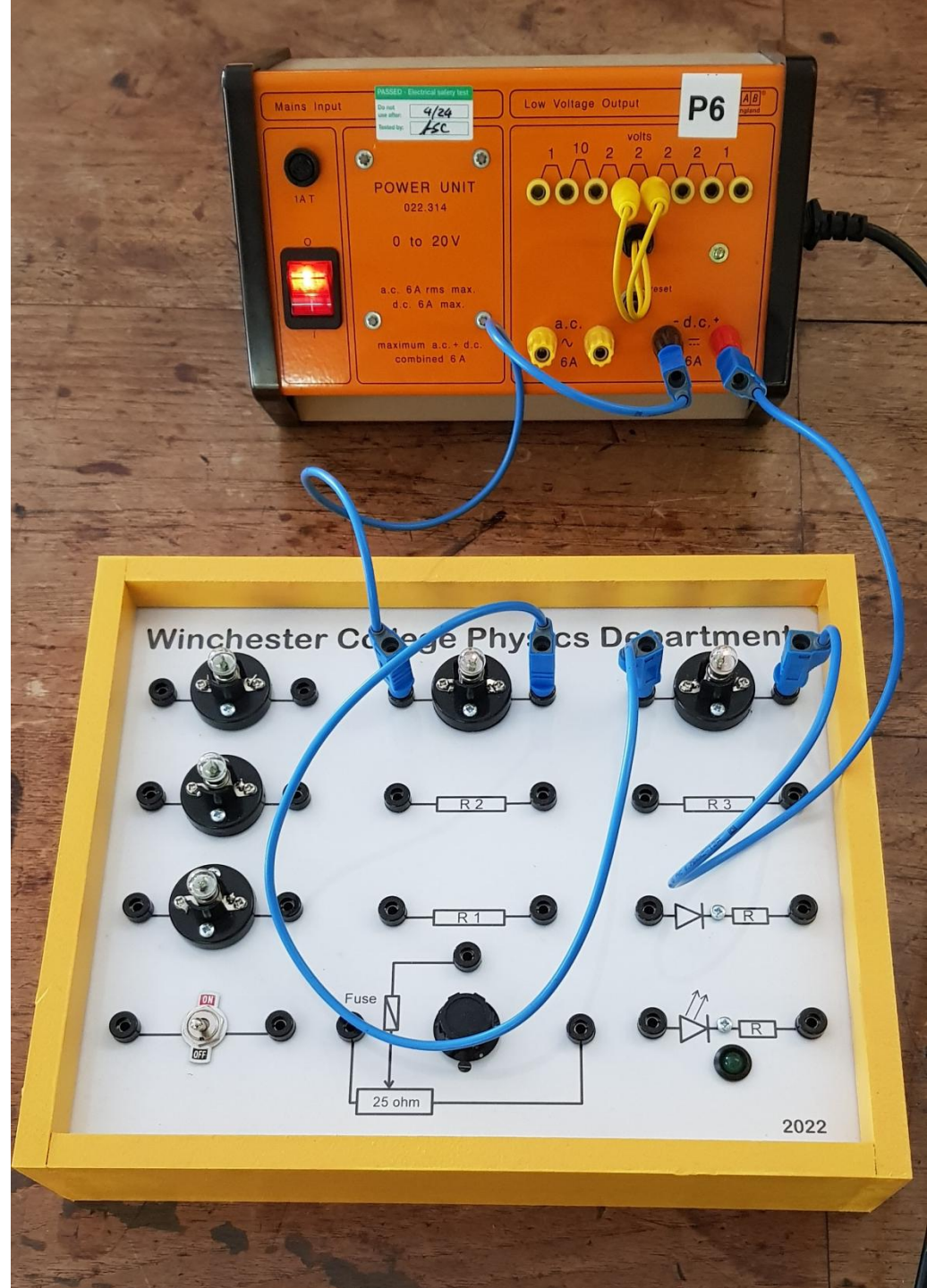Since 1 volt = 1 J of electrical energy transformed per coulomb of charge moved, this means *less energy per bulb* is converted into light (and heat)



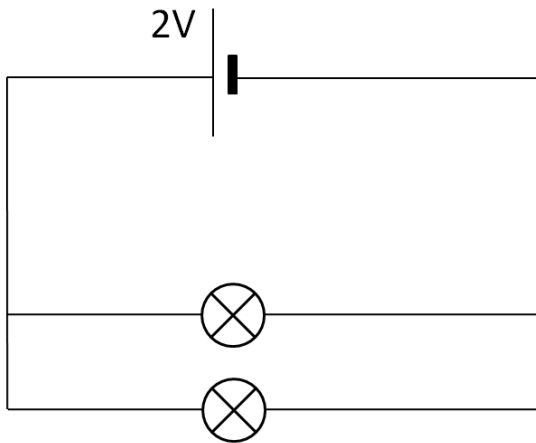
### Circuit #3 : Two filament bulbs in *parallel*

What happens to the brightness of the bulbs, compared to the *series* arrangement?




Each bulb is in a **parallel circuit branch**, and is *separately connected to the power supply*.

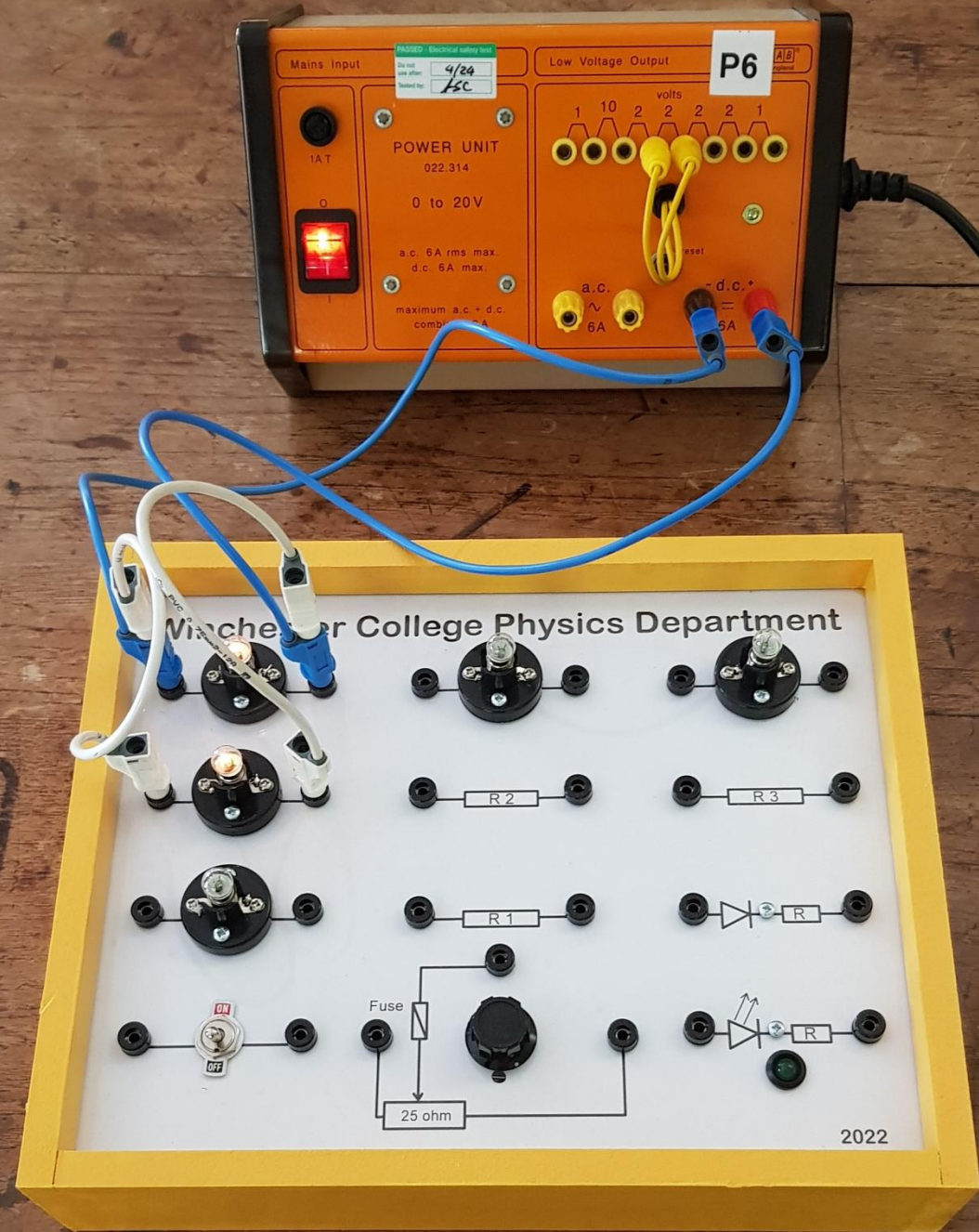Therefore 2V is applied to each bulb so both should be as bright as one bulb in series.


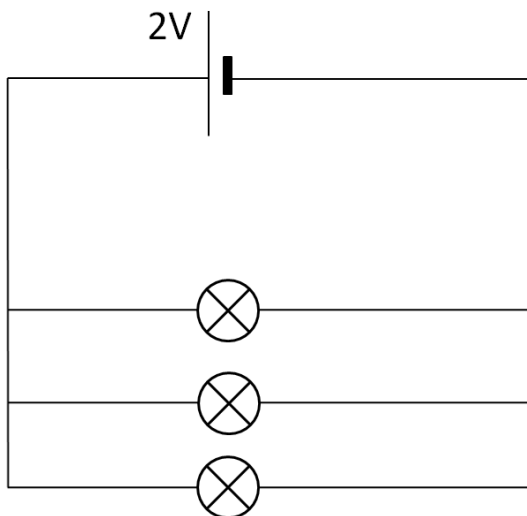
## Circuit #4 : Three filament bulbs in *parallel*

Add yet another bulb in parallel. Does the brightness change?



What do you think is happening to the amount of *current* drawn from the power supply? How does this compare to the *double* and *single* loops?




**Circuit #5a : Measure current for a single bulb series circuit**


Return to the original single series loop, but now connect an **ammeter** in series.

Write down your current (in Amps):


I = ..... A

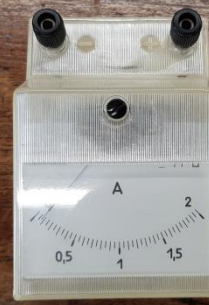

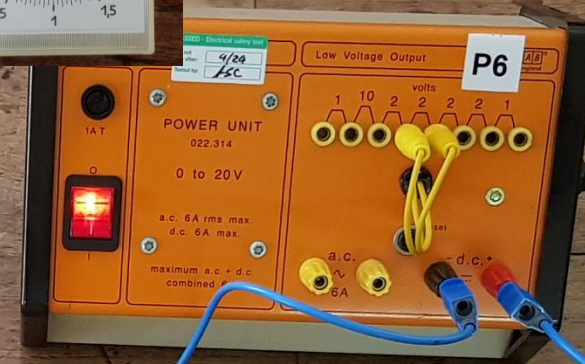
Note you may have an analogue ammeter instead of a digital one




In this case, the current is **0.17A**

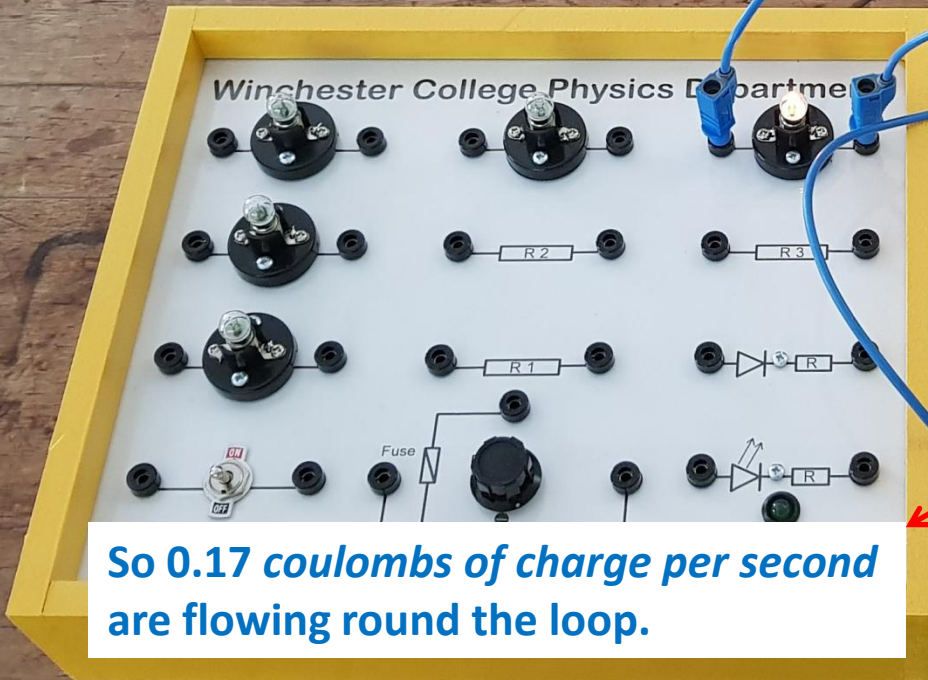

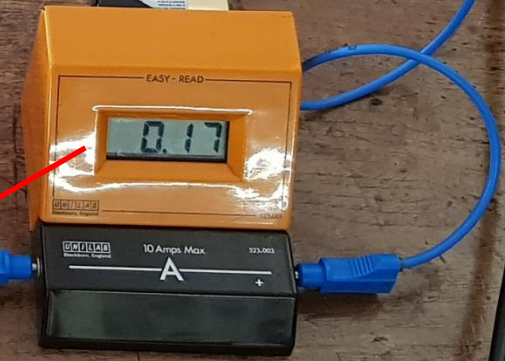So **0.17 coulombs of charge per second** are flowing round the loop.




**Ammeter**

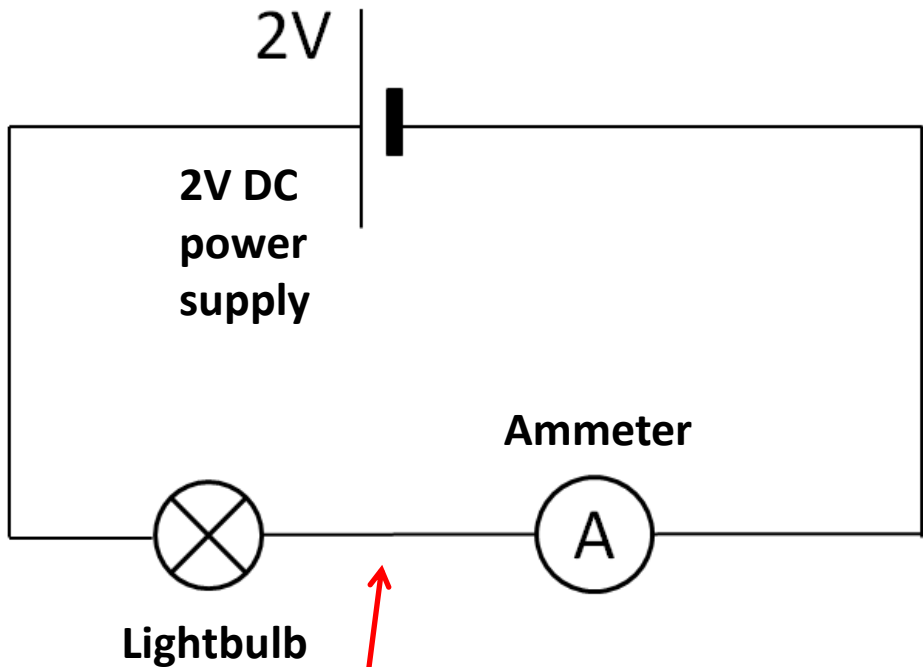

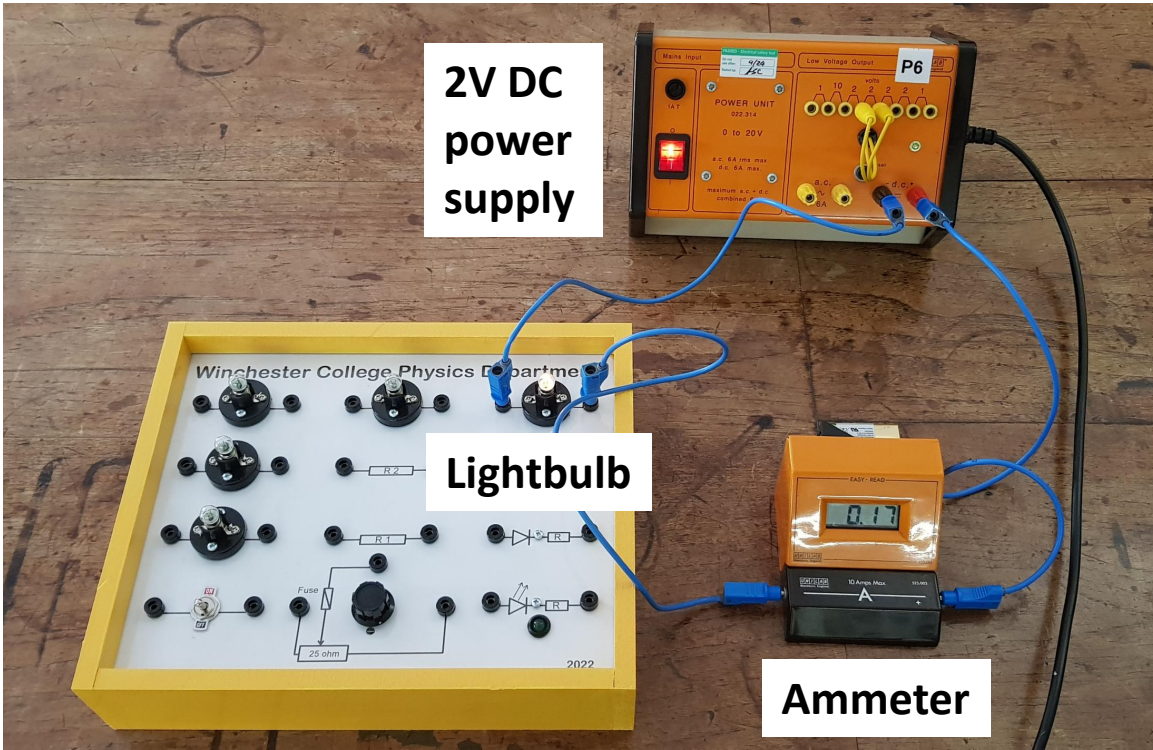**Circuit #5a : Measure current for a single bulb series circuit**

Return to the original single series loop, but now connect an **ammeter** in series.

Circuit diagram (sometimes called a 'schematic') vs the real kit





**Circuit #5b : Measure current and voltage for a single bulb series circuit**

Add a **voltmeter** in *parallel* to the filament bulb.

So 1.4V or 1.4 J/coulomb are being transformed across the bulb


**Voltmeter**


Write down your voltage (in volts):

V = ..... V

In this case, the current is 0.17A

**Ammeter**

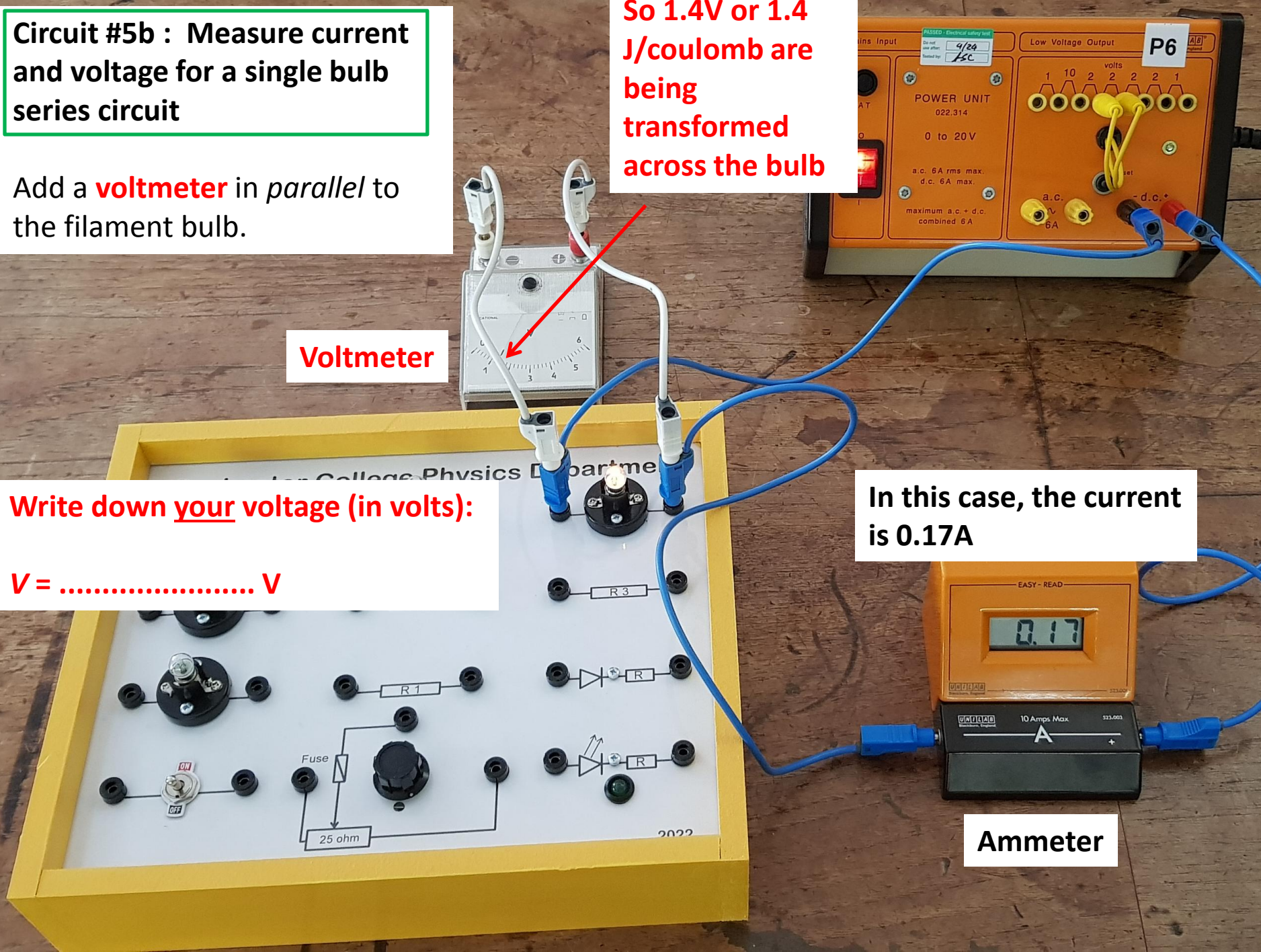

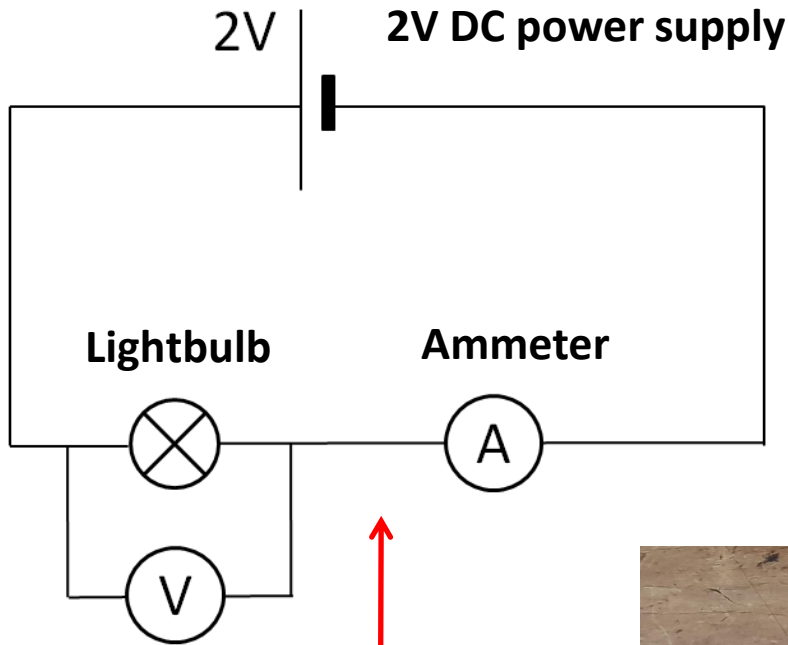


**Circuit #5b : Measure current and voltage for a single bulb series circuit**

Add a **voltmeter** in *parallel* to the filament bulb.

**Voltmeter**

Note how this is clearly in parallel

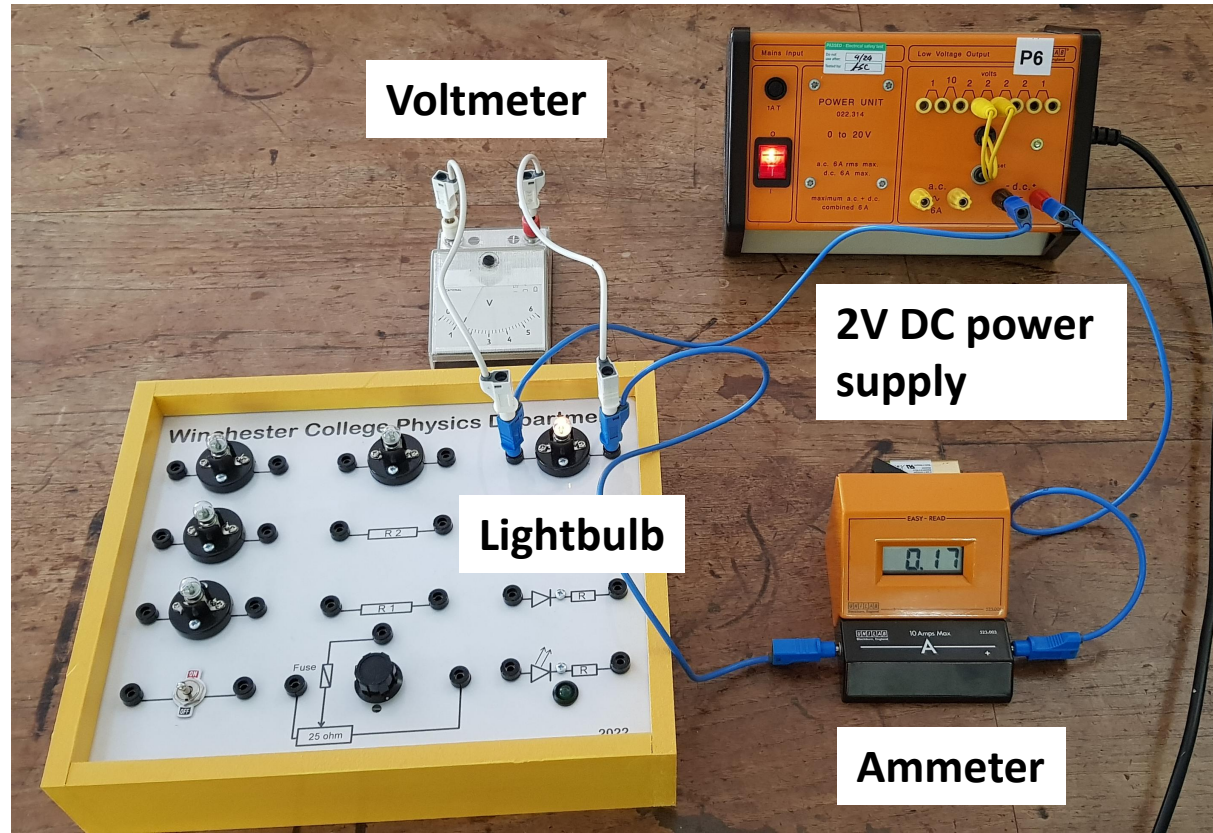**Circuit diagram (sometimes called a 'schematic') vs the real kit**





# Circuit #5c : Measure current and voltage for a single bulb series circuit

If you have the kit, try a **digital voltmeter** instead.

You'll gain an extra digit of precision.

Voltmeter

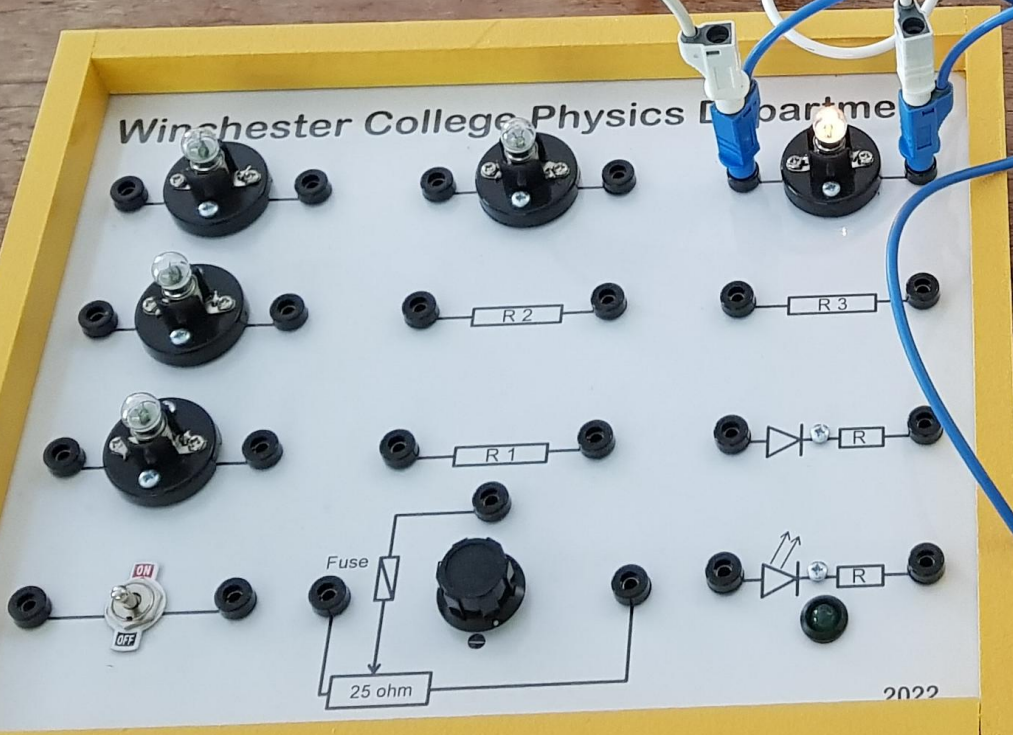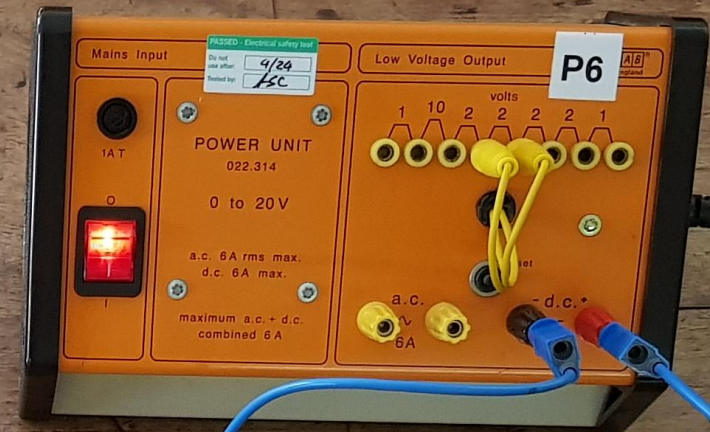


Ammeter

**Circuit #5d : Measure current and voltage for a single bulb series circuit**

Now measure the voltage across the **power supply**

Note the power supply provides 1.40V, *not exactly 2V*. The power unit voltage labels are only approximate.

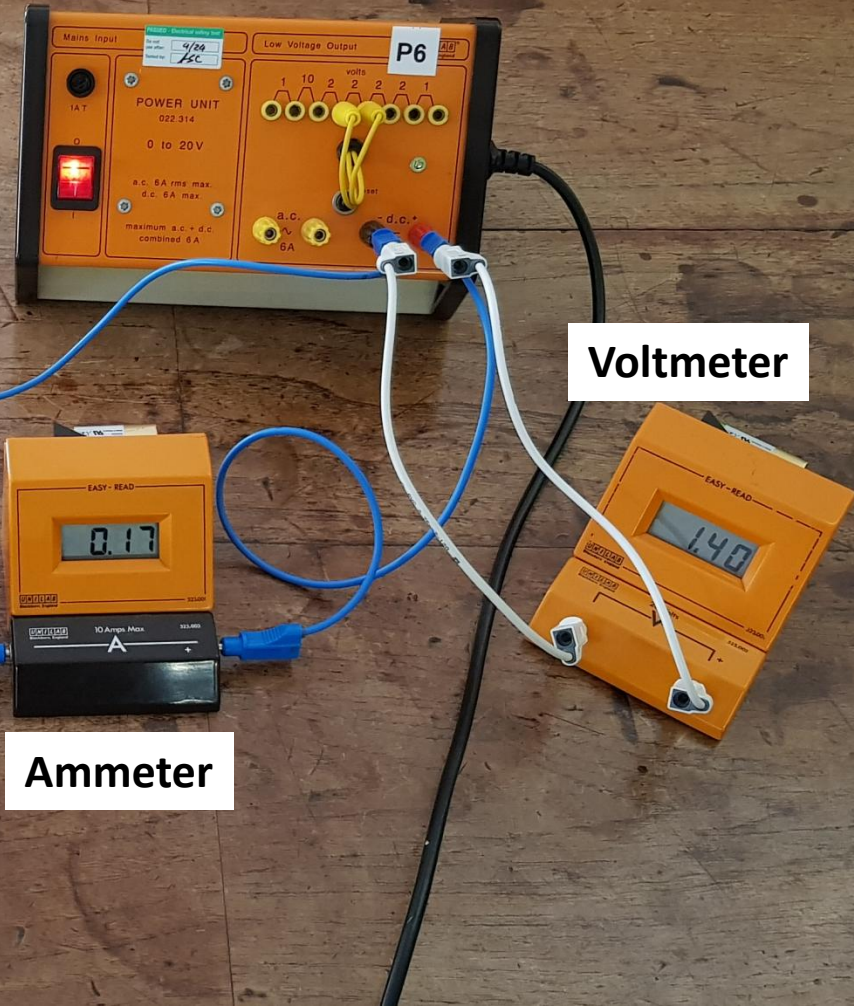It should be *slightly higher* than the *potential difference (i.e. voltage)* across the light bulb, as some energy will be dissipated in the wires and the electrical connections.




Voltmeter

Ammeter


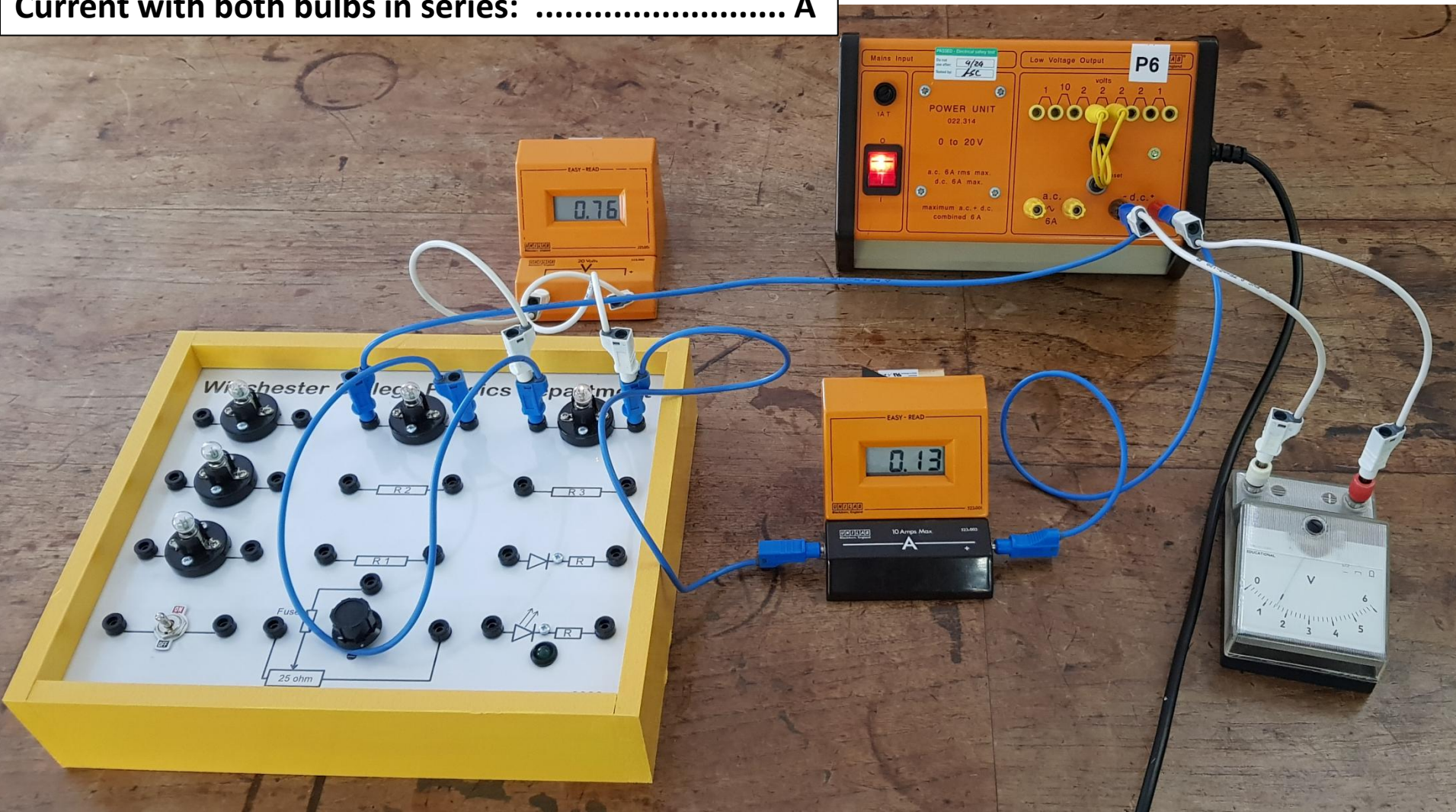
**Circuit #6 : Measure current and voltage for two bulbs in series**

**Voltage across power supply: ..... V**  
**Voltage across first bulb: ..... V**  
**Voltage across second bulb: ..... V**

**Current with only one bulb in series: ..... A**  
**Current with both bulbs in series: ..... A**





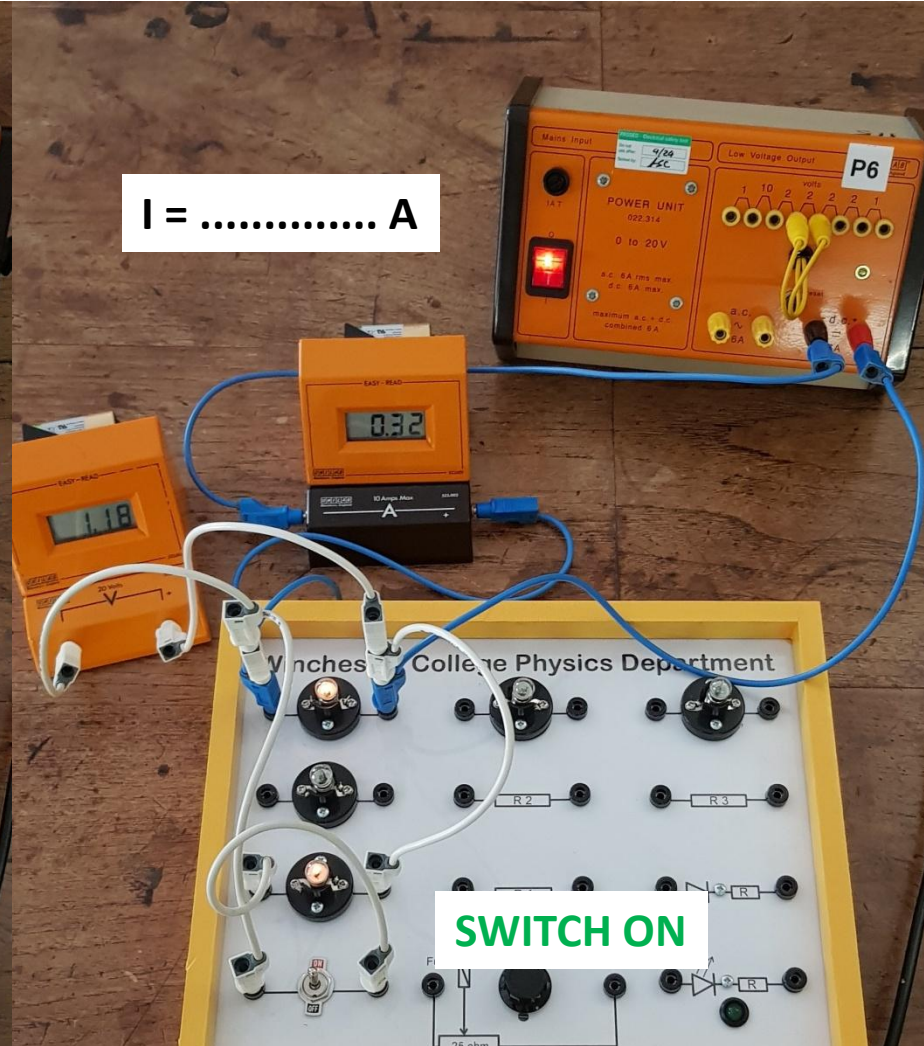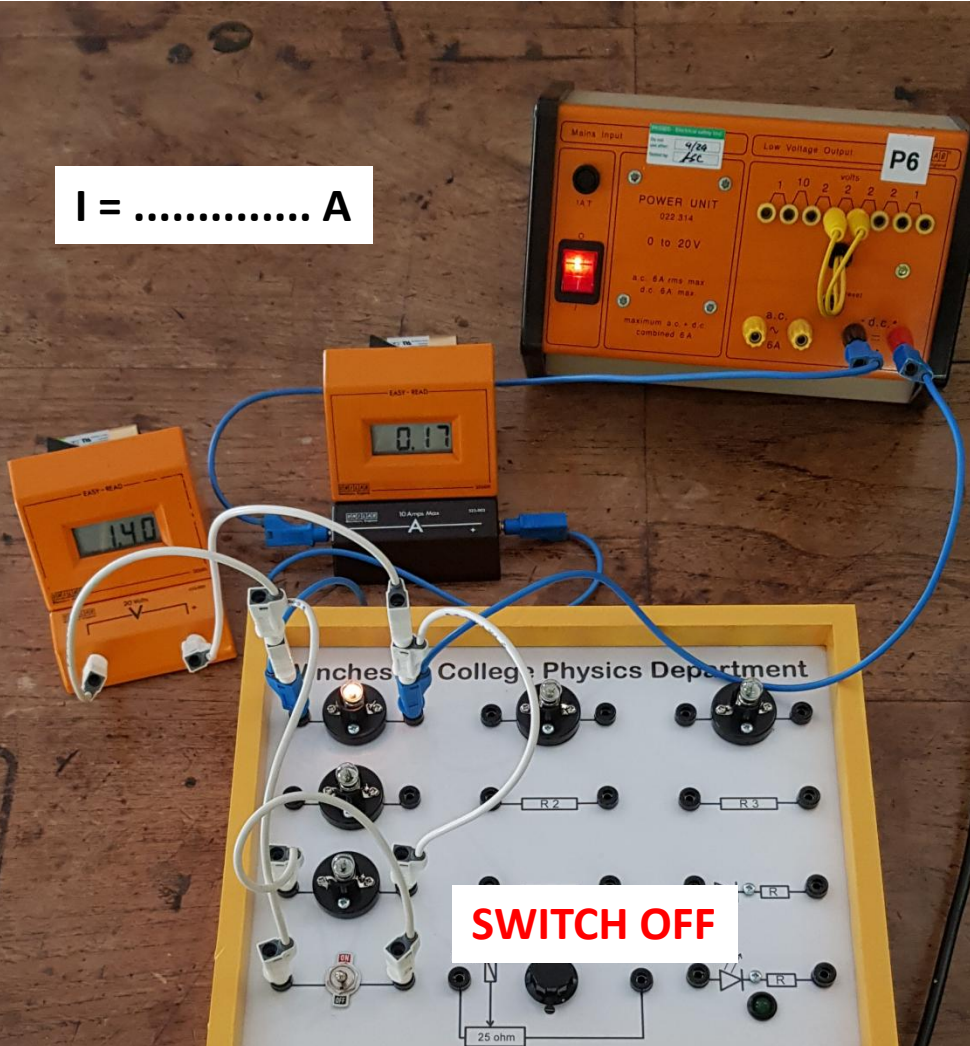**Circuit #7: Connect two bulbs in parallel, with the second loop in series with a switch. Record how the voltage across the first bulb, and the total current drawn change as the switch position is changed.**



**The voltage across each bulb in parallel should be the same, (check it by moving the voltmeter across the lower bulb) but you might observe a small difference before and after the switch. The total current draw should *approximately double* when the switch is ON.**

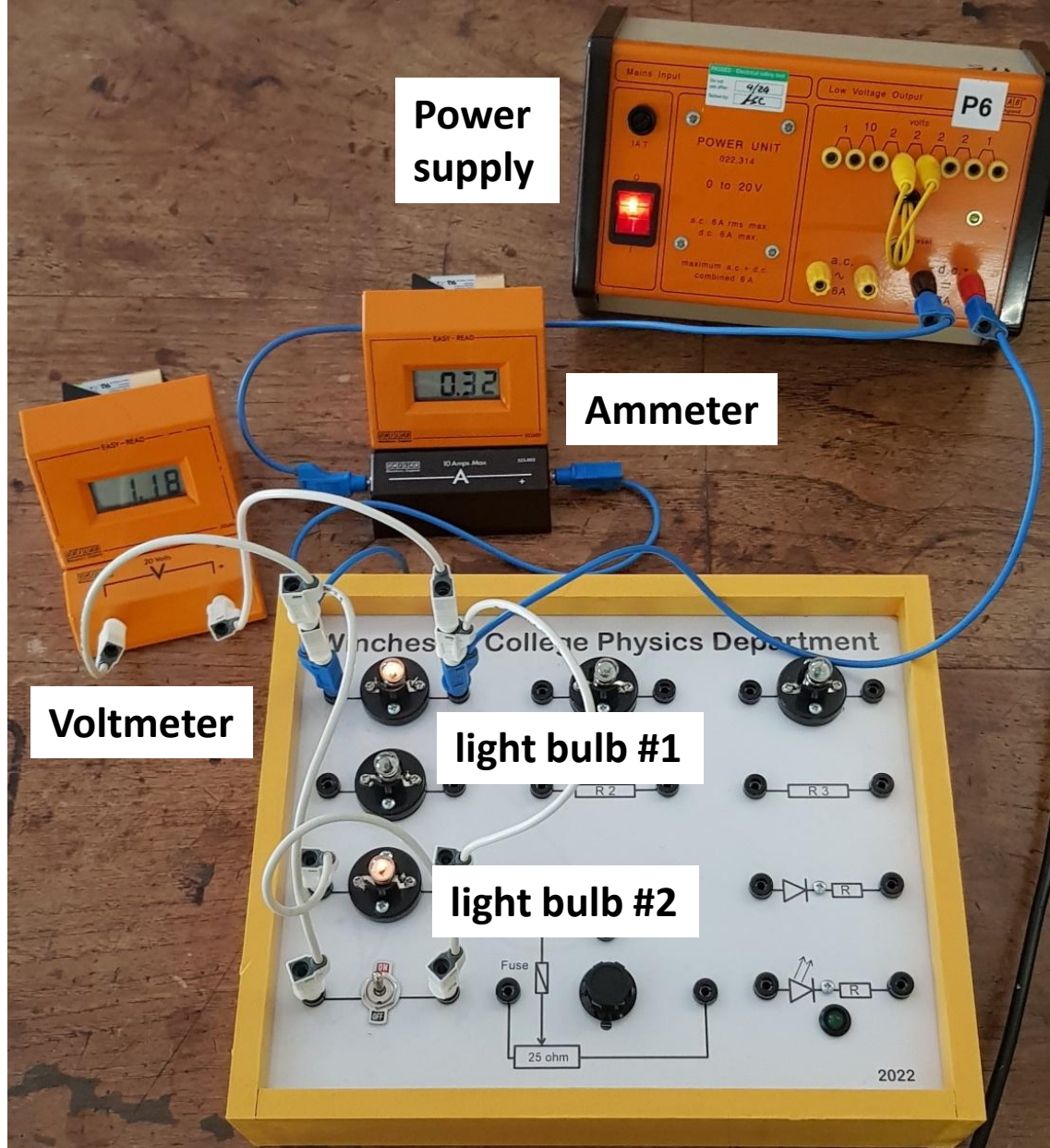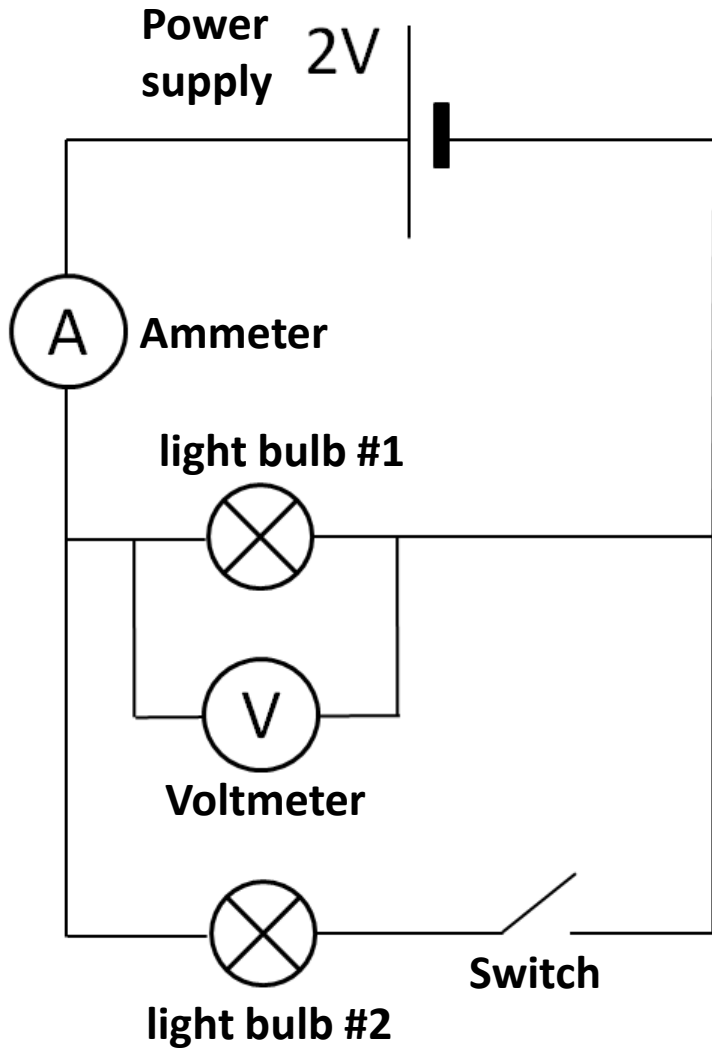**Circuit #7: Connect *two bulbs in parallel*, with the *second loop in series with a switch*.**



**NOW YOU HAVE  
MASTERED THE BASICS  
LET'S USE SOME MORE  
ADVANCED**

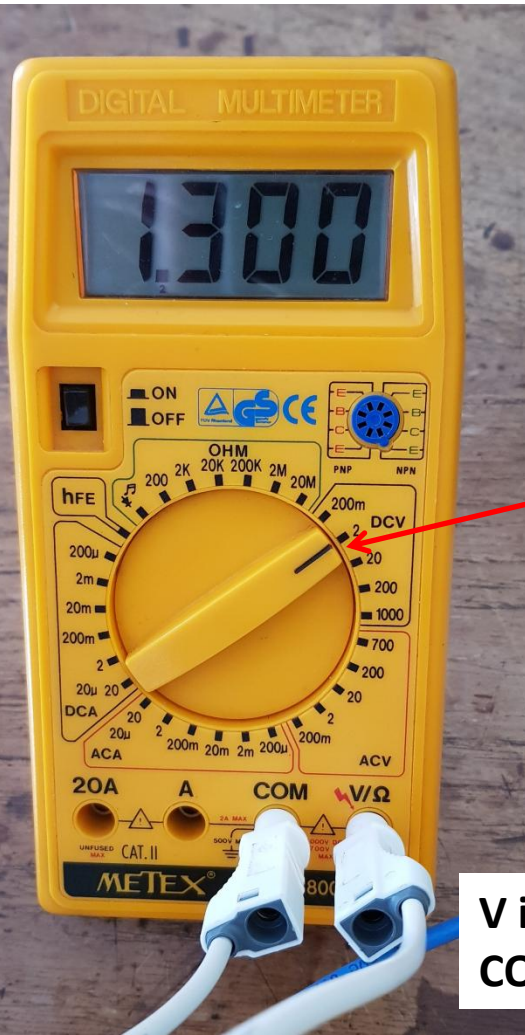
**EQUIPMENT!**






\* Always set a multimeter to the desired setting BEFORE turning it on a plugging it into a circuit \*

An ammeter used as a voltmeter (i.e. placed in parallel to a circuit) will cause it to blow its fuse.



DC voltmeter  
setting

V is positive  
COM is negative

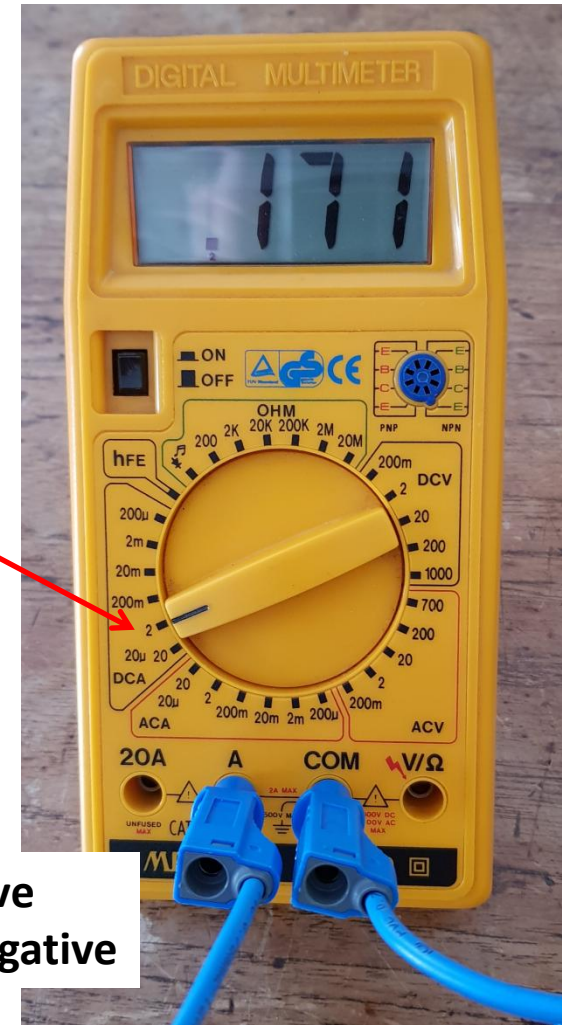



DC ammeter  
setting

A is positive  
COM is negative


Voltmeter



Ammeter

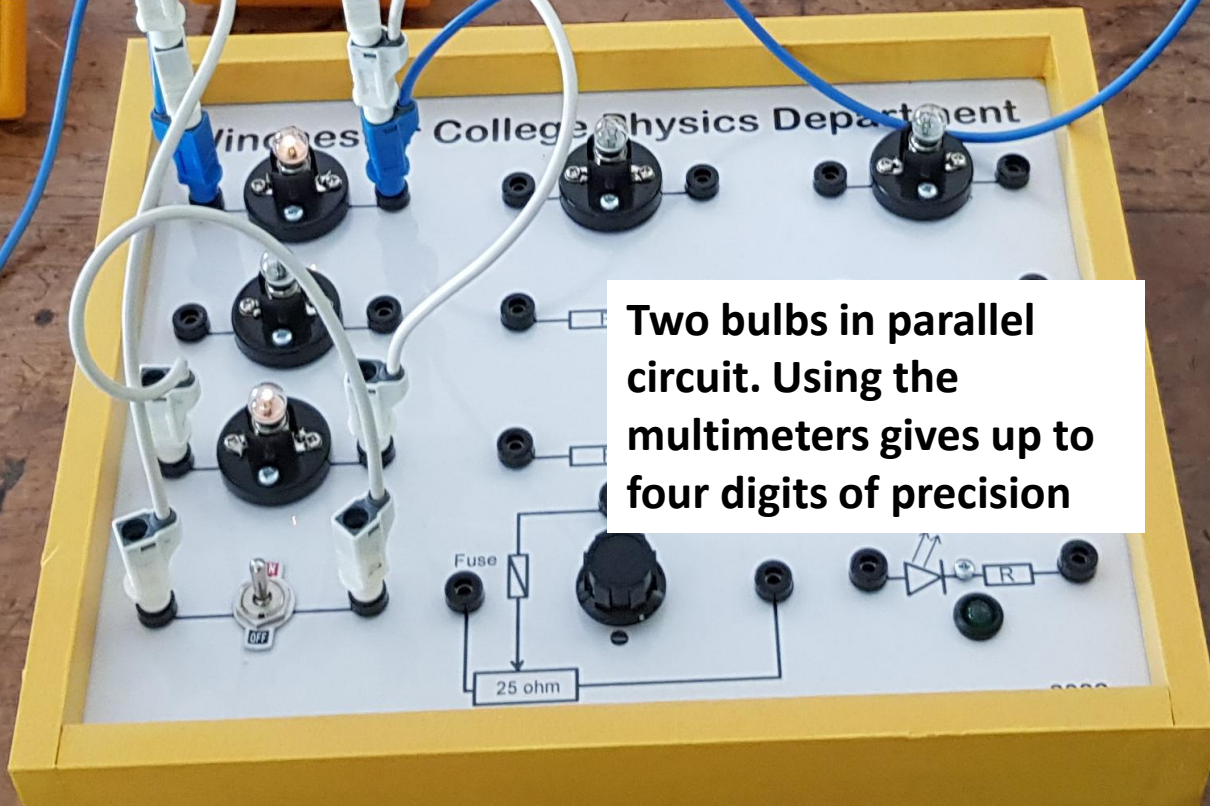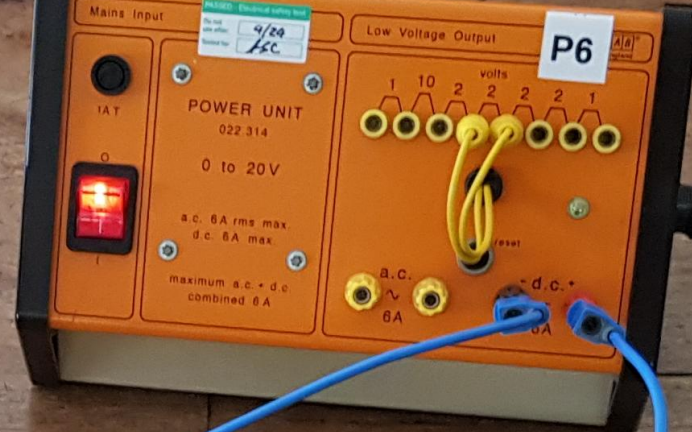

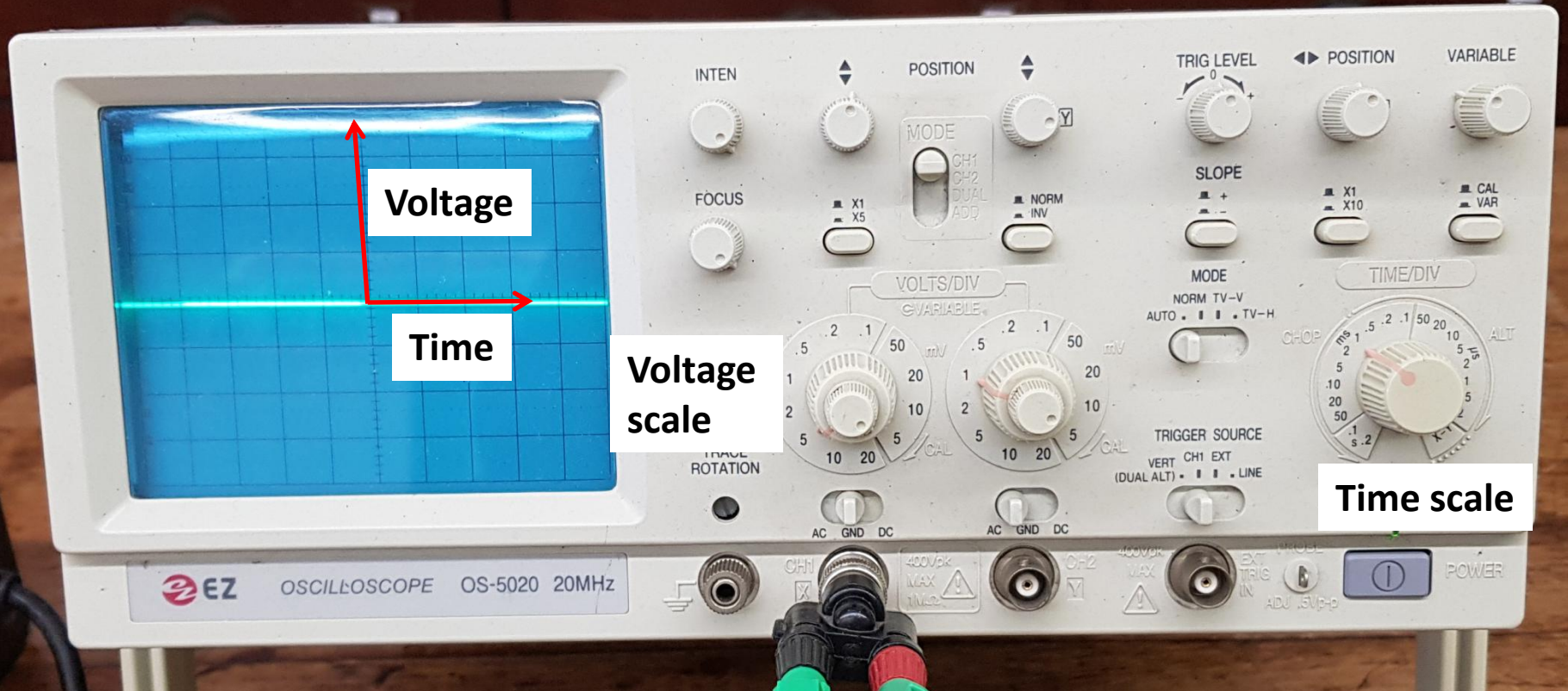Two bulbs in parallel circuit. Using the multimeters gives up to four digits of precision



This is called a **Cathode Ray Oscilloscope (CRO)**.  
The screen gives voltage (vertical) vs time (horizontal). Set the dials for scales.




We'll use the CRO  
like a voltmeter, using the  
BNC cable adapter.

Connect to Channel 1  
(CH1)



Set up the oscilloscope across the terminals of a single bulb in a series circuit. Also have a voltmeter in parallel.

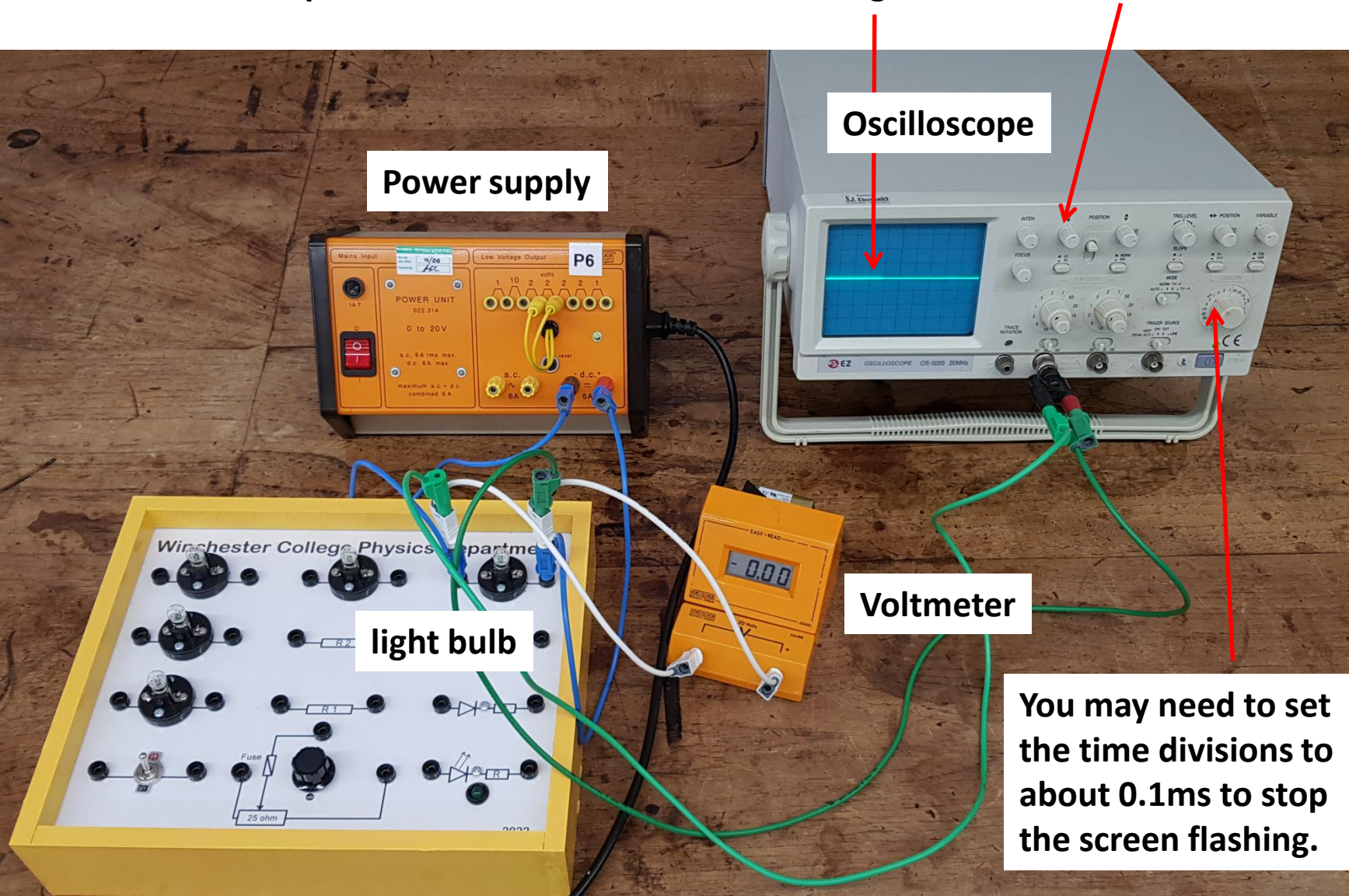Use the vertical position knob to set the horizontal signal level to zero.



Power supply

Oscilloscope



light bulb

Voltmeter

You may need to set the time divisions to about 0.1ms to stop the screen flashing.

Now turn the circuit on. The oscilloscope should show a voltage which has an average of what the voltmeter reads – but you may see a bit of a ‘saw-tooth’ time variation. The supposedly DC voltage from the power supply may not be perfectly constant!

‘saw tooth’ signal

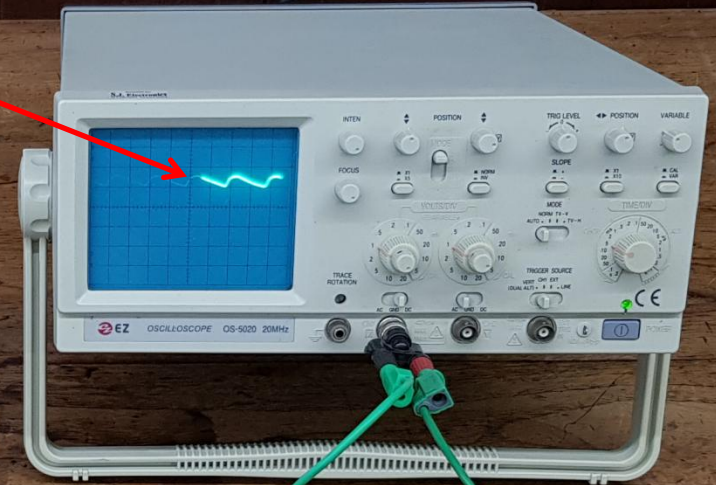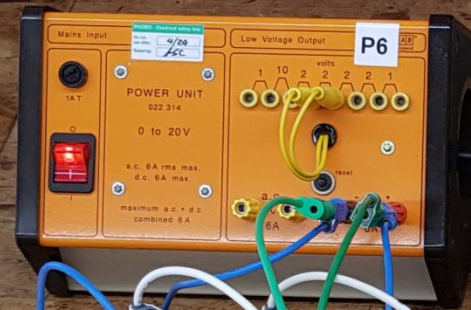


DC voltage across bulb




Move the green wires from the power supply to the bulb. There shouldn't be much of a difference.

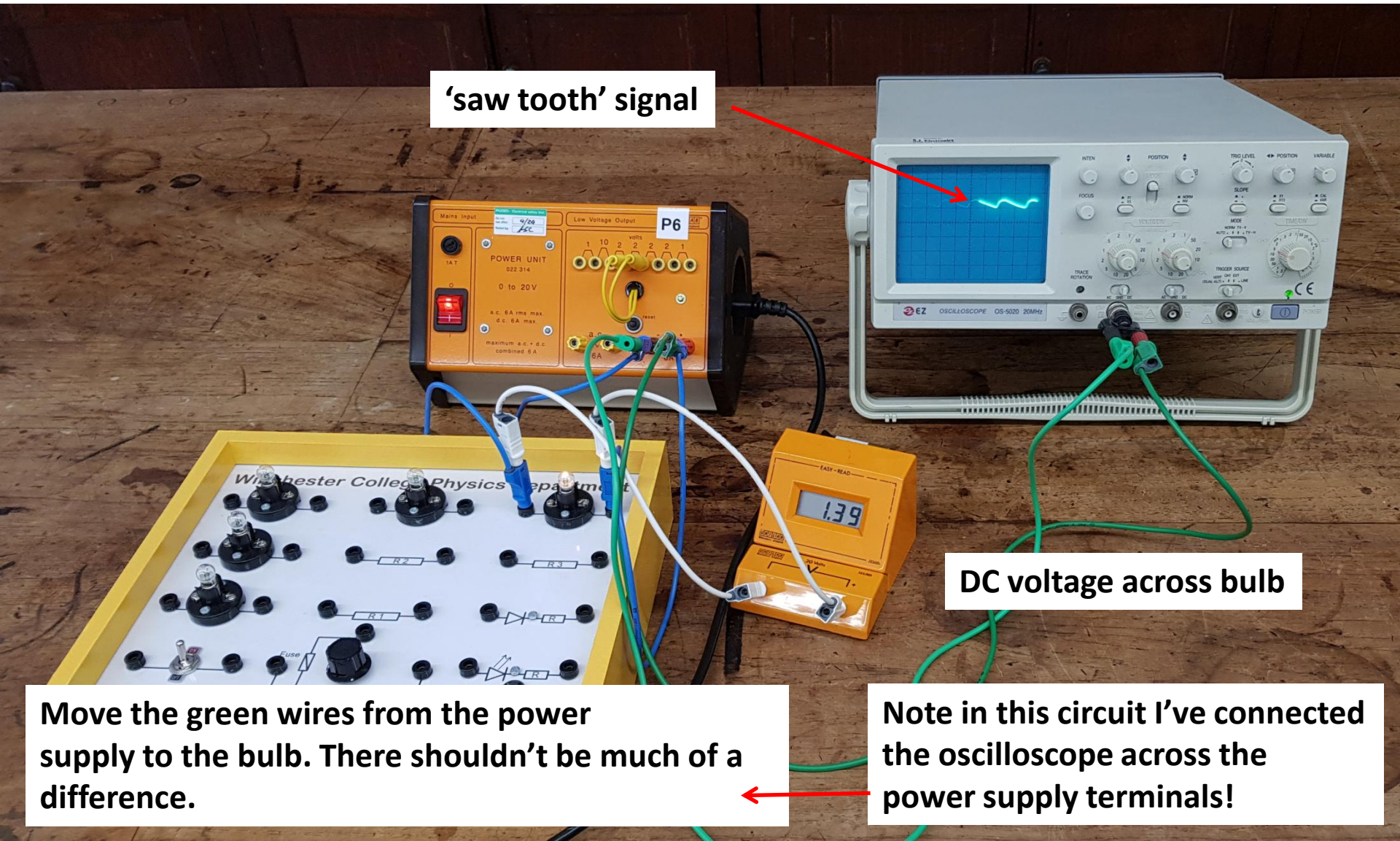Note in this circuit I've connected the oscilloscope across the power supply terminals!



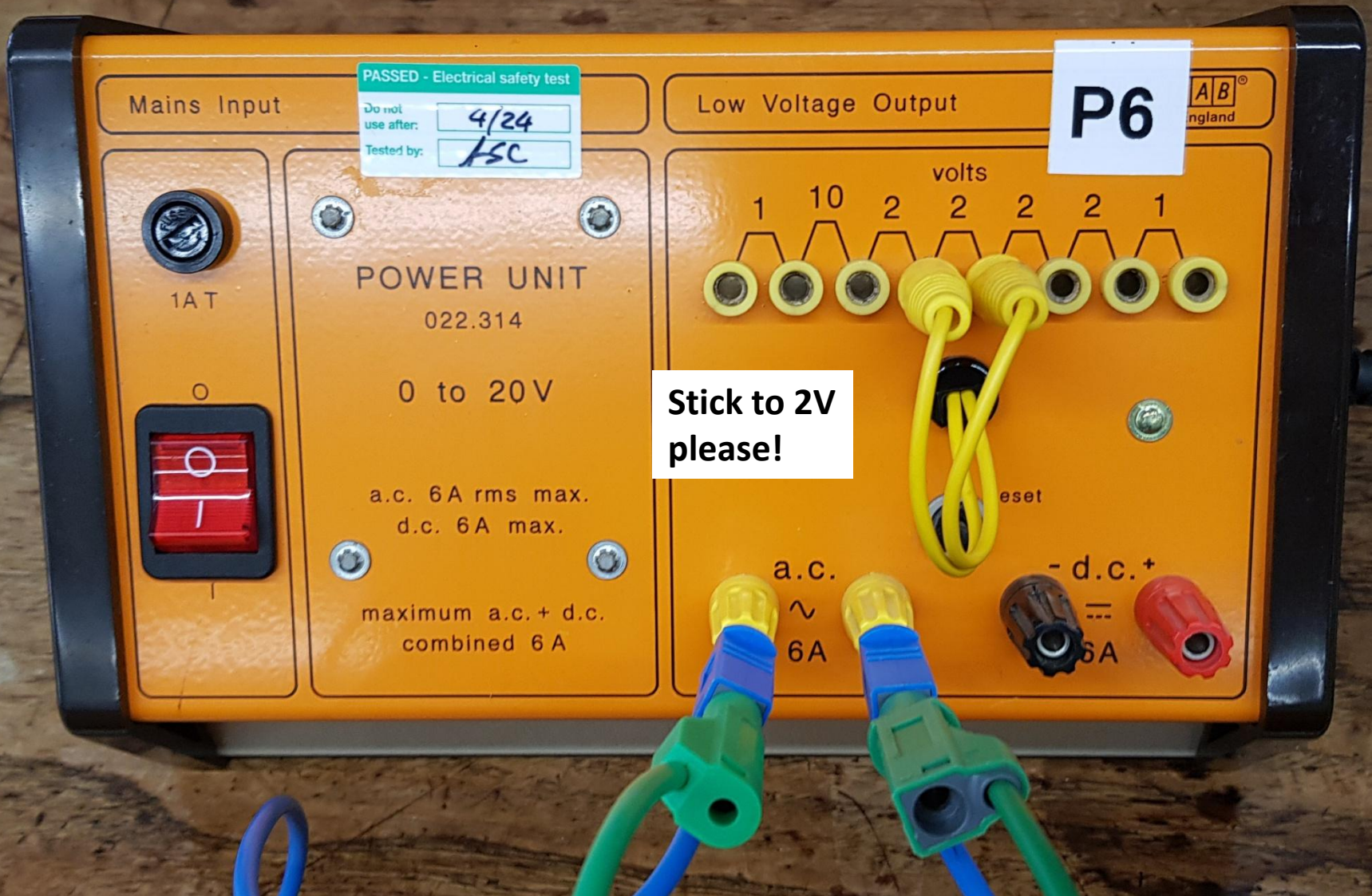
Turn the power off and swap the power supply output to AC



**AC** Alternating Current

**DC** Direct Current

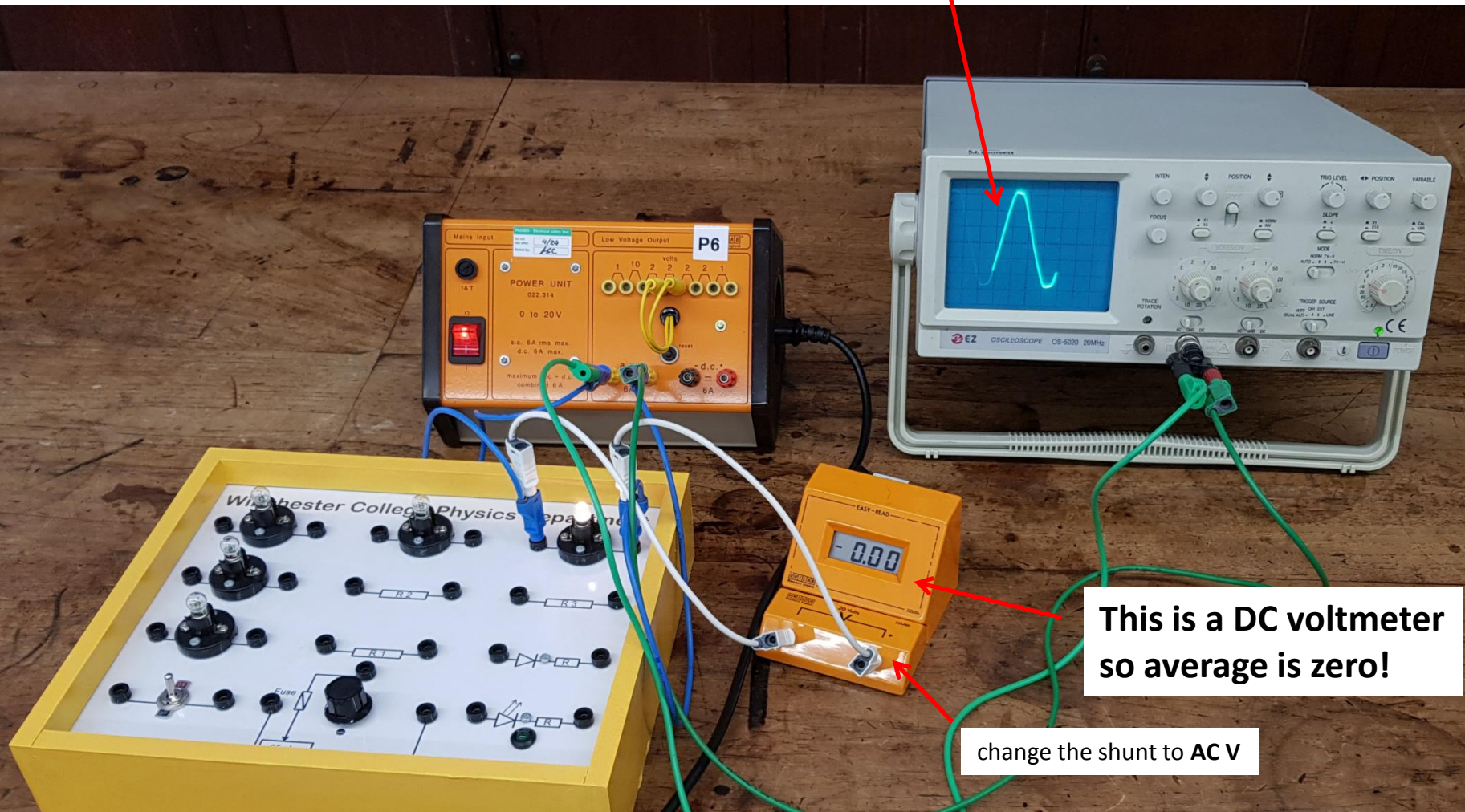You should now see a *sinusoidal* trace of *period* (time between wave peaks) of about  $1/50 \text{ s} = 0.02 \text{ s}$ . This is because the AC (Alternating Current) output of the power supply is the same **50Hz frequency** as mains electricity in the UK.



This is a DC voltmeter so average is zero!

change the shunt to AC V

Exchange the voltmeter for one with an AC mode and hopefully you'll see the **square root of half the square of the maximum voltage shown**. This is called the **RMS voltage**, and is equivalent to the DC voltage of the *same average power*. (More about this in a later course!)