
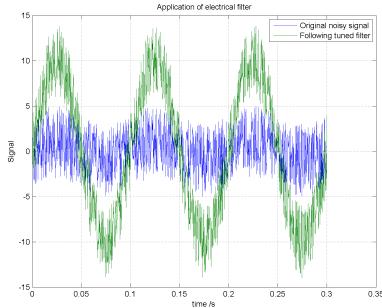



Simple Harmonic Motion (SHM) and Electrical Oscillations

Dr Andrew French
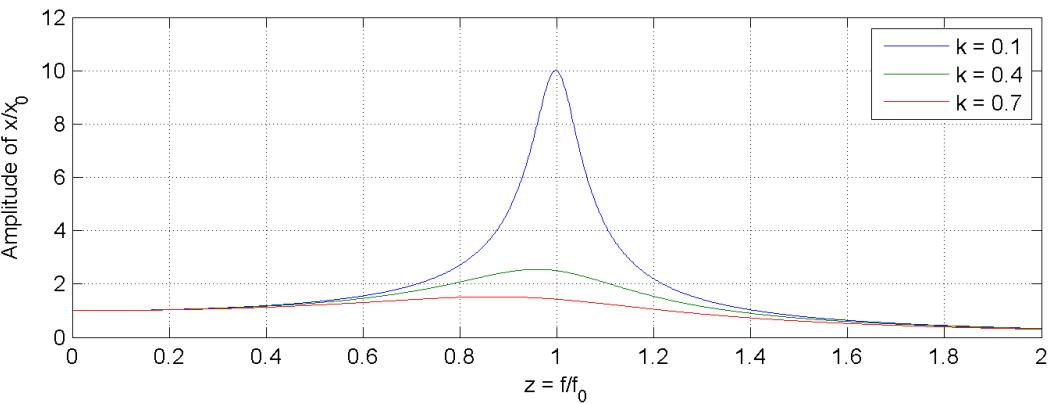
$$\frac{d^2x}{dt^2} + 2\gamma \frac{dx}{dt} + \omega_0^2 x = A_0 e^{i\omega t}$$



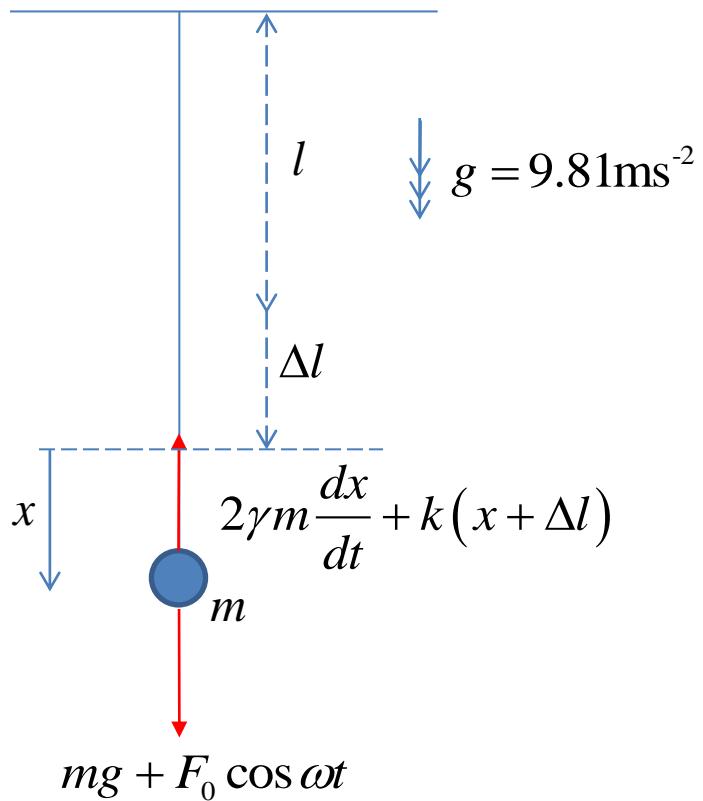SHM equation from driven mechanical oscillations



$$\omega = 2\pi f$$

oscillation frequency

By Newton's Second Law:

Consider a particle of mass m suspended from a light elastic string from a fixed surface. The string has natural length l .

Assume a *Hookean* law of elasticity i.e. restoring force is proportional to extension. The elastic constant in this case is k .


Also assume mass is subject to air resistance which is proportional to velocity and mass m .

The mass is also pulled 'driven' via an oscillatory force of magnitude F_0 and frequency $f = \omega/2\pi$

In the absence of any driving force, the mass rests at string extension Δl . It is assumed at time $t = 0$ that extension from this equilibrium point, (x), is zero and the mass is at instantaneous rest.

$$m \frac{d^2x}{dt^2} = mg + F_0 \cos \omega t - 2\gamma m \frac{dx}{dt} - k(x + \Delta l)$$

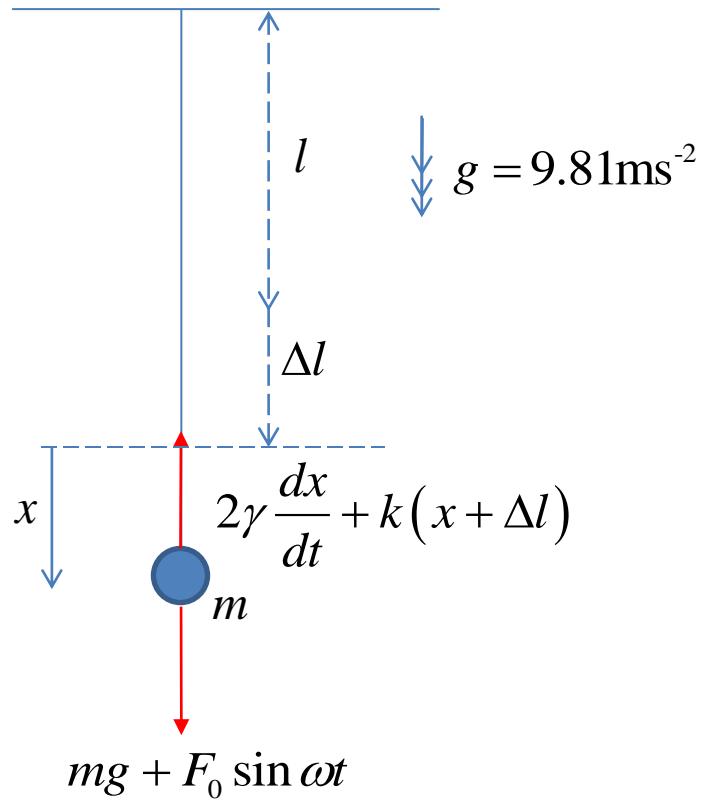SHM equation from driven mechanical oscillations



By Newton's Second Law:

$$m \frac{d^2x}{dt^2} = mg + F_0 \sin \omega t - 2\gamma m \frac{dx}{dt} - k(x + \Delta l)$$

At equilibrium $x = 0, F_0 = 0$

$$0 = mg - k\Delta l$$

$$\therefore \Delta l = \frac{mg}{k}$$

Hence:

$$m \frac{d^2x}{dt^2} + 2\gamma m \frac{dx}{dt} + kx = F_0 \sin \omega t$$

$$\boxed{\frac{d^2x}{dt^2} + 2\gamma \frac{dx}{dt} + \frac{k}{m}x = \frac{F_0}{m} \sin \omega t}$$

This equation has a very similar form to the generic equation of **Simple Harmonic Motion (SHM)**

$$\boxed{\frac{d^2x}{dt^2} + 2\gamma \frac{dx}{dt} + \omega_0^2 x = A_0 \sin \omega t}$$

$$\frac{d^2x}{dt^2} + 2\gamma \frac{dx}{dt} + \omega_0^2 x = A_0 \sin \omega t \quad \text{can have oscillatory solutions if } \gamma < \omega_0$$

The general solution is: $x(t) = Ae^{-\gamma t} \cos\left(t\sqrt{\omega_0^2 - \gamma^2} - \Phi\right) + B \sin(\omega t - \phi)$


'Transient solution' (which exponentially decays)

Steady state oscillation at same frequency as driving force

Transient amplitude and phase

$$\Phi = \tan^{-1} \left(\frac{\dot{x}_0 + \gamma(x_0 + B \sin \phi) - B \omega \cos \phi}{(x_0 + B \sin \phi) \sqrt{\omega_0^2 - \gamma^2}} \right)$$
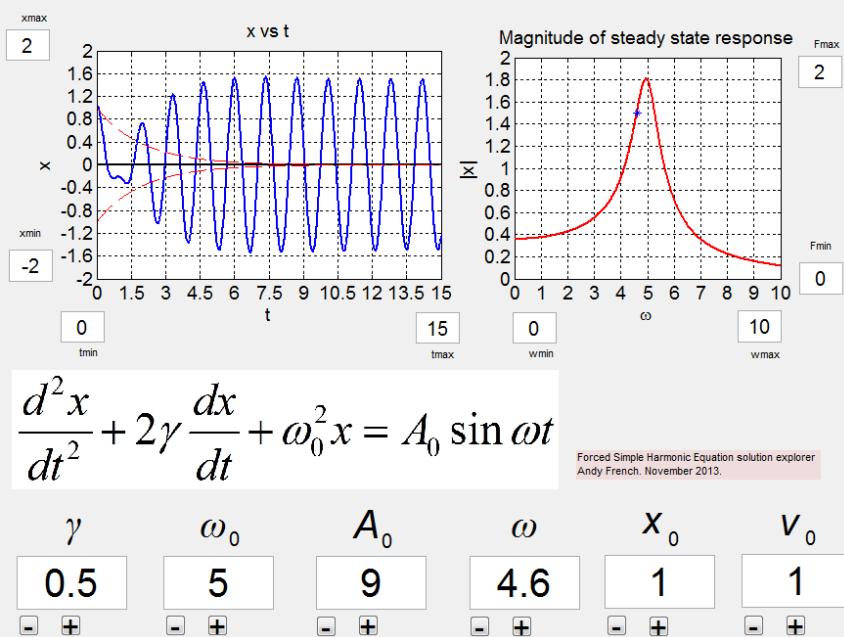
$$A = \frac{x_0 + B \sin \phi}{\cos \Phi}$$



The *steady state amplitude* exhibits **resonance phenomenon** i.e. it has a *maximum* at a particular 'resonance frequency'

$$B = \frac{A_0}{\sqrt{(\omega_0^2 - \omega^2)^2 + 4\gamma^2\omega^2}}$$

$$\phi = \tan^{-1} \left(\frac{2\gamma\omega}{\omega_0^2 - \omega^2} \right)$$

B_{\max} when $\omega = \sqrt{\omega_0^2 - 2\gamma^2}$

$$\frac{d^2x}{dt^2} + 2\gamma \frac{dx}{dt} + \omega_0^2 x = A_0 \sin \omega t \quad \text{can have oscillatory solutions if } \gamma < \omega_0$$

$$x(t) = B \sin(\omega t - \phi) \quad \text{Steady state oscillation at same frequency as driving force}$$

$$B = \frac{A_0}{\sqrt{(\omega_0^2 - \omega^2)^2 + 4\gamma^2\omega^2}}$$

$$B_{\max} \text{ when } \frac{d}{d\omega} \left\{ (\omega_0^2 - \omega^2)^2 + 4\gamma^2\omega^2 \right\} = 0$$


$$2(\omega_0^2 - \omega^2)(-2\omega) + 8\gamma^2\omega = 0$$

$$\omega(2\gamma^2 - \omega_0^2 + \omega^2) = 0$$

$$\omega^2 = \omega_0^2 - 2\gamma^2$$

$$\omega = \sqrt{\omega_0^2 - 2\gamma^2}$$
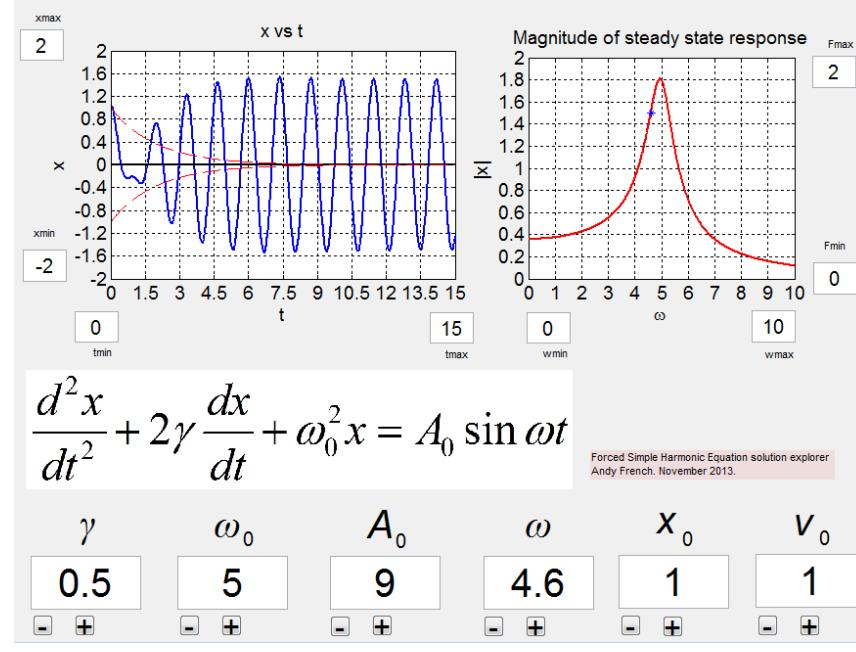
$$B_{\max} \text{ when } \omega = \sqrt{\omega_0^2 - 2\gamma^2}$$



The **steady state amplitude** exhibits **resonance phenomenon** i.e. it has a **maximum** at a particular 'resonance frequency'

$$\omega_{\max} = \sqrt{\omega_0^2 - 2\gamma^2}$$

$$\therefore (\omega_0^2 - \omega^2)^2 + 4\gamma^2 \omega^2$$

$$= (\omega_0^2 - \omega_0^2 - 2\gamma^2)^2 + 4\gamma^2 (\omega_0^2 - 2\gamma^2)$$

$$= 4\gamma^4 + 4\gamma^2 \omega_0^2 - 8\gamma^4$$

$$= 4\gamma^2 \omega_0^2 - 4\gamma^4$$

$$\therefore B_{\max} = \frac{A_0}{\sqrt{(\omega_0^2 - \omega^2)^2 + 4\gamma^2 \omega^2}}$$



$$B_{\max} = \frac{A_0}{\sqrt{4\gamma^2 \omega_0^2 - 4\gamma^4}}$$

$$B_{\max} = \frac{A_0}{2\gamma \sqrt{\omega_0^2 - \gamma^2}}$$


$$\frac{d^2x}{dt^2} + 2\gamma \frac{dx}{dt} + \omega_0^2 x = A_0 \sin \omega t$$

$$x = \frac{A_0}{\sqrt{(\omega_0^2 - \omega^2)^2 + 4\gamma^2 \omega^2}} \sin(\omega t - \phi)$$
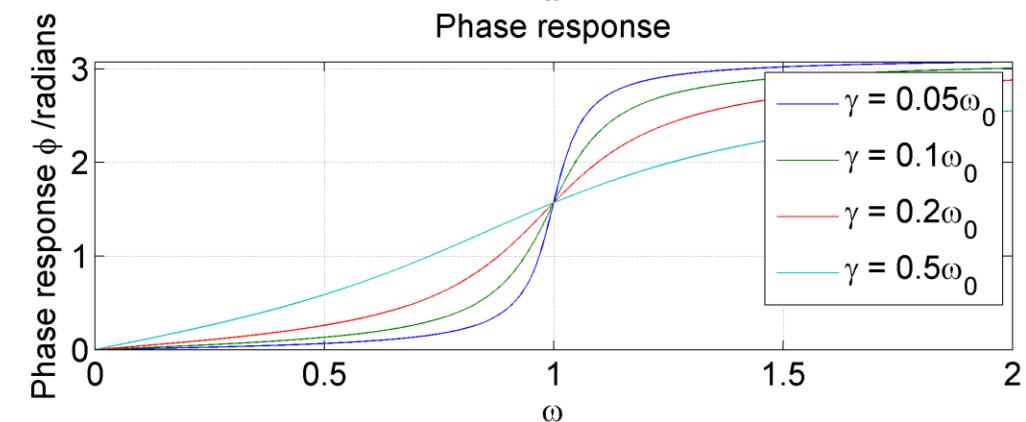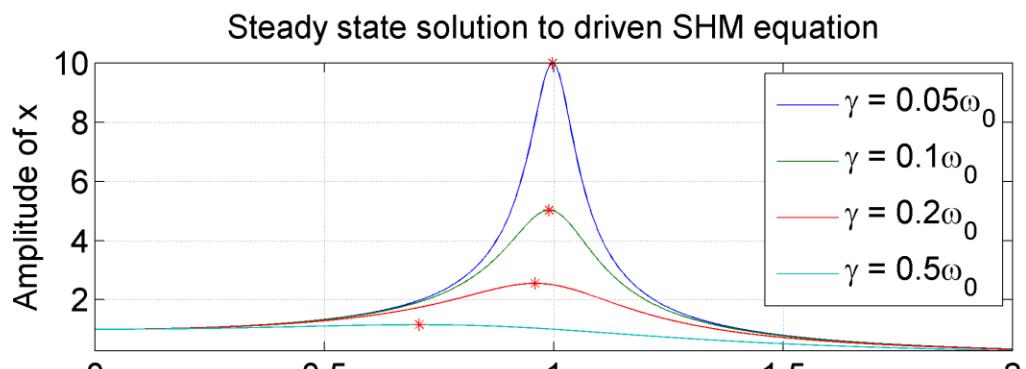
$$\phi = \tan^{-1} \left(\frac{2\gamma\omega}{\omega_0^2 - \omega^2} \right)$$



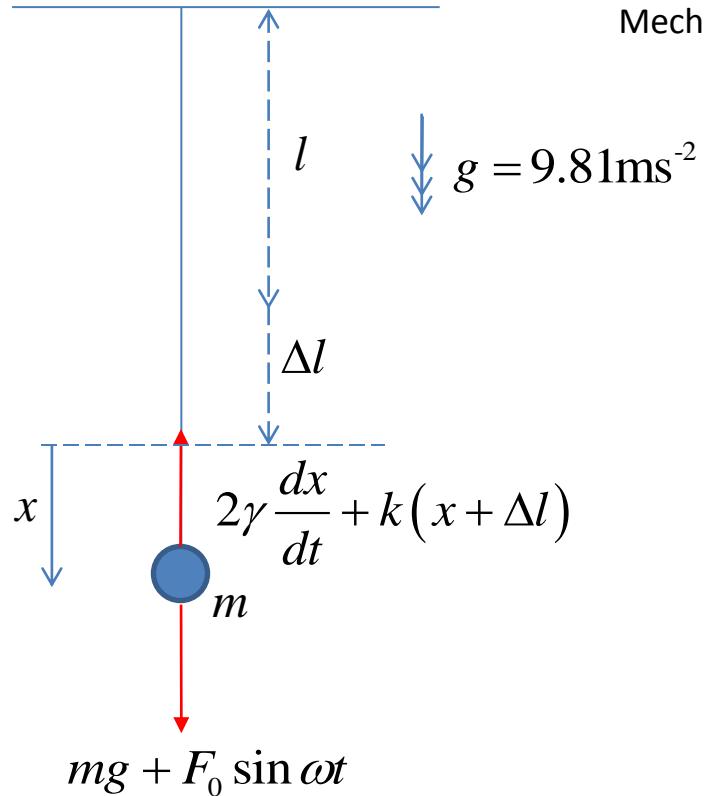SHM parameters for the driven mechanical oscillator



Mechanical oscillator

$$\frac{d^2x}{dt^2} + 2\gamma \frac{dx}{dt} + \frac{k}{m} x = \frac{F_0}{m} \sin \omega t$$

SHM

$$\frac{d^2x}{dt^2} + 2\gamma \frac{dx}{dt} + \omega_0^2 x = A_0 \sin \omega t$$

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{k}{m}}$$

$\omega_0 = 2\pi f_0$

Natural oscillation frequency

$$A_0 = \frac{F_0}{m}$$

$$\omega_{\text{res}} = \sqrt{\omega_0^2 - 2\gamma^2}$$

Resonance frequency

Solving the SHM equation (steady state) using **complex variables**

$$\frac{d^2x}{dt^2} + 2\gamma \frac{dx}{dt} + \omega_0^2 x = A_0 e^{i\omega t}$$

$$x = Be^{i(\omega t - \phi)}$$

$$(-\omega^2 + 2i\gamma\omega + \omega_0^2)Be^{i(\omega t - \phi)} = A_0 e^{i\omega t}$$

$$(-\omega^2 + 2i\gamma\omega + \omega_0^2)Be^{-i\phi} = A_0$$

$$B = \frac{A_0}{|-\omega^2 + 2i\gamma\omega + \omega_0^2|}$$

$$B = \frac{A_0}{\sqrt{(\omega_0^2 - \omega^2)^2 + 4\gamma^2\omega^2}}$$

$$\phi = \arg(-\omega^2 + 2i\gamma\omega + \omega_0^2)$$

$$\phi = \tan^{-1}\left(\frac{2\gamma\omega}{\omega_0^2 - \omega^2}\right)$$

$$x = Be^{i(\omega t - \phi)}$$

$$x = B \cos(\omega t - \phi) + iB \sin(\omega t - \phi)$$

$$\frac{d^2x}{dt^2} + 2\gamma \frac{dx}{dt} + \omega_0^2 x = A_0 \cos \omega t$$

$$x = \frac{A_0}{\sqrt{(\omega_0^2 - \omega^2)^2 + 4\gamma^2\omega^2}} \cos(\omega t - \phi)$$


$$\phi = \tan^{-1}\left(\frac{2\gamma\omega}{\omega_0^2 - \omega^2}\right)$$

$$\frac{d^2x}{dt^2} + 2\gamma \frac{dx}{dt} + \omega_0^2 x = A_0 \sin \omega t$$

$$x = \frac{A_0}{\sqrt{(\omega_0^2 - \omega^2)^2 + 4\gamma^2\omega^2}} \sin(\omega t - \phi)$$

$$\phi = \tan^{-1}\left(\frac{2\gamma\omega}{\omega_0^2 - \omega^2}\right)$$

Steady state solution to the LCR circuit

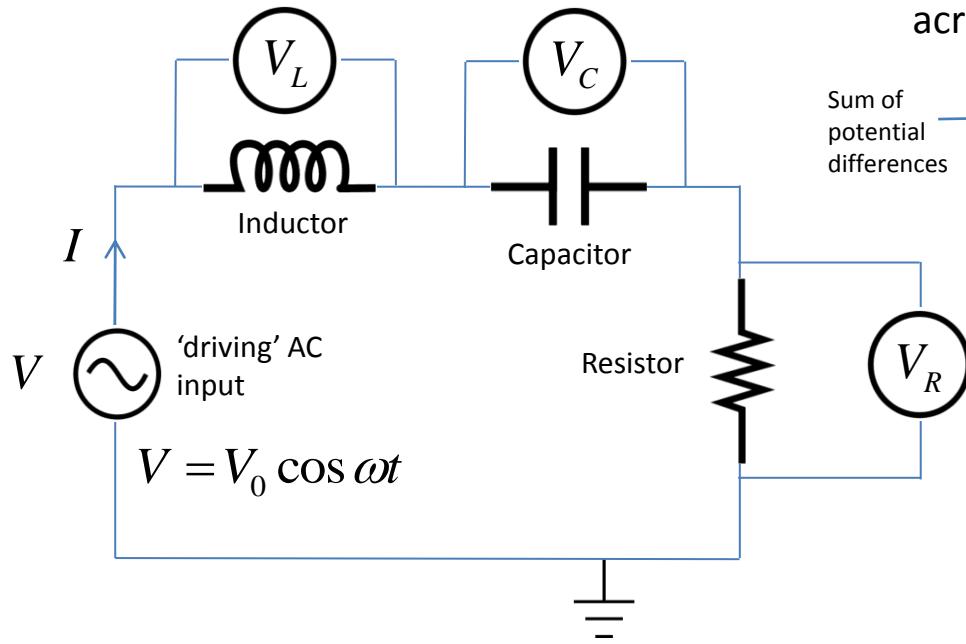

Let current I flow through the circuit. The net EMF $V - V_L$ must equal the sum of the potential drops across each electrical component.

$$\text{Sum of potential differences} \rightarrow V_R + V_C = V - V_L \quad \text{EMF - 'back EMF' due to induction in the coil}$$

$$V_R = IR$$

$$V_C = \frac{1}{C} \int Idt \quad Q = CV$$

$$V_L = L \frac{dI}{dt} \quad I = \frac{dQ}{dt} \therefore CV = \int Idt$$

$$IR + \frac{1}{C} \int Idt = V_0 \cos \omega t - L \frac{dI}{dt}$$

$$R \frac{dI}{dt} + \frac{I}{C} + L \frac{d^2I}{dt^2} = -\omega V_0 \sin \omega t$$

$$\frac{d^2I}{dt^2} + \frac{R}{L} \frac{dI}{dt} + \frac{1}{LC} I = \frac{-\omega V_0}{L} \sin \omega t$$

Steady state solution to SHM equation

$$\frac{d^2x}{dt^2} + 2\gamma \frac{dx}{dt} + \omega_0^2 x = A_0 \sin \omega t$$


$$x = \frac{A_0}{\sqrt{(\omega_0^2 - \omega^2)^2 + 4\gamma^2 \omega^2}} \sin(\omega t - \phi)$$

$$\phi = \tan^{-1} \left(\frac{2\gamma\omega}{\omega_0^2 - \omega^2} \right)$$



$$\gamma = \frac{R}{2L}, \quad \omega_0^2 = \frac{1}{LC}, \quad A_0 = \frac{-\omega V_0}{L}$$

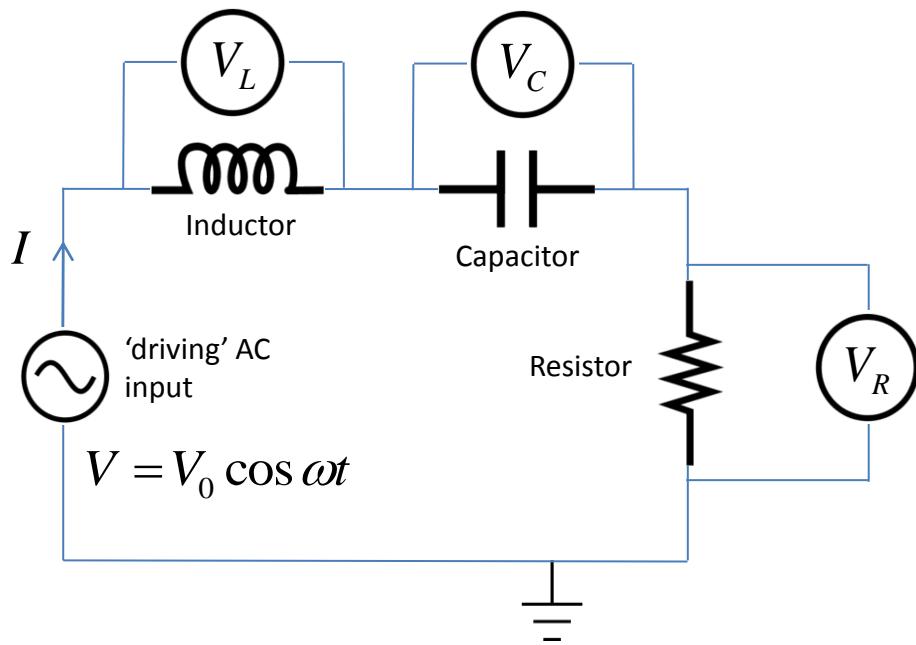Steady state solution to the LCR circuit cont



$$\frac{d^2I}{dt^2} + \frac{R}{L} \frac{dI}{dt} + \frac{I}{LC} = -\frac{\omega V_0}{L} \sin \omega t$$

$$\gamma = \frac{R}{2L}, \quad \omega_0^2 = \frac{1}{LC}, \quad A_0 = \frac{-\omega V_0}{L}$$

$$I = \frac{-\omega V_0 / L}{\sqrt{\left(\frac{1}{LC} - \omega^2\right)^2 + \left(\frac{RC}{LC}\right)^2}} \sin(\omega t - \phi)$$

$$\phi = \tan^{-1}\left(\frac{RC\omega}{1 - LC\omega^2}\right)$$

Steady state solution to SHM equation

$$\frac{d^2x}{dt^2} + 2\gamma \frac{dx}{dt} + \omega_0^2 x = A_0 \sin \omega t$$

$$x = \frac{A_0}{\sqrt{(\omega_0^2 - \omega^2)^2 + 4\gamma^2\omega^2}} \sin(\omega t - \phi)$$

$$\phi = \tan^{-1}\left(\frac{2\gamma\omega}{\omega_0^2 - \omega^2}\right)$$

$$I_{\max} \text{ when } \omega = \sqrt{\omega_0^2 - 2\gamma^2}$$

$$f_{\max} = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \left(\frac{RC}{LC}\right)^2}$$

$$f_{\max} = f_0 \sqrt{1 - \frac{(RC)^2}{LC}}$$

$$f_{\max} = f_0 \sqrt{1 - 4\pi^2 (f_0\tau)^2}$$

$$\omega = 2\pi f$$

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$$

$$\tau = RC$$

$$LC = \frac{1}{4\pi^2 f_0^2}$$

$$4\pi^2 (f_0\tau)^2 < 1$$

$$f_0\tau < \frac{1}{2\pi}$$

Using dimensionless variables ...

$$\frac{d^2I}{dt^2} + \frac{R}{L} \frac{dI}{dt} + \frac{I}{LC} = \frac{-\omega V_0}{L} \sin \omega t$$

$$\gamma = \frac{R}{2L}, \quad \omega_0^2 = \frac{1}{LC}, \quad A_0 = \frac{-\omega V_0}{L}$$

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$$

$$z = \frac{f}{f_0}$$

$$I_0 = \frac{-\omega V_0}{L\omega_0^2} = -\frac{2\pi f V_0 LC}{L} = -2\pi f C V_0 = -2\pi z f_0 C V_0$$

$$k = \frac{R}{L\omega_0} = \frac{R\sqrt{LC}}{L} = R\sqrt{\frac{C}{L}} = RC\sqrt{\frac{1}{LC}} = 2\pi f_0 RC$$

$$I = \frac{-2\pi z f_0 C V_0}{\sqrt{(1-z^2)^2 + k^2 z^2}} \sin(\omega t - \phi)$$

$$\phi = \tan^{-1}\left(\frac{kz}{1-z^2}\right)$$



$$\frac{d^2x}{dt^2} + 2\gamma \frac{dx}{dt} + \omega_0^2 x = A_0 \sin \omega t$$

$$x_0 = \frac{A_0}{\omega_0^2} \quad z = \frac{\omega}{\omega_0} \quad k = \frac{2\gamma}{\omega_0}$$


$$x = \frac{x_0}{\sqrt{(1-z^2)^2 + k^2 z^2}} \sin(\omega t - \phi)$$

$$\phi = \tan^{-1}\left(\frac{kz}{1-z^2}\right)$$

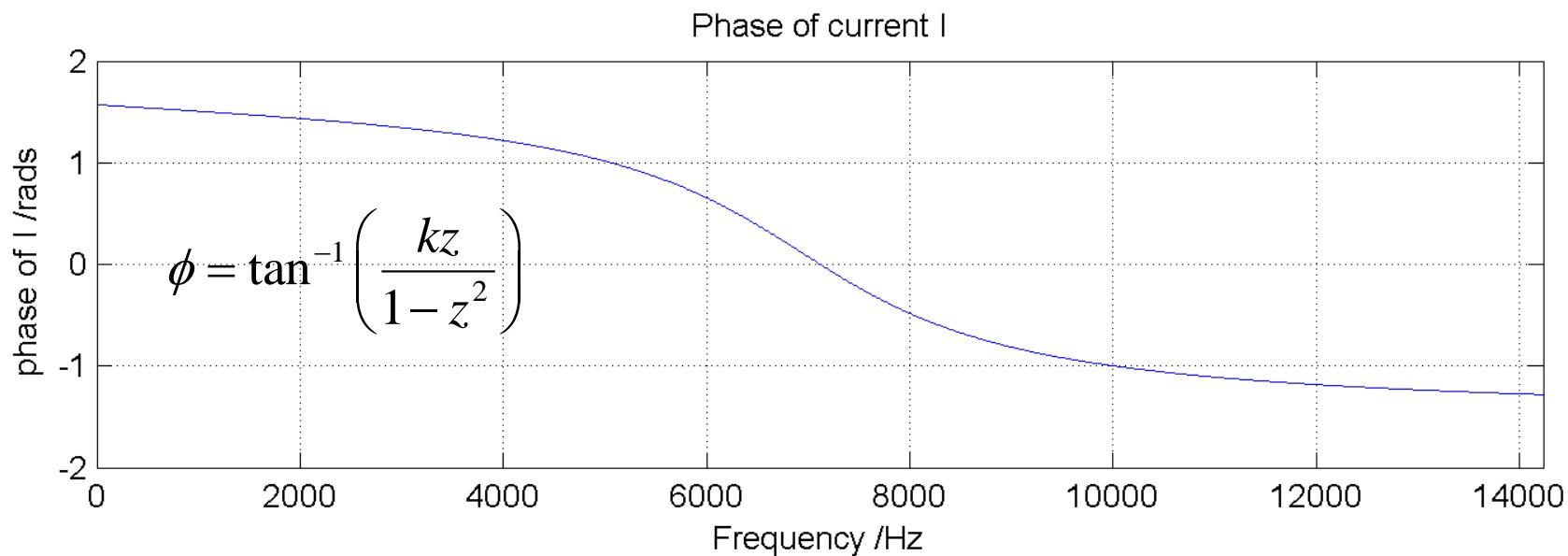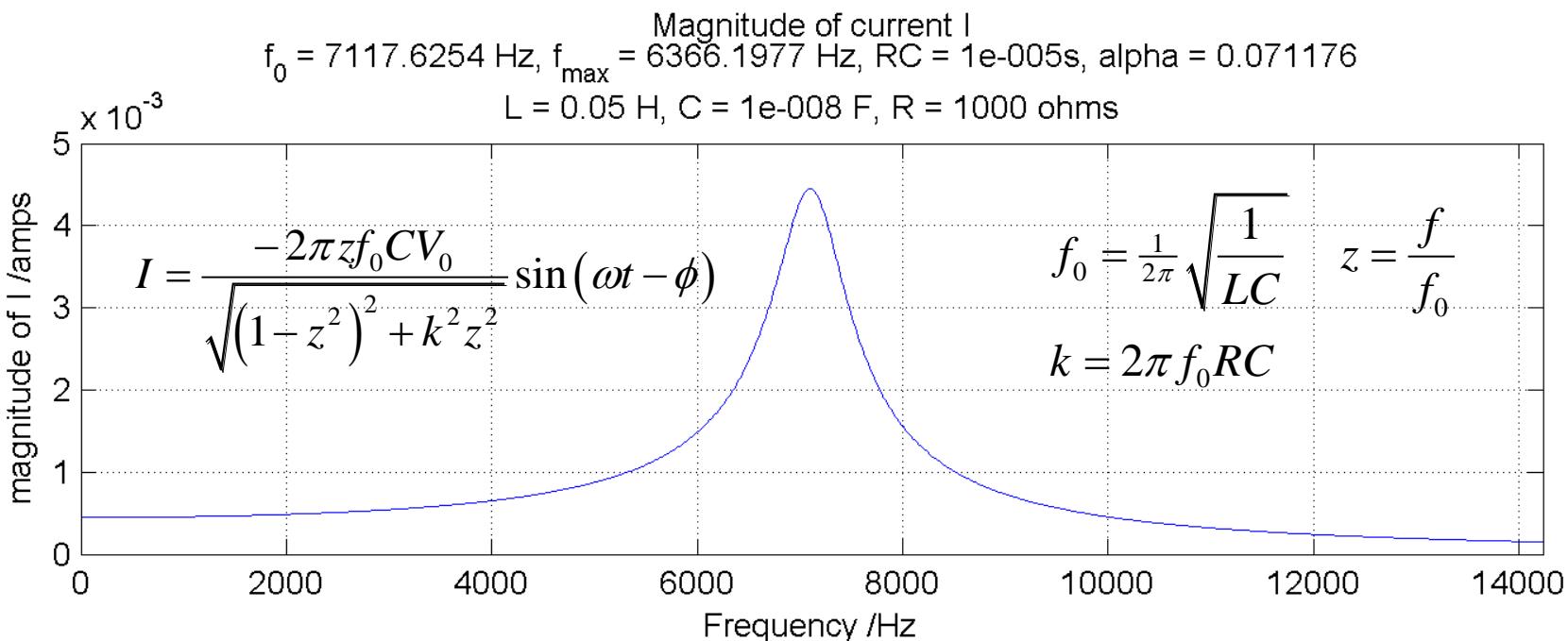Note $f_0 C V_0$
is the average current
when the maximum amount
of charge stored in the capacitor
is discharged over one complete
period at frequency f_0



Complex impedance

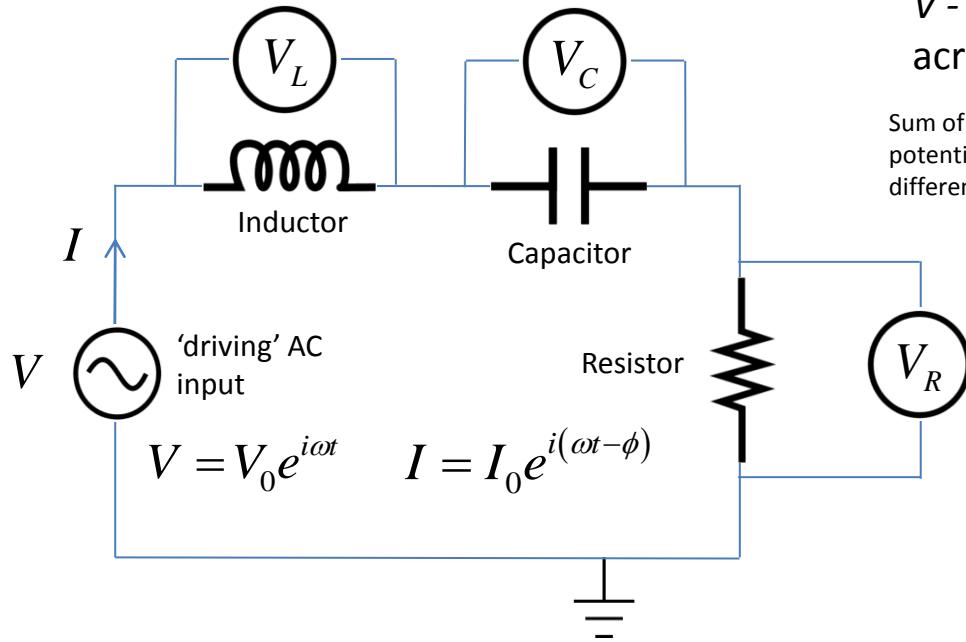

$$IR + \frac{1}{C} \int Idt + L \frac{dI}{dt} = V_0 e^{i\omega t}$$

$$I_0 e^{i(\omega t - \phi)} \left(R + \frac{1}{i\omega C} + i\omega L \right) = V_0 e^{i\omega t}$$

$$Z = R + \frac{1}{i\omega C} + i\omega L$$

$$\therefore V = I |Z| e^{i\arg(Z)}$$

$$\phi = \arg(Z)$$

$\therefore V = IZ$

Ohm's Law,
generalized for AC

Let current I flow through the circuit. The net EMF $V - V_L$ must equal the sum of the potential drops across each electrical component.

Sum of potential differences $\rightarrow V_R + V_C = V - V_L$ ← EMF – 'back EMF' due to induction in the coil

$$V_R = IR$$

$$V_C = \frac{1}{C} \int Idt \quad Q = CV$$


$$V_L = L \frac{dI}{dt}$$


$$IR + \frac{1}{C} \int Idt = V_0 e^{i\omega t} - L \frac{dI}{dt}$$

$$Z = Z_L + Z_C + Z_R$$

$$Z_L = i\omega L$$

$$Z_C = \frac{1}{i\omega C}$$

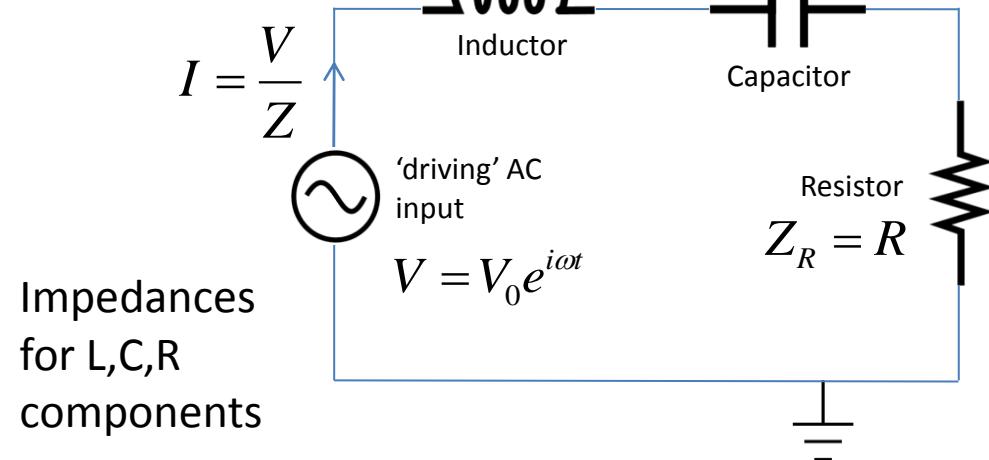

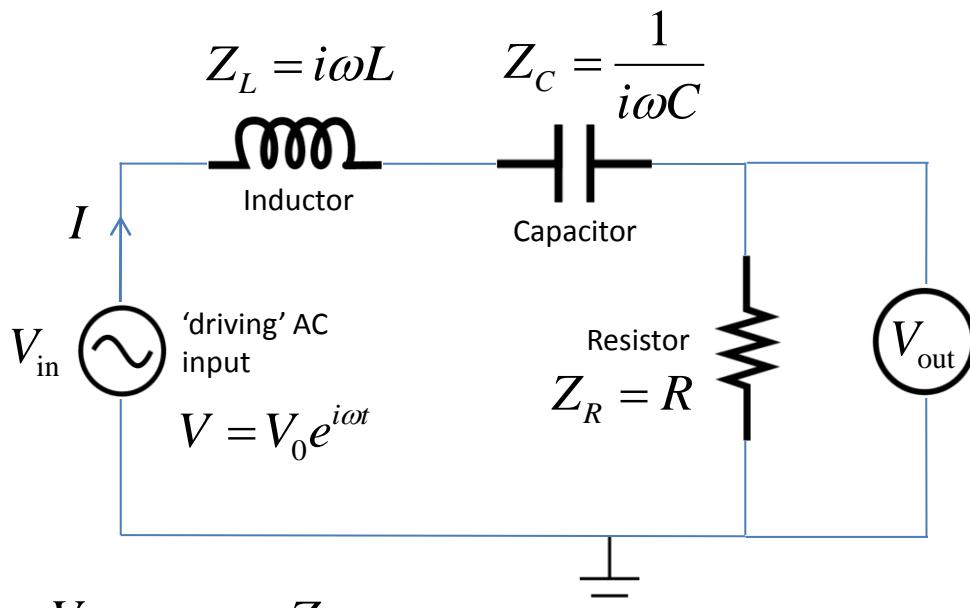

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{Z_R}{Z_L + Z_C + Z_R}$$

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{R}{R + i\left(\omega L - \frac{1}{\omega C}\right)}$$

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{RC\omega}{RC\omega + i(\omega^2 LC - 1)}$$

$$x = \frac{f}{f_0} \quad f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$$



$$\tau = RC \quad \alpha = f_0 \tau$$


$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{2\pi f \tau}{2\pi f \tau + i\left(\frac{4\pi^2 f^2}{4\pi^2 f_0^2} - 1\right)}$$

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{2\pi x f_0 \tau}{2\pi x f_0 \tau + i(x^2 - 1)}$$

$$\boxed{\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{2\pi x \alpha}{2\pi x \alpha + i(x^2 - 1)}}$$

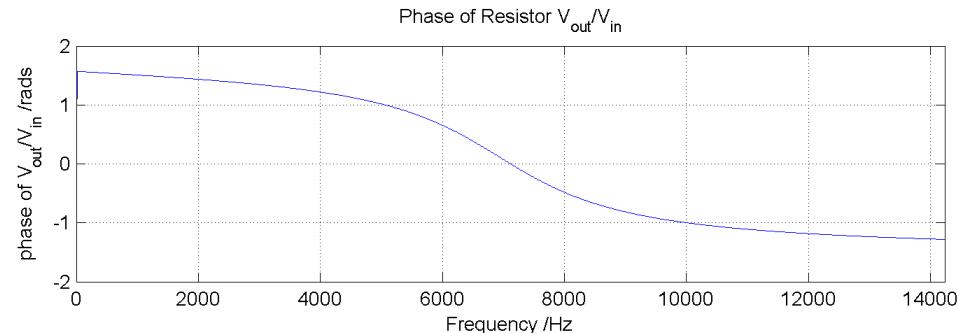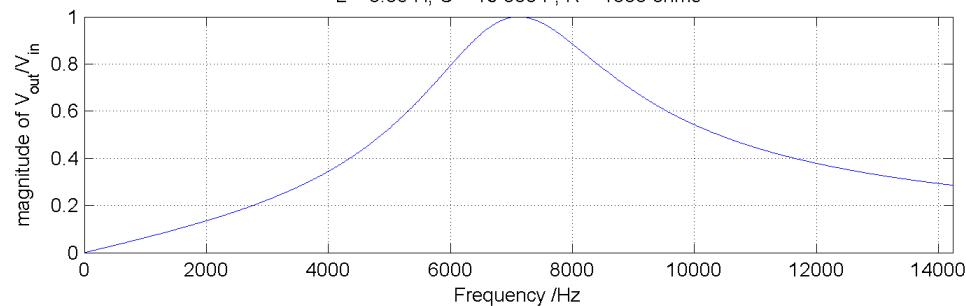Magnitude of Resistor $V_{\text{out}}/V_{\text{in}}$
 $f_0 = 7117.6254$ Hz, $f_{\text{max}} = 6366.1977$ Hz, $RC = 1e-005$ s, $\alpha = 0.071176$
 $L = 0.05$ H, $C = 1e-008$ F, $R = 1000$ ohms



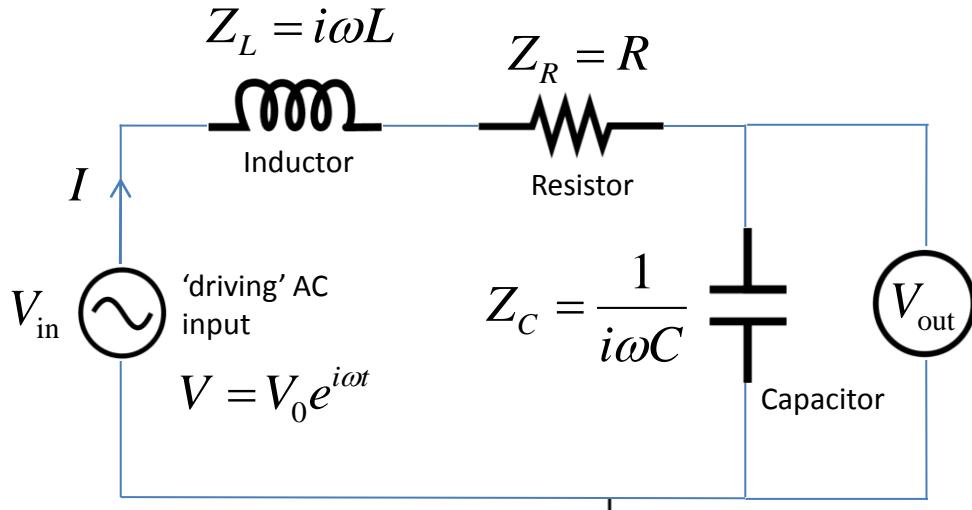

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{Z_C}{Z_L + Z_C + Z_R}$$

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{\frac{1}{i\omega C}}{R + i\left(\omega L - \frac{1}{\omega C}\right)}$$

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{1}{iRC\omega - (\omega^2 LC - 1)}$$

$$x = \frac{f}{f_0} \quad f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$$



$$\tau = RC \quad \alpha = f_0\tau$$


$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{1}{2\pi f\tau + i\left(\frac{4\pi^2 f^2}{4\pi^2 f_0^2} - 1\right)}$$

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{1}{2\pi xf_0\tau + i(x^2 - 1)}$$

$$\boxed{\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{1}{2\pi x\alpha + i(x^2 - 1)}}$$

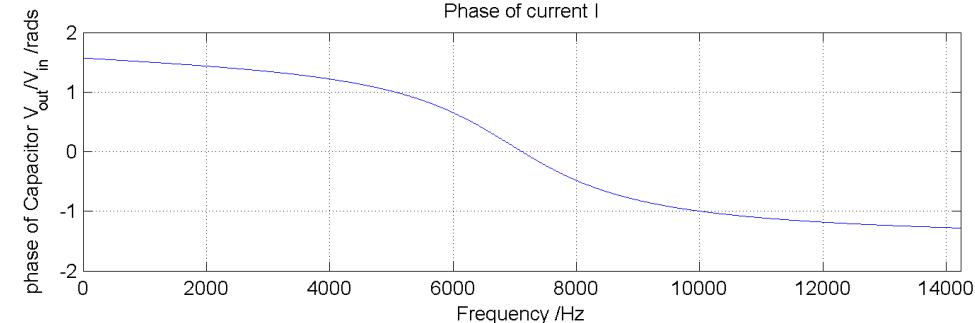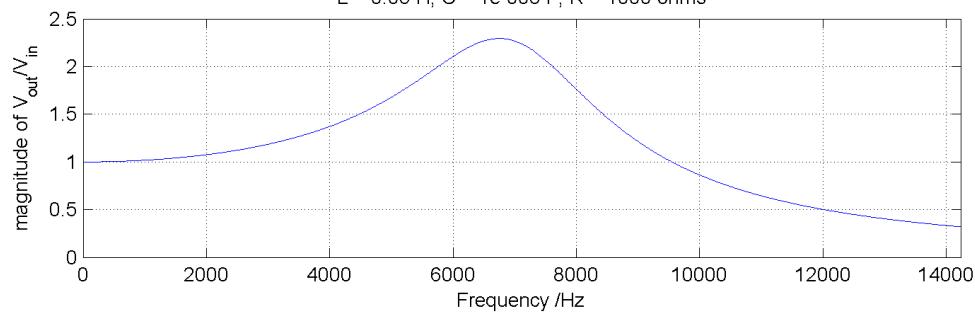Magnitude of Capacitor $V_{\text{out}}/V_{\text{in}}$
 $f_0 = 7117.6254$ Hz, $f_{\text{max}} = 6366.1977$ Hz, $RC = 1e-005$ s, $\alpha = 0.071176$
 $L = 0.05$ H, $C = 1e-008$ F, $R = 1000$ ohms



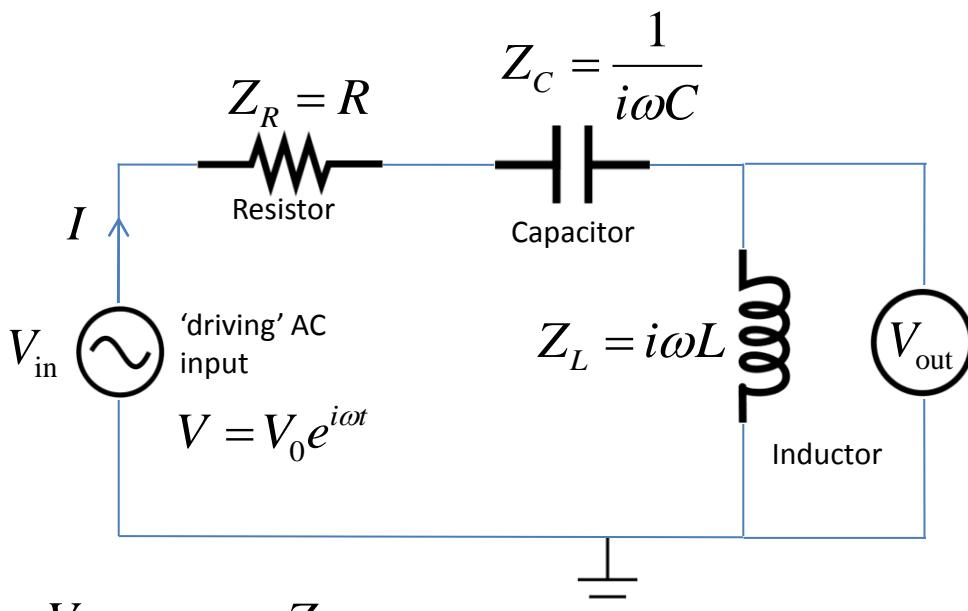

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{Z_L}{Z_L + Z_C + Z_R}$$

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{i\omega L}{R + i\left(\omega L - \frac{1}{\omega C}\right)}$$

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{i\omega^2 LC}{RC\omega + i(\omega^2 LC - 1)}$$



$$x = \frac{f}{f_0} \quad f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$$

$$\tau = RC \quad \alpha = f_0 \tau$$



$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{i \frac{4\pi^2 f^2}{4\pi^2 f_0^2}}{2\pi f \tau + i \left(\frac{4\pi^2 f^2}{4\pi^2 f_0^2} - 1 \right)}$$

$$\boxed{\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{ix}{2\pi\alpha x + i(x^2 - 1)}}$$

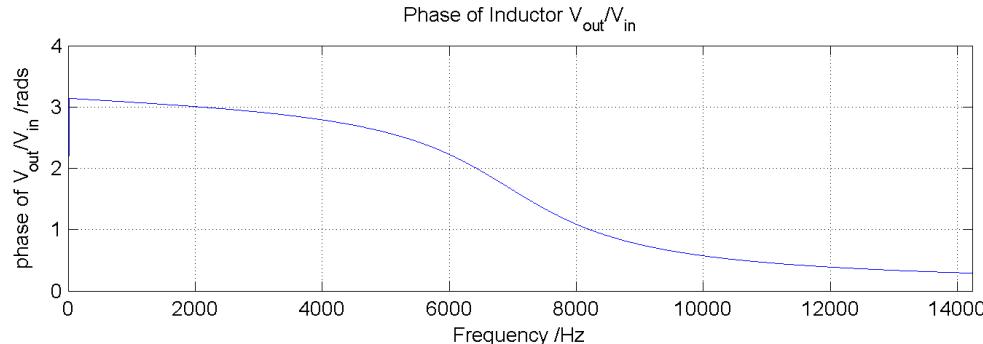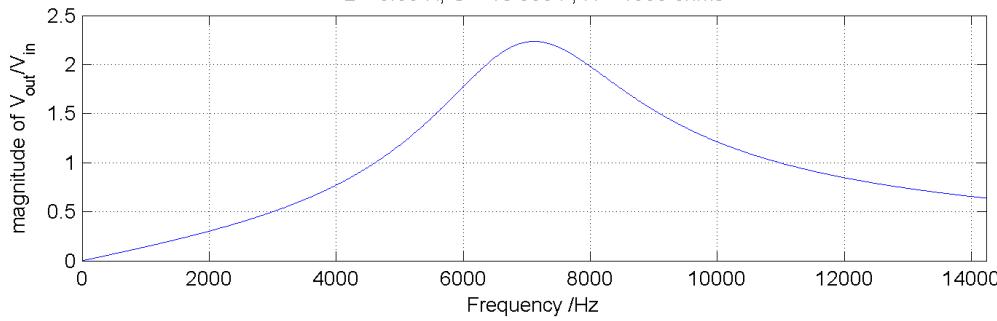
Magnitude of Inductor $V_{\text{out}}/V_{\text{in}}$
 $f_0 = 7117.6254$ Hz, $f_{\text{max}} = 6366.1977$ Hz, $RC = 1e-005$ s, $\alpha = 0.071176$
 $L = 0.05$ H, $C = 1e-008$ F, $R = 1000$ ohms



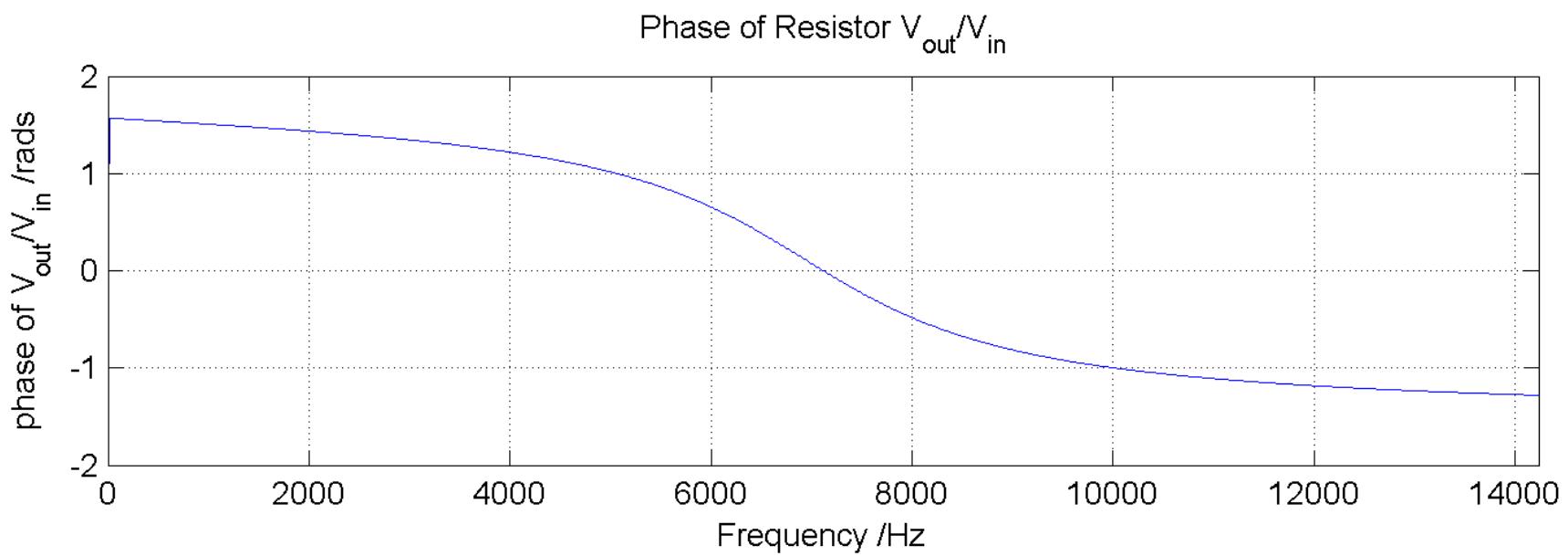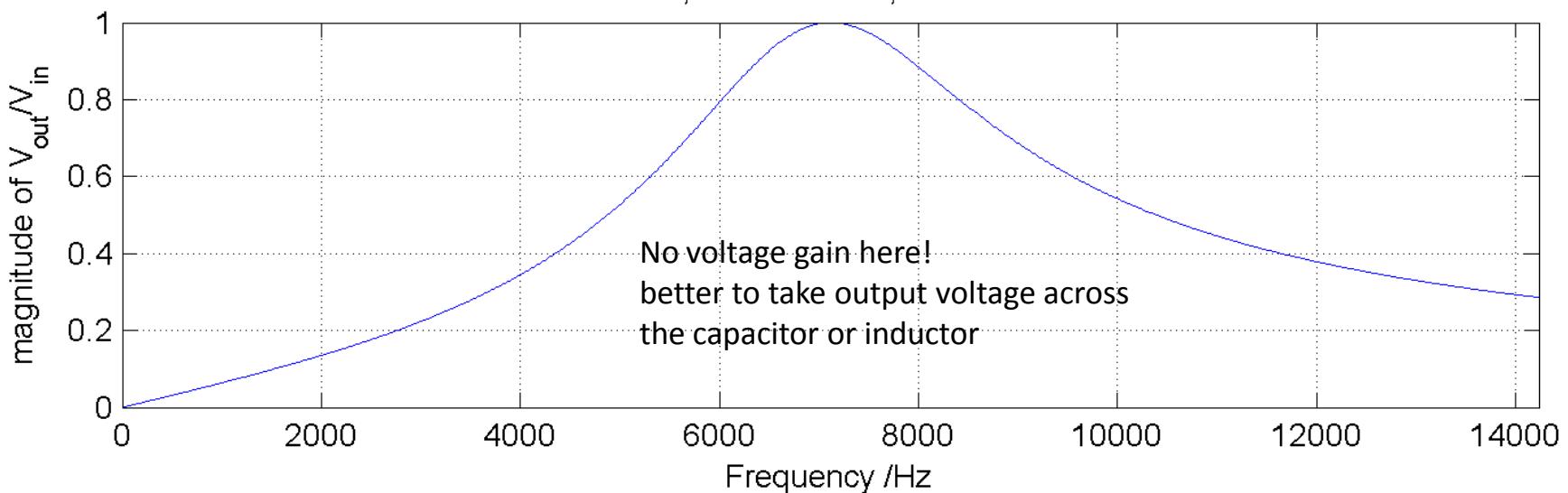
Magnitude of Resistor $V_{\text{out}}/V_{\text{in}}$
 $f_0 = 7117.6254 \text{ Hz}$, $f_{\text{max}} = 6366.1977 \text{ Hz}$, $RC = 1e-005 \text{ s}$, $\alpha = 0.071176$
 $L = 0.05 \text{ H}$, $C = 1e-008 \text{ F}$, $R = 1000 \text{ ohms}$



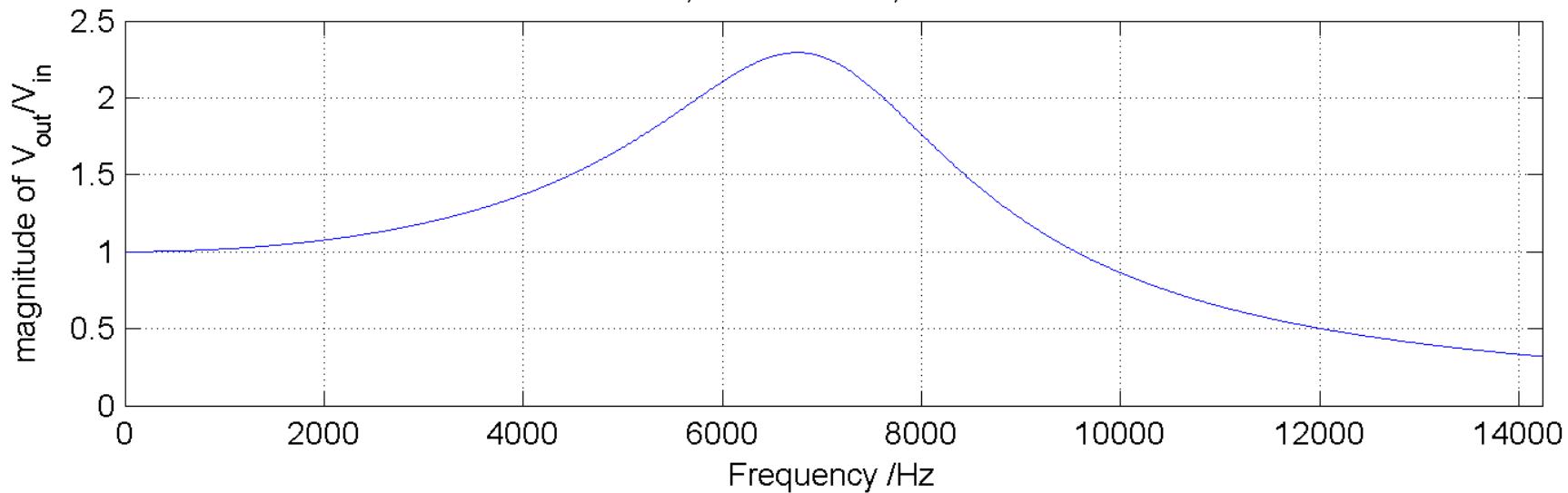Magnitude of Capacitor $V_{\text{out}}/V_{\text{in}}$
 $f_0 = 7117.6254 \text{ Hz}$, $f_{\text{max}} = 6366.1977 \text{ Hz}$, $RC = 1e-005 \text{ s}$, $\alpha = 0.071176$
 $L = 0.05 \text{ H}$, $C = 1e-008 \text{ F}$, $R = 1000 \text{ ohms}$




Phase of current I

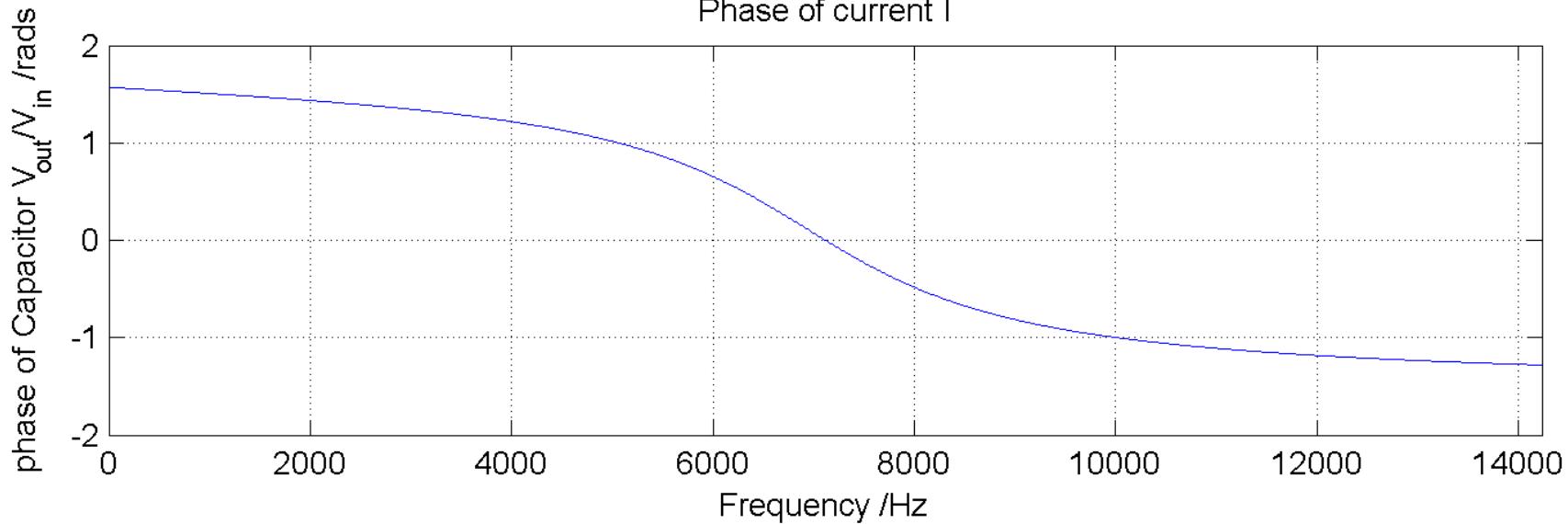


Magnitude of Inductor $V_{\text{out}}/V_{\text{in}}$

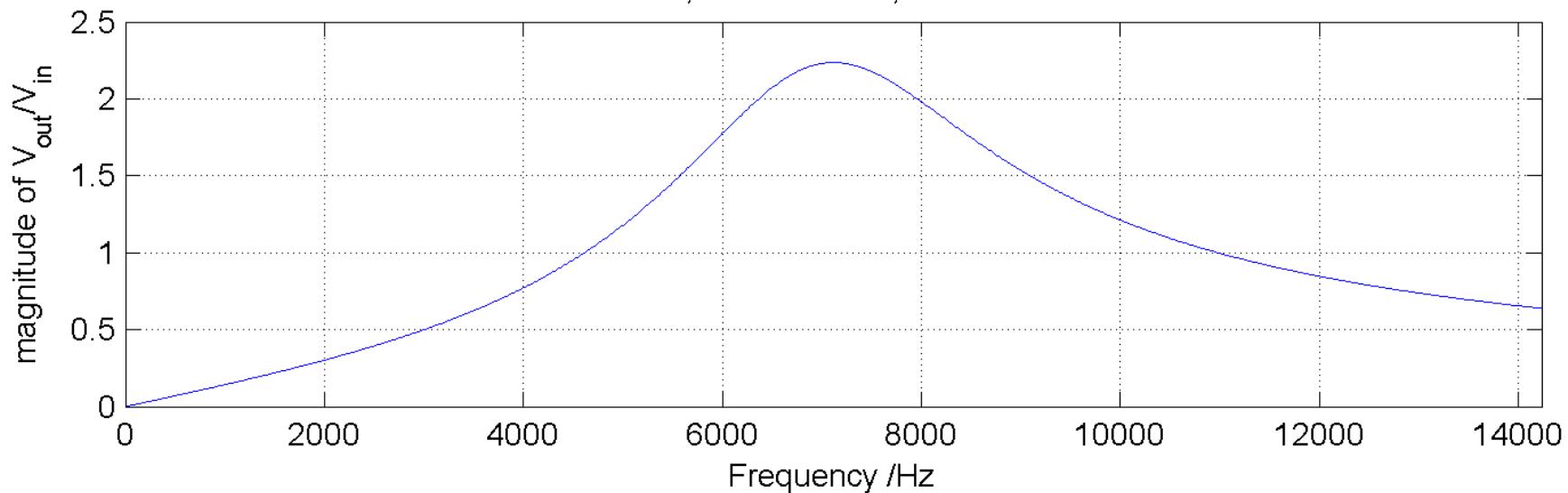$f_0 = 7117.6254 \text{ Hz}$, $f_{\text{max}} = 6366.1977 \text{ Hz}$, $RC = 1e-005 \text{ s}$, $\alpha = 0.071176$
 $L = 0.05 \text{ H}$, $C = 1e-008 \text{ F}$, $R = 1000 \text{ ohms}$





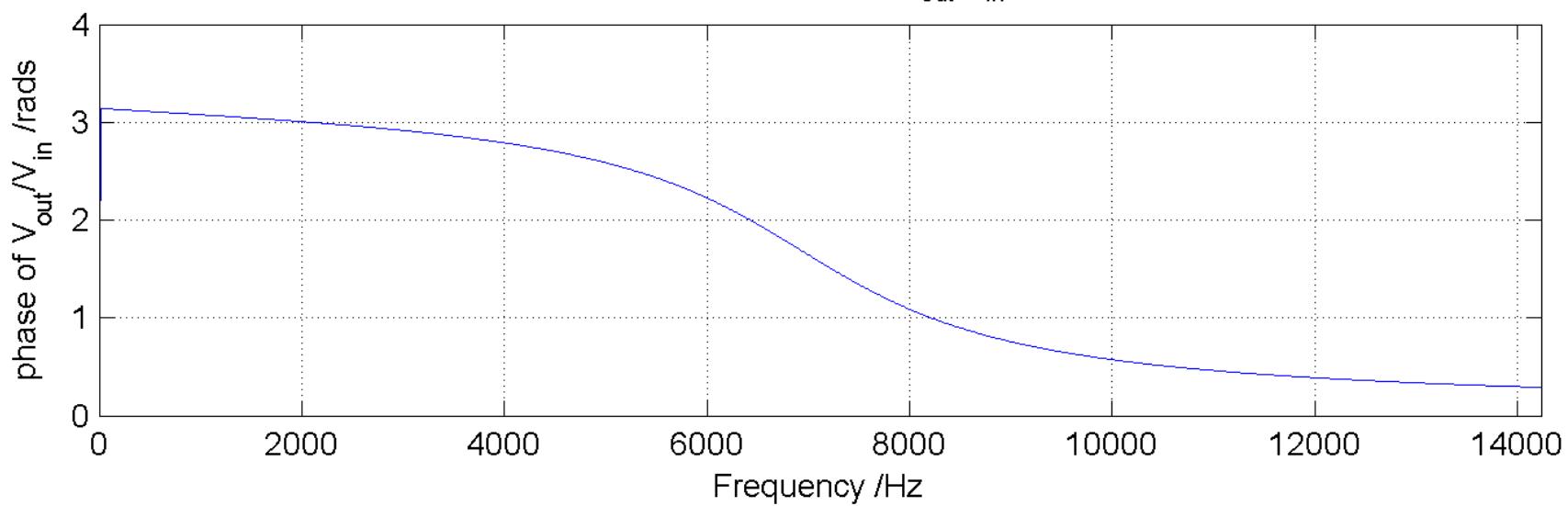Phase of Inductor $V_{\text{out}}/V_{\text{in}}$



LCR circuits can be used as **electrical filters**. If a signal consists of a superposition of oscillations at different frequencies, an LCR circuit can be tuned to preferentially boost signal components whose frequencies are near the resonance peak of the circuit.

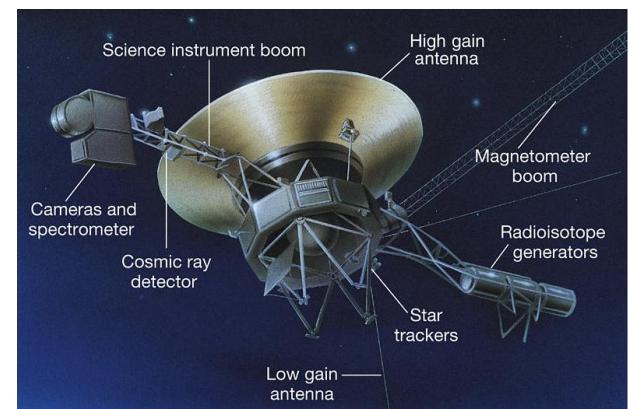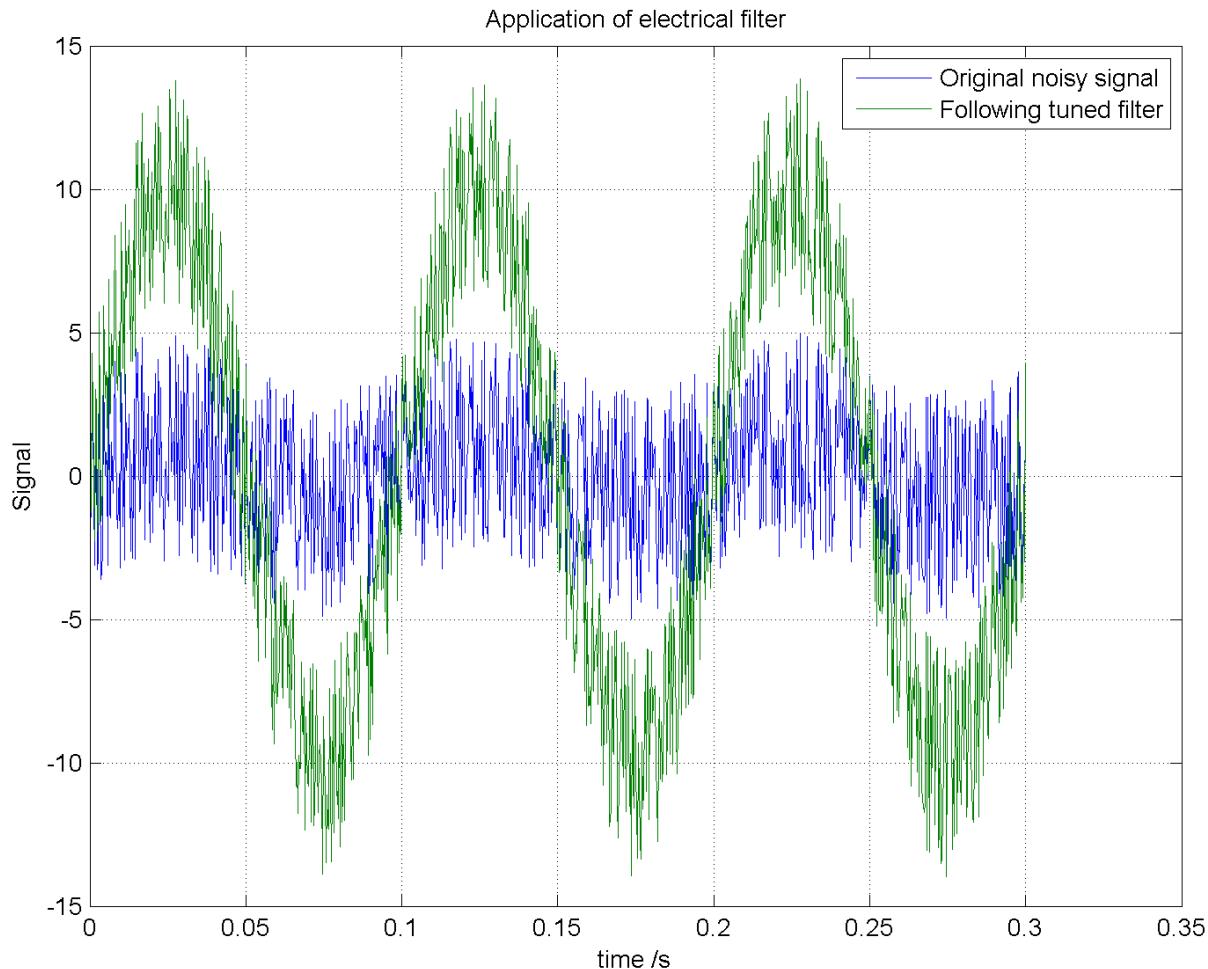This has *enormous* application in communications or Radar technology, whereby a weak signal of a known frequency (e.g. a local radio station, or indeed the broadcasts from Voyager!) may be buried in electrical noise ‘across the waveband’.



Designing a mains noise filter


In many applications we would like to filter out electrical signals associated with mains AC at 50Hz

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$$

$$\therefore LC = \frac{1}{4\pi^2 f_0^2}$$

If $L = 0.05$, therefore $C = 2.03 \times 10^{-4}$ F

'Knotch filter'

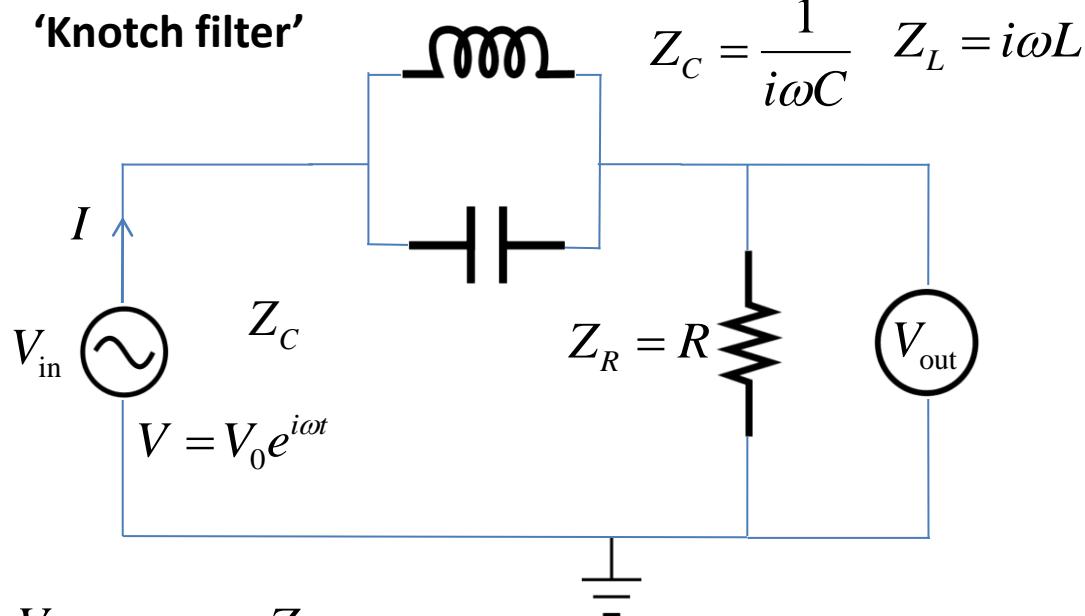

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{Z_R}{\frac{1}{Z_C} + Z_R}$$

$$\frac{1}{Z_C} + \frac{1}{Z_L}$$

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{R}{\frac{1}{i\omega C} + R}$$

$$i\omega C + \frac{1}{i\omega L}$$


$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{1}{i\omega RC - i\frac{RC}{\omega LC} + 1}$$

$$Z_C = \frac{1}{i\omega C} \quad Z_L = i\omega L$$

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{i\omega RC - i\frac{RC}{\omega LC}}{1 + i\omega RC - i\frac{RC}{\omega LC}}$$

$$\boxed{\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{i2\pi\alpha\left(x - \frac{1}{x}\right)}{1 + i2\pi\alpha\left(x - \frac{1}{x}\right)}}$$

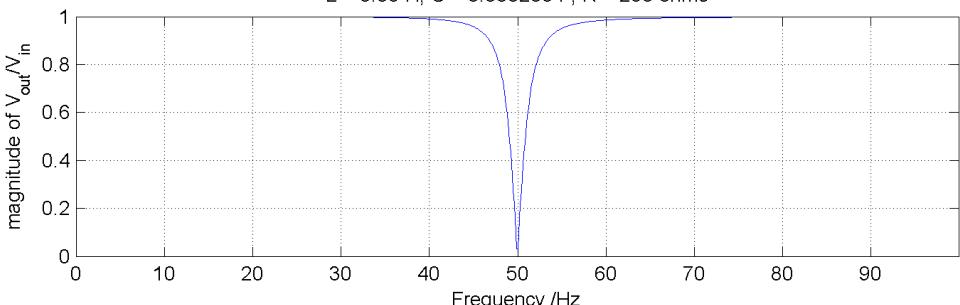Magnitude of Resistor $V_{\text{out}}/V_{\text{in}}$
 $f_0 = 49.9559 \text{ Hz}$, $f_0 = 49.9559 \text{ Hz}$, $RC = 0.05075 \text{ s}$, $\alpha = 2.5353$
 $L = 0.05 \text{ H}$, $C = 0.000203 \text{ F}$, $R = 250 \text{ ohms}$




$$x = \frac{f}{f_0}$$



$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$$

$$\tau = RC$$


$$\alpha = f_0\tau$$

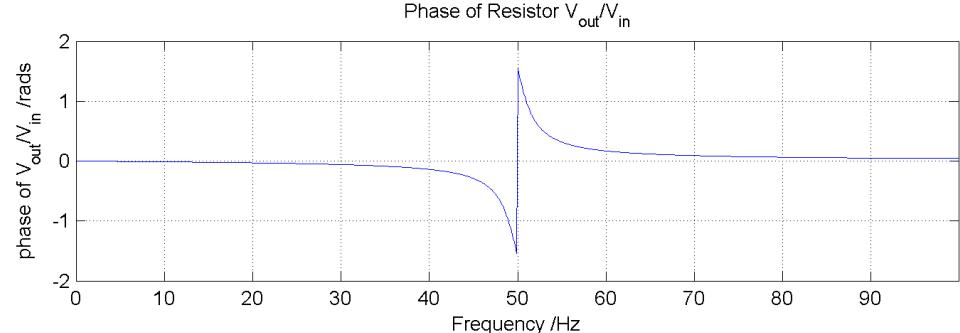

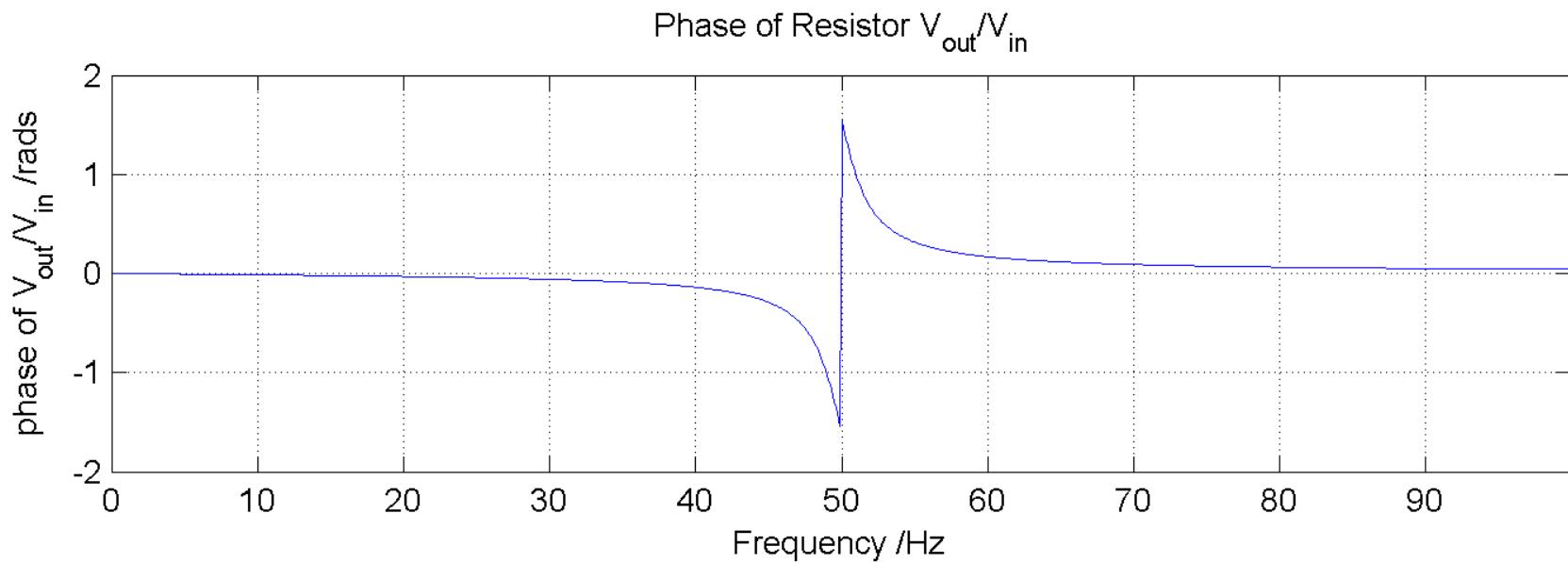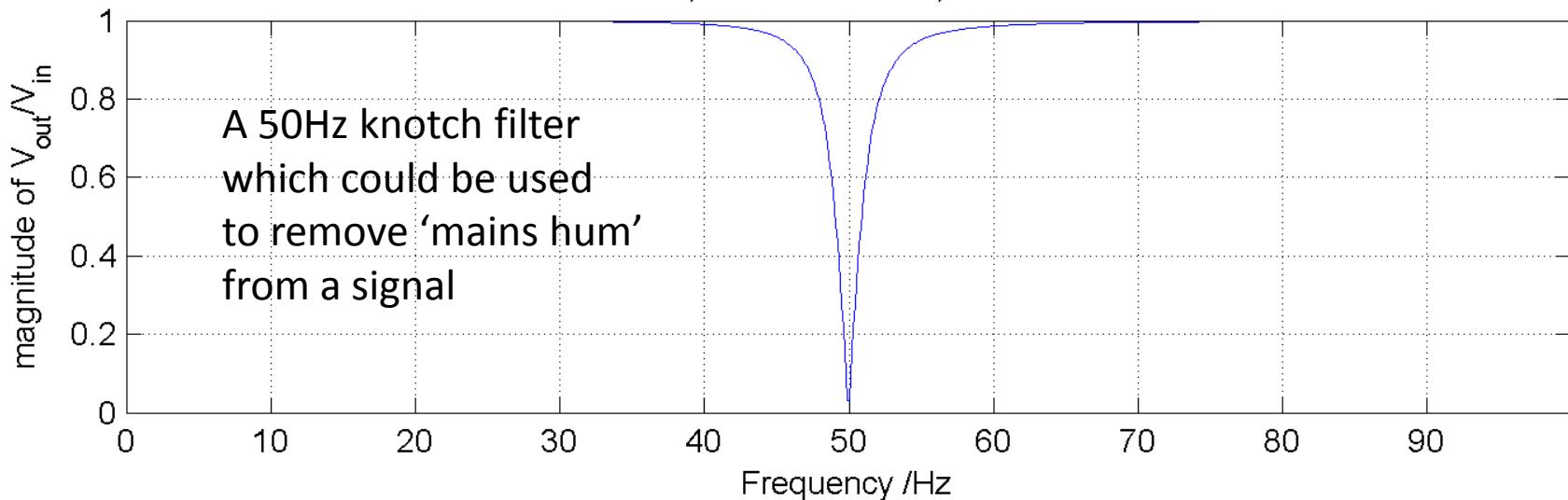
Magnitude of Resistor $V_{\text{out}}/V_{\text{in}}$
 $f_0 = 49.9559 \text{ Hz}$, $f_0 = 49.9559 \text{ Hz}$, $RC = 0.05075 \text{ s}$, $\alpha = 2.5353$
 $L = 0.05 \text{ H}$, $C = 0.000203 \text{ F}$, $R = 250 \text{ ohms}$



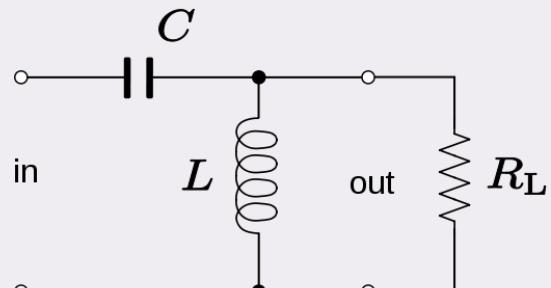
Other types of filter using just R,L,C configurations




High pass filter

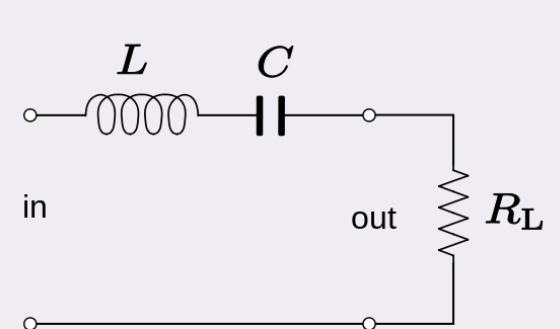


Band pass filter

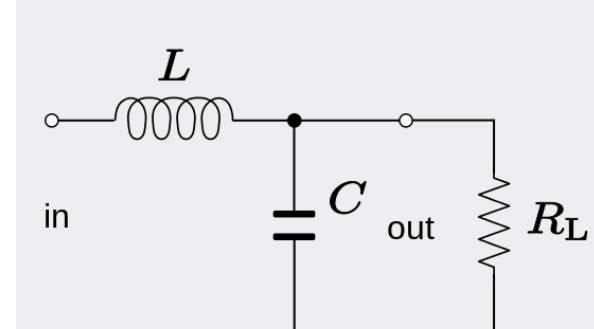


Low pass filter

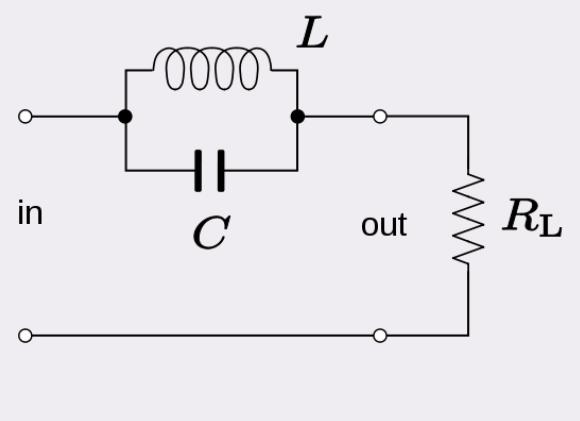

Band stop filter

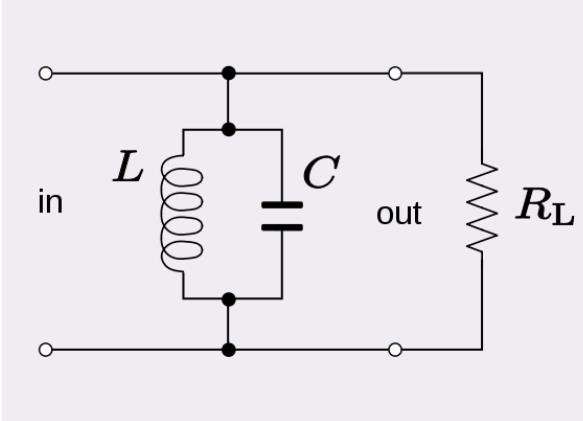


Band pass filter

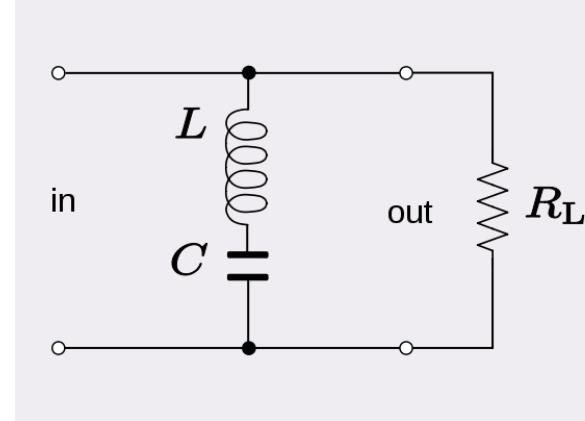

Band stop filter



More complicated L,C,R filter circuits

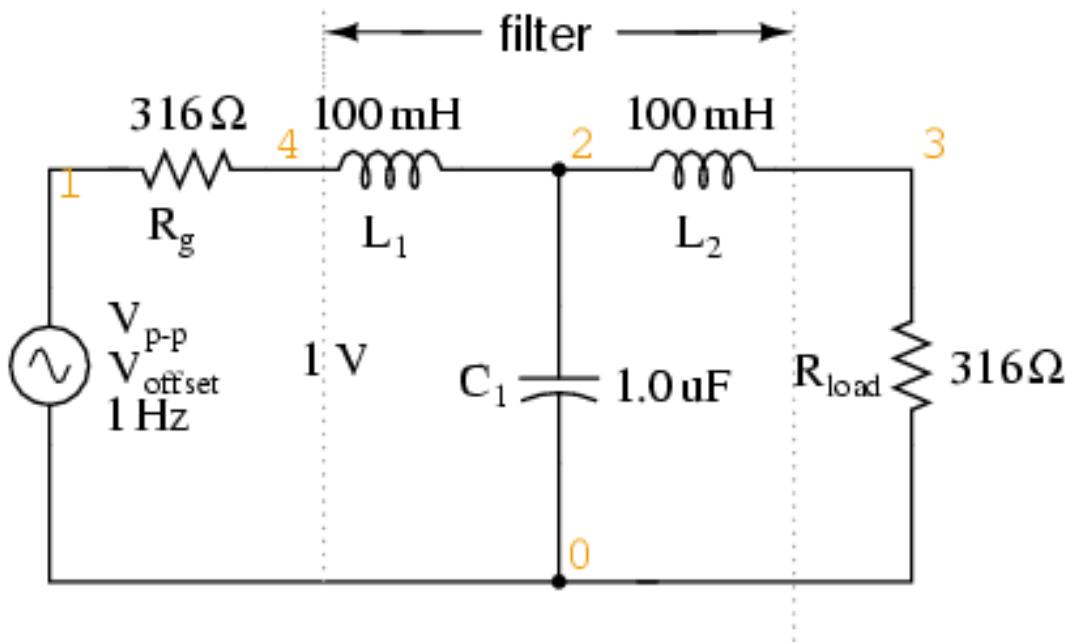

$$Z_R = R$$

$$Z_C = \frac{1}{i\omega C}$$

$$Z_L = i\omega L$$

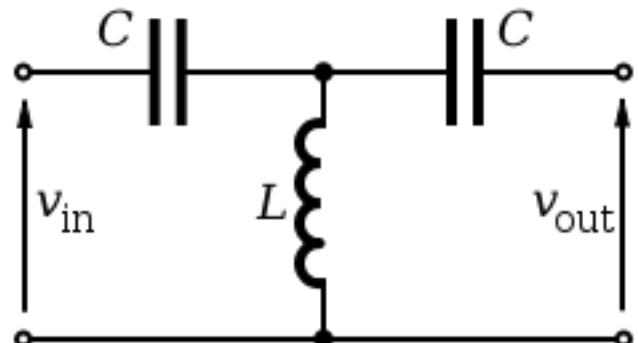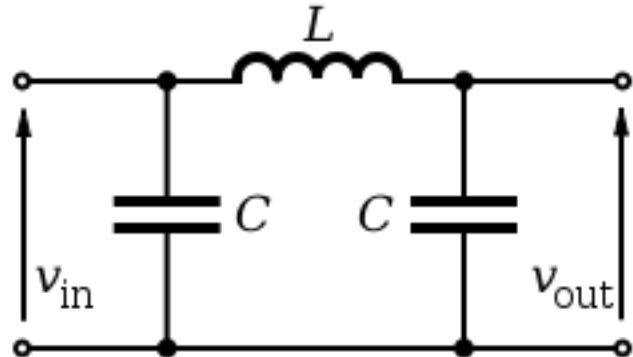

Write down equations for the currents in each loop ...
 Apply $V = IZ$...
 Solve simultaneously!


Impedance matching

Note *maximum power is transferred* from input to output if impedances

$$Z_L = Z_S^*$$

if source impedance is *fixed*. (If it is adjustable, then setting $Z_S = 0$ will maximise the power dissipated in the load).

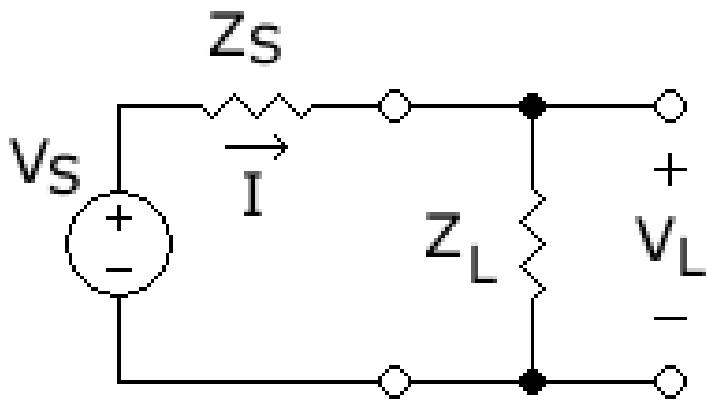A change in impedance will cause a fraction of the signal to be reflected, which results in a loss of power conveyed to the output



$$Z_L = R_L + iX_L \quad Z_S = R_S + iX_S$$

$$P_L = I_{rms} R_L = \frac{1}{2} |I|^2 R_L$$

$$V_S = I(Z_S + Z_L) \quad \therefore |V_S|^2 = |I|^2 |Z_S + Z_L|^2$$

$$|Z_S + Z_L|^2 = |R_L + iX_L + R_S + iX_S|^2$$

$$|Z_S + Z_L|^2 = |R_L + R_S + i(X_L + X_S)|^2$$

$$P_L = \frac{1}{2} \frac{|V_S|^2 R_L}{(R_S + R_L)^2 + (X_S + X_L)^2}$$

P_L is maximized when

$$R_L = R_S \quad \text{See next page!}$$

$$X_L = -X_S$$

$$\therefore R_L + iX_L = R_S - iX_S$$

$$\therefore Z_L = Z_S^*$$

Maximizing the load power in the ‘power dissipation theorem’ is equivalent to maximizing y given constant a in the equation


$$y = \frac{x}{(a+x)^2}, \quad x > 0$$

$$\frac{dy}{dx} = \frac{(a+x)^2(1) - x(2(a+x))}{(a+x)^4}$$

$$\frac{dy}{dx} = \frac{(a+x)(a+x-2x)}{(a+x)^4}$$

$$\frac{dy}{dx} = \frac{a-x}{(a+x)^3}$$

$$\therefore \left. \frac{dy}{dx} \right|_{x=a} = 0$$

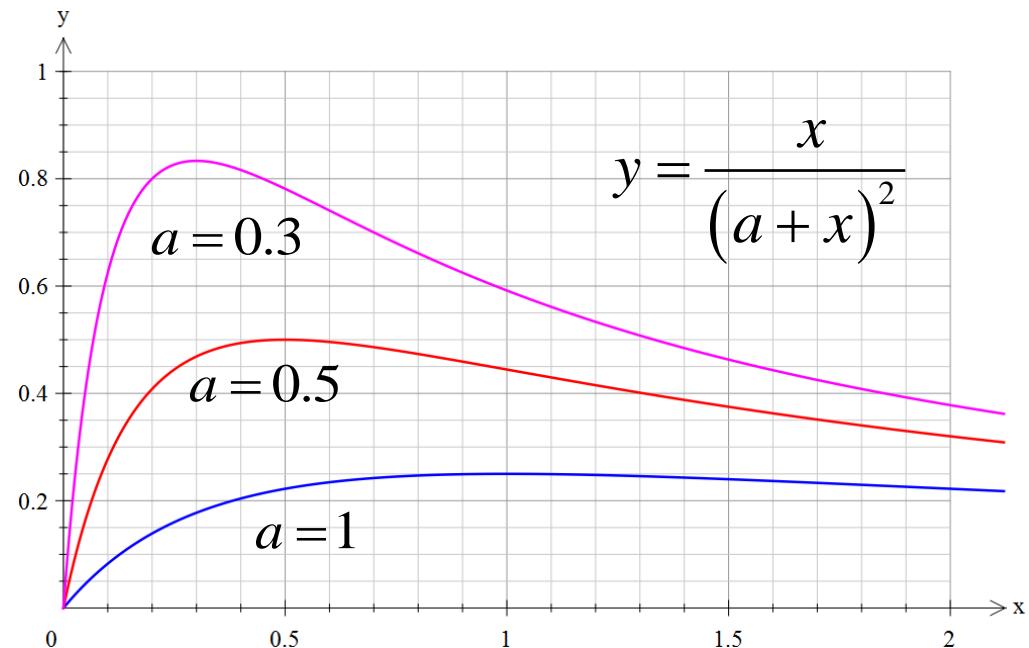

Hence maxima at

$$x = a$$

$$y = \frac{a}{(a+a)^2} = \frac{1}{4a}$$

Radiated electromagnetic waves

Maxwell developed the experimental work of Faraday and others into a mathematical theory of electric and magnetic fields.

It is a vector theory, encapsulated in four equations which are now known as Maxwell's Equations.

One can combine them to form a wave equation in both the electric and magnetic fields. In each case, the velocity of waves (in 'free space' i.e. a perfect vacuum) is


$$c = \frac{1}{\sqrt{\epsilon_0 \mu_0}}$$

i.e. the **speed of light**
 $c = 2.998 \times 10^8 \text{ ms}^{-1}$.

This is *independent* of the frame of reference! A big clue that **Albert Einstein** used to help him develop the *theory of Relativity*.



Heinrich Hertz
1857-1894

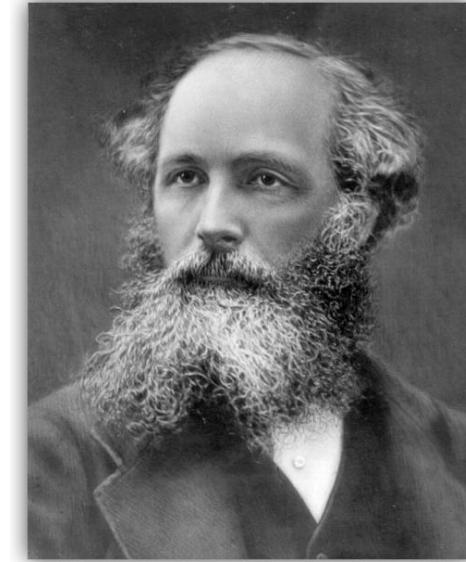

James Clerk Maxwell
1831-1879

Guglielmo Marconi
Wireless transmission pioneer
1874-1937



Permittivity & permeability

Coulomb's Law of force (F) between two charges (Q_1, Q_2) separated by distance r

$$F = \frac{1}{4\pi\epsilon_0} \frac{Q_1 Q_2}{r^2}$$

$$\epsilon_0 = 8.85418782 \times 10^{-12} \text{ kg}^{-1}\text{m}^{-3}\text{s}^4\text{A}^2$$


$$B = \mu\mu_0 \frac{NI}{l}$$

Magnetic field strength inside a *solenoid* of N turns and cross section A

$$L = \frac{\mu\mu_0 N^2 A}{l}$$

Inductance of a coil of N turns and cross section A

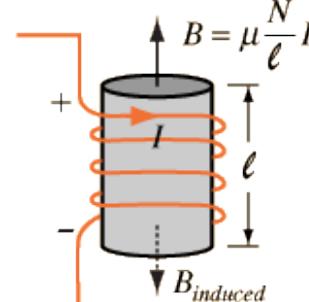
$$\mu_0 = 4\pi \times 10^{-7} \text{ kgms}^{-2}\text{A}^{-2}$$



Charles-Augustin de Coulomb
1736-1806

Joseph Henry
1797-1878



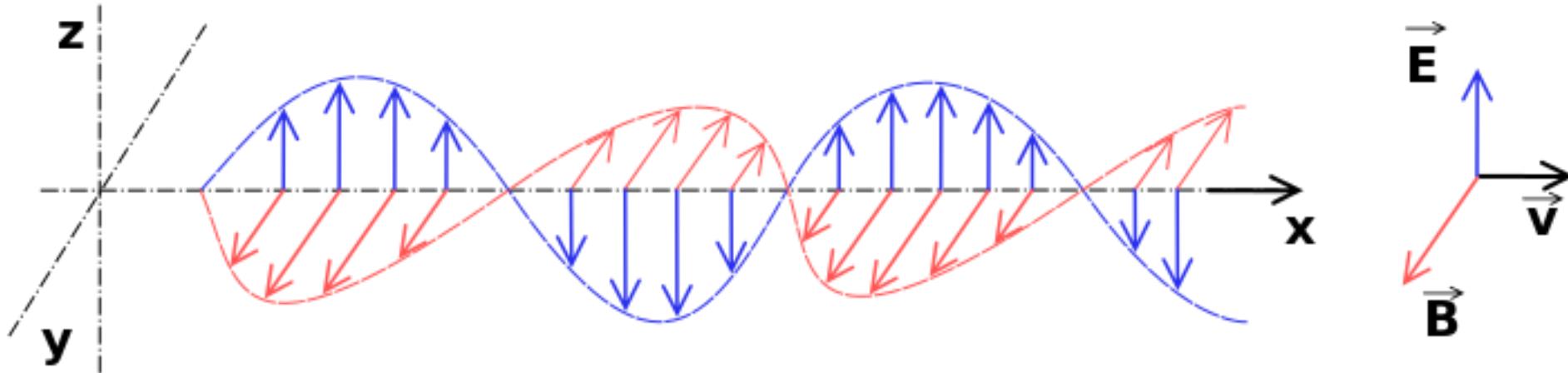

$$\nabla^2 \mathbf{E} = \frac{1}{c^2} \frac{\partial^2 \mathbf{E}}{\partial t^2}$$


$$\nabla^2 \mathbf{B} = \frac{1}{c^2} \frac{\partial^2 \mathbf{B}}{\partial t^2}$$

$$c = \frac{1}{\sqrt{\epsilon_0 \mu_0}}$$

*Wave equations for electric fields **E** and magnetic fields **B***

c = 2.998 x 10⁸ ms⁻¹ independent of any coordinate system! So no matter how fast you are moving, electromagnetic waves always propagate at the same speed

The Electromagnetic Spectrum

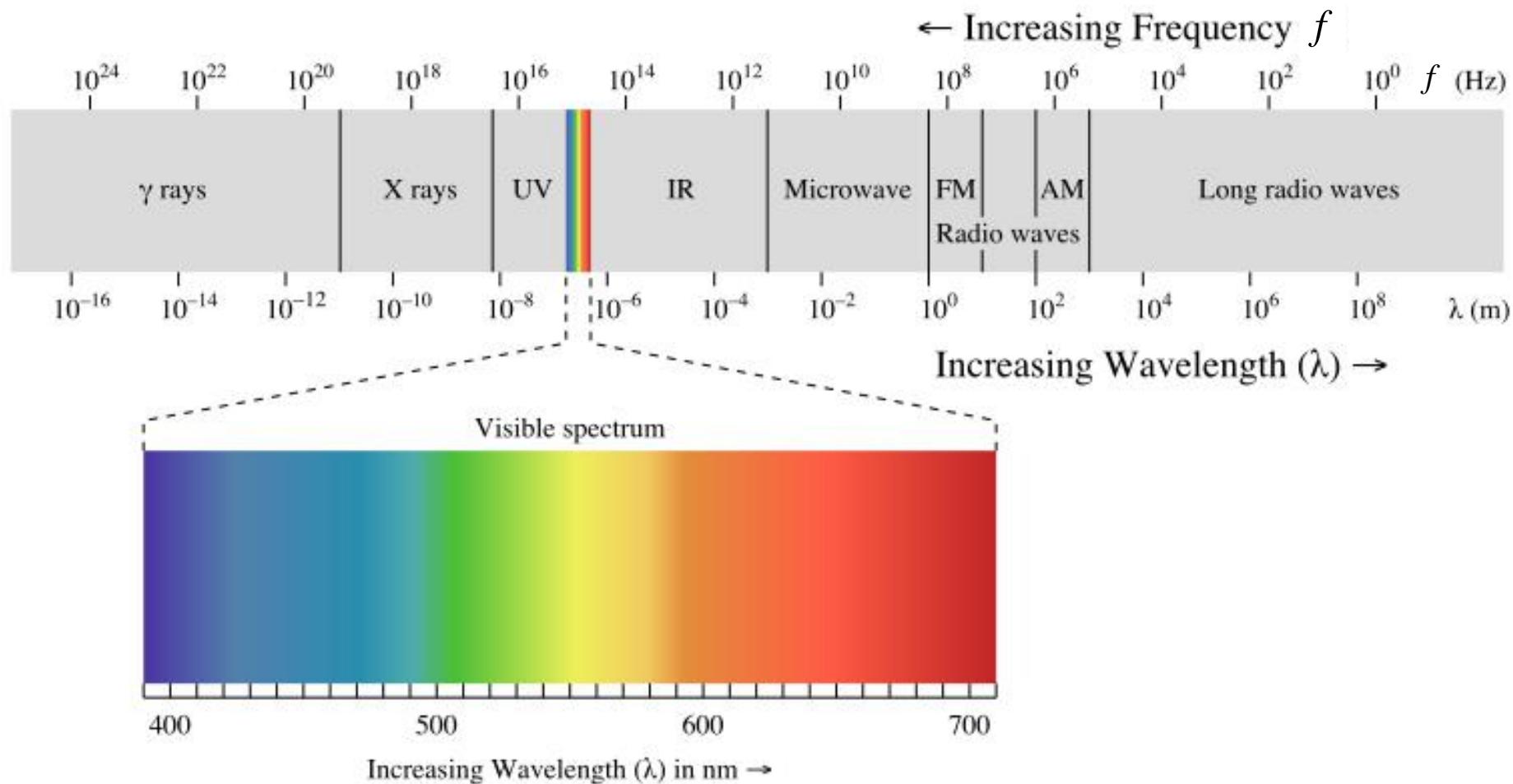

$$c = f\lambda$$

Differential form:

$$\nabla \cdot \mathbf{E} = \frac{\rho}{\epsilon_0} \quad (7.50)$$

$$\nabla \cdot \mathbf{B} = 0 \quad (7.52)$$

$$\nabla \times \mathbf{E} = -\frac{\partial \mathbf{B}}{\partial t} \quad (7.54)$$

$$\nabla \times \mathbf{B} = \mu_0 \mathbf{J} + \mu_0 \epsilon_0 \frac{\partial \mathbf{E}}{\partial t} \quad (7.56)$$

Integral form:

$$\oint_{\text{closed surface}} \mathbf{E} \cdot d\mathbf{s} = \frac{1}{\epsilon_0} \int_{\text{volume}} \rho \, d\tau \quad (7.51)$$

$$\oint_{\text{closed surface}} \mathbf{B} \cdot d\mathbf{s} = 0 \quad (7.53)$$

$$\oint_{\text{loop}} \mathbf{E} \cdot d\mathbf{l} = -\frac{d\Phi}{dt} \quad (7.55)$$

$$\oint_{\text{loop}} \mathbf{B} \cdot d\mathbf{l} = \mu_0 I + \mu_0 \epsilon_0 \int_{\text{surface}} \frac{\partial \mathbf{E}}{\partial t} \cdot d\mathbf{s} \quad (7.57)$$

Equation (7.51) is “Gauss’s law”

Equation (7.55) is “Faraday’s law”

\mathbf{E} electric field

\mathbf{B} magnetic flux density

\mathbf{J} current density

ρ charge density

$d\mathbf{s}$ surface element

$d\tau$ volume element

$d\mathbf{l}$ line element

Φ linked magnetic flux ($= \int \mathbf{B} \cdot d\mathbf{s}$)

I linked current ($= \int \mathbf{J} \cdot d\mathbf{s}$)

t time