

ELECTRICAL CIRCUITS

Q1/ (i) $Q = I t$


so $Q = 1.00 \times 10^{-9} \times 1.00 \times 10^{-9} \text{ (C)}$

$\therefore \# \text{ electrons} = \frac{Q}{e} = \frac{1.00 \times 10^{-18}}{1.602 \times 10^{-19}} = 6.24$

so **Six electrons**

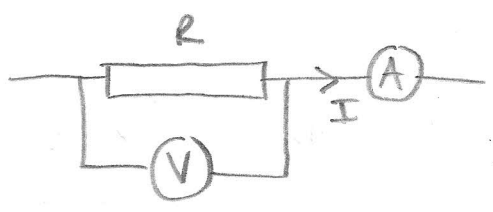(ii) $P = I^2 R \therefore I = \sqrt{\frac{P}{R}} = \sqrt{\frac{2.0}{10}} = 0.45 \text{ A}$


$V = IR \therefore V = 4.47 \text{ Volts}$



$P = \frac{V^2}{R}$ so if $V \rightarrow 2V$
 $R \rightarrow \frac{1}{2}R$

$P \rightarrow \frac{(2V)^2}{\frac{1}{2}R} \Rightarrow P \rightarrow 8 \frac{V^2}{R} \text{ i.e. } P \rightarrow 8P$

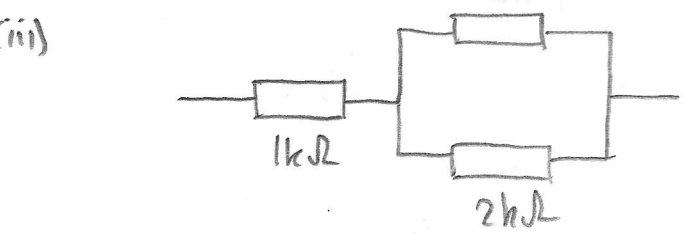so multiply power dissipated by a factor of eight.



$R = 1 + \frac{1}{\frac{1}{3} + \frac{1}{2}} \text{ (k}\Omega\text{)}$

$= 2\frac{1}{5} \text{ k}\Omega \leftarrow \text{Don't express as fractions} \Rightarrow \text{infinite precision!}$
 $= 2.2 \text{ k}\Omega$

(iv) $eV = E = 1.602 \times 10^{-19} \times 5000 \text{ (J)}$
 $= 8.01 \times 10^{-16} \text{ J}$

(KE of electron if conversion of electrical energy is 100% efficient)


so $\frac{1}{2} m_e v^2 = eV \leftarrow \text{Classical KE formula.}$

$v = \sqrt{\frac{2eV}{m_e}}$

$\frac{v}{c} = \sqrt{\frac{eV}{\frac{1}{2} m_e c^2}} = \sqrt{\frac{1.602 \times 10^{-19} \times 5000}{\frac{1}{2} \times 9.109 \times 10^{-31} \times (2.998 \times 10^8)^2}} = 0.14$

(i) so 14% of the speed of light mean relativistic effects probably cannot be ignored.

(v)

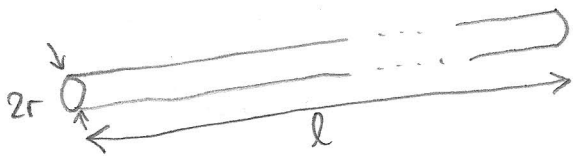

$$2r = 1 \text{ mm}$$

$$R = 1 \Omega$$

$$\rho = 1.68 \times 10^{-8} \Omega \text{m}$$

↑
resistivity of
copper.

$$R = \frac{\rho l}{\pi r^2}$$

so

$$l = \frac{\pi R r^2}{\rho}$$

$$\therefore l = \frac{\pi \times 1 \times (0.5 \times 10^{-3})^2}{1.68 \times 10^{-8}}$$

$$l = 46.7 \text{ m} \rightarrow \text{calculator memory.}$$

Now $l \rightarrow 3l$ and $R \rightarrow 0.5 \Omega$ i.e. $R \rightarrow R/2$

$$r = \sqrt{\frac{\rho l}{\pi R}}$$

so

$$2r = 2 \sqrt{\frac{\rho l}{\pi R}}$$

$$2r = 2 \sqrt{\frac{\rho \cdot 3l}{\pi R/2}}$$

$$2r = 2 \sqrt{\frac{\rho l}{\pi R}} \times \sqrt{6}$$


$$\text{So } 2r = \underbrace{1 \text{ mm}}_{\text{previous diameter}} \times \sqrt{6}$$

$$= 2.45 \text{ mm}$$

Check by direct substitution:

$$2r = 2 \times \sqrt{\frac{1.68 \times 10^{-8} \times 3 \times 46.7}{\pi \times 0.5}} = 2.45 \times 10^{-3} \text{ m} \quad \checkmark$$

(vi)

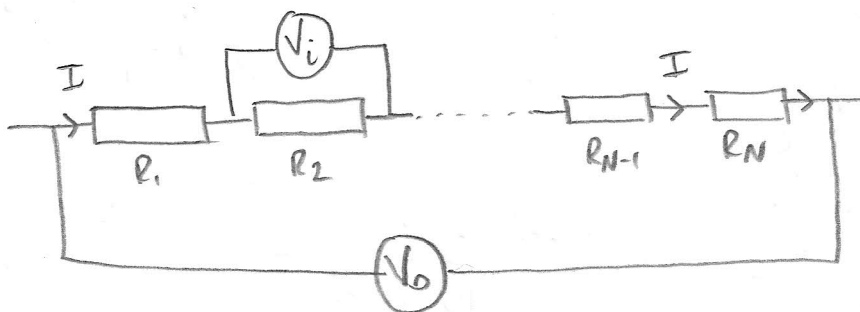

Kirchoff I
(i.e. conservation of
charge) \Rightarrow current
 I_i flowing

through resistor $R_i = I = \text{constant}$. If this were not
the case, charge would be gained or lost in the circuit.

(2)

So if $R_i = V_i / I_i$ (definition of resistance)


and $V_0 = V_1 + V_2 + \dots + V_N$ { Kirchhoff II or conservation of energy) and $I_i = I$

$$\Rightarrow V_0 = I (R_1 + R_2 + \dots + R_N)$$

Now total resistance is V_0 / I

$$\therefore R_{\text{TOT}} = R_1 + R_2 + \dots + R_N$$

So resistances in series add.

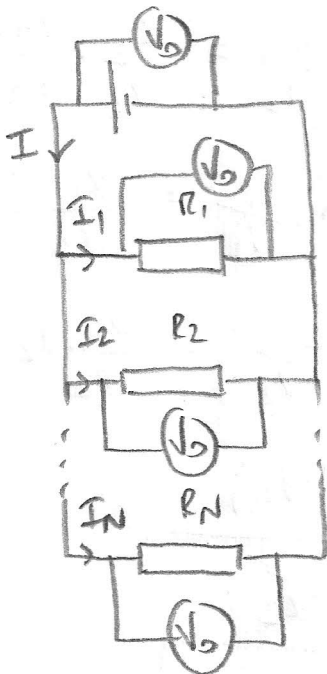

Each resistor is connected to the same cell, so "feels" the same electric field and \therefore PD across each loop is $= V_0$.

Now current I drawn from cell (wired pure supply providing voltage V_0)

$$\text{is } I = I_1 + I_2 + \dots + I_N$$

(Kirchhoff I). Now $I_i = V_i / R_i$
and $V_i = V_0$


$$\therefore I = V_0 \left(\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} \right)$$

If total resistance $R_{\text{TOT}} = V_0 / I \Rightarrow I / V_0 = \frac{1}{R_{\text{TOT}}}$

$$\therefore \frac{1}{R_{\text{TOT}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

So resistances add in reciprocals when wired in parallel.

(viii)

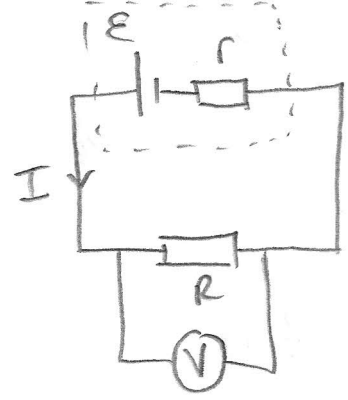

ϵ EMF

r internal resistance

Potential divider idea:

$$V = \epsilon \times \frac{R}{R+r} \quad (\text{Direct } \checkmark)$$

$$\text{or: } \epsilon = Ir + IR \quad (\text{KII})$$

$$\therefore \frac{\epsilon}{R+r} = I$$

$$V = IR \therefore V = \frac{\epsilon R}{R+r} \checkmark$$

$$\text{So } V_1 = \frac{\epsilon R_1}{R+r_1} \quad (1)$$

$$(1)/(2) : \frac{V_1}{V_2} = \frac{R_1}{R_2} \cdot \frac{R+r_2}{R+r_1}$$

$$V_2 = \frac{\epsilon R_2}{R+r_2} \quad (2)$$

$$\therefore (R+r_1) \frac{V_1}{V_2} = \frac{R_1}{R_2} (R+r_2)$$

$$\text{So } r \left(\frac{V_1}{V_2} - \frac{R_1}{R_2} \right) = \frac{R_1}{R_2} R_2 - R_1 \frac{V_1}{V_2}$$

$$\therefore r = \frac{R_1 \left(1 - \frac{V_1}{V_2} \right)}{\frac{V_1}{V_2} - \frac{R_1}{R_2}}$$

$$\therefore r = \frac{R_1 \left(\frac{V_1}{V_2} - 1 \right)}{\frac{R_1}{R_2} - \frac{V_1}{V_2}}$$

$$\text{So } r = \frac{10.0 \left(\frac{10.43}{9.88} - 1 \right)}{\frac{10.0}{7.0} - \frac{10.43}{9.88}} = \boxed{1.5 \Omega} \quad (1.49 \Omega \text{ to } 3 \text{sf})$$

$$\text{In (1): } \epsilon = \frac{V_1 (R+r_1)}{R_1} = \frac{10.43 (1.49 + 10)}{10} = \boxed{12.0 \text{ V}}$$

(4)

$$(ix) R = \frac{\rho l}{\pi r^2}$$

$$r = 10 \times 10^{-6} \text{ m}$$

(radius of tungsten filament)


$$\rho = 5.4 \times 10^{-8} \text{ } \Omega \text{ m}$$

$$R = 40 \text{ } \Omega$$

$$\text{So } l = \frac{R \pi r^2}{\rho}$$



$$\therefore l = \frac{40 \times \pi \times (10 \times 10^{-6})^2}{5.4 \times 10^{-8}}$$

$$l = 0.233 \text{ m}$$

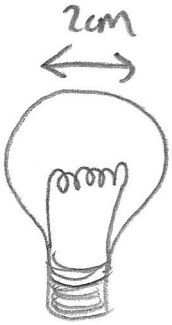

A 23 cm filament is rather on the long side for a lightbulb (!) So filaments tend to be tightly coiled. The width of a filament bulb might be $\approx 2 \text{ cm}$.

(x)

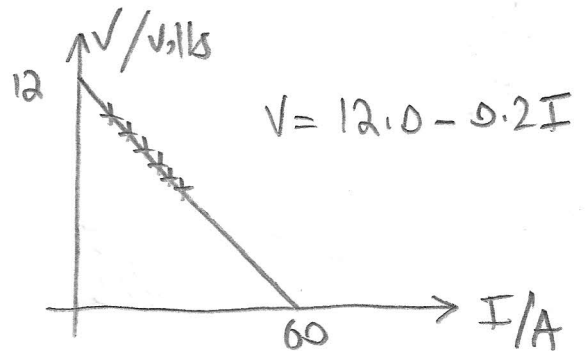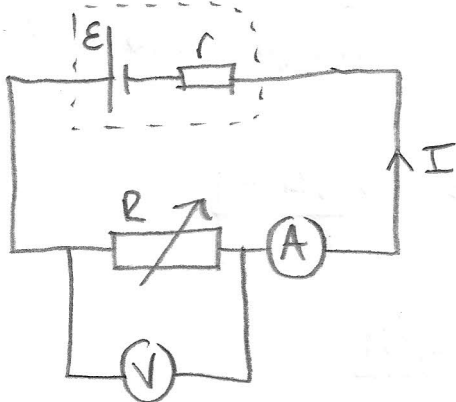

$$\mathcal{E} = Ir + V$$

$$V = IR$$

$$\text{So } V = \mathcal{E} - Ir \text{ . Comparing with } V = 12.0 - 0.2I$$

$$\therefore \boxed{\begin{matrix} \mathcal{E} = 12.0 \text{ volts} \\ r = 0.2 \text{ } \Omega \end{matrix}}$$

{ You probably won't measure currents more than 2.0 A safely! }

↑
So extrapolate to $V=0$.

Power dissipated by variable resistor is $I^2 R = P$


$$\text{Now } I = \frac{\mathcal{E}}{R+r}$$

$$\text{So } P = \frac{\mathcal{E}^2 R}{(R+r)^2}$$

$$\{ I = \frac{12.0}{5+0.2} = 2.31 \text{ A} \}$$

$$\therefore \text{ when } R = 5.0 \text{ } \Omega : P = \frac{12^2 \times 5}{(5+0.2)^2} = \boxed{26.6 \text{ W}}$$

(5)

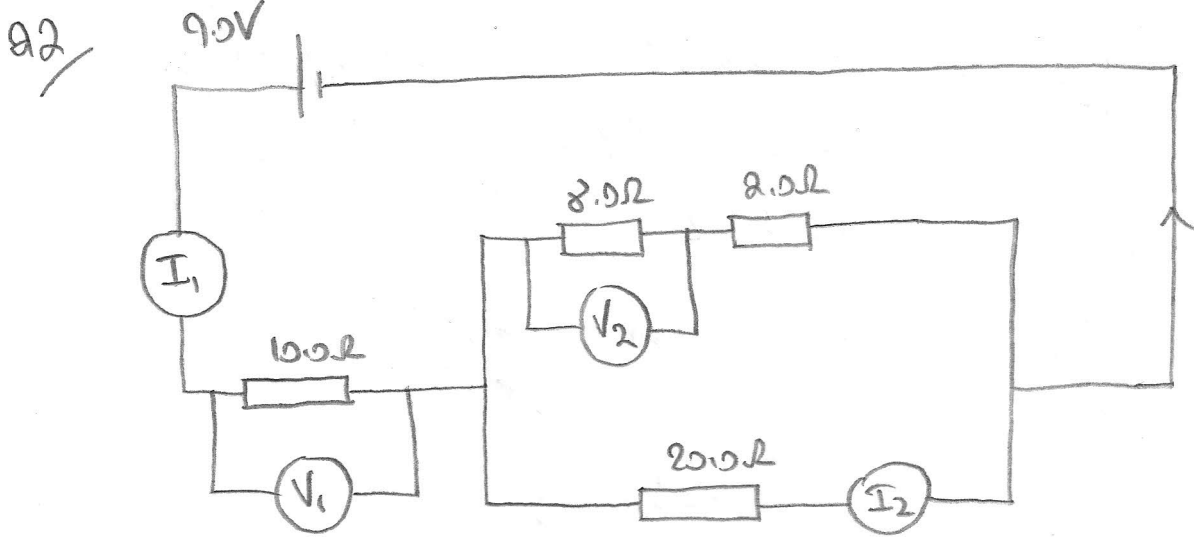

Total resistance is: $R = 10.0 + \frac{1}{\frac{1}{8+2} + \frac{1}{20}}$

$$= 16\frac{2}{3} \Omega \quad (16.7\Omega)$$

↑
keep exact for below or calc

$$\therefore I_1 = \frac{9.0}{16\frac{2}{3}} \text{ (A)} = \boxed{0.54 \text{ A}}$$


$$V_1 = I_1 \times 10.0\Omega = \boxed{5.4 \text{ V}}$$

$$\therefore I_2 = \frac{9 - 5.4}{20.0} \text{ (A)} = \boxed{0.18 \text{ A}}$$

$$\therefore V_2 = (0.54 - 0.18) \times 8.0 \quad (\text{V})$$

$$= \boxed{2.88 \text{ V}}$$

3/

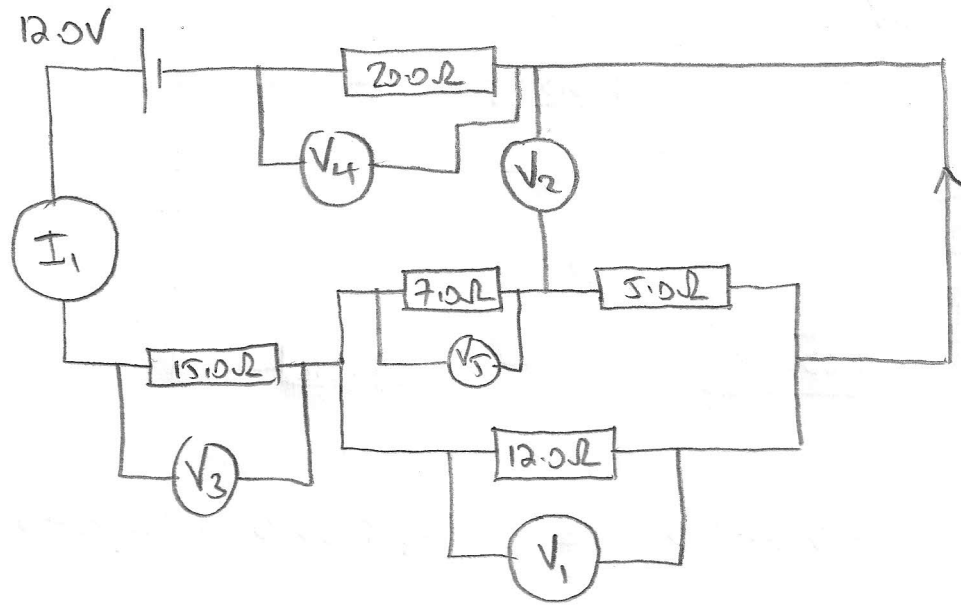

$$I_1 = \frac{12.0}{R_{TOT}} = \frac{12.0}{15.0 + \frac{1}{\frac{1}{7+5} + \frac{1}{12}} + 20.0} \quad (A)$$

$$= \frac{12.0}{41} = \boxed{0.293 \text{ A}}$$

Total resistance = 41Ω

$$V_3 = 12.0 \times \frac{15}{41} = \boxed{4.39 \text{ V}}$$

$$V_4 = 12.0 \times \frac{20}{41} = \boxed{5.85 \text{ V}}$$

$$V_1 = 12.0 - V_3 - V_4 = 12.0 \times \left(1 - \frac{15}{41} - \frac{20}{41}\right)$$

$$= 1\frac{31}{41} \text{ V} = \boxed{1.76 \text{ V}}$$

$$V_5 = V_1 \times \frac{7}{7+5} = \boxed{1.02 \text{ V}}$$


$$V_2 = 12.0 - V_3 - V_5 - V_4$$

$$= 12.0 - 12 \times \frac{15}{41} - \underbrace{1\frac{31}{41} \times \frac{7}{12}}_{V_5} - 12 \times \frac{20}{41}$$

$$= \frac{30}{41} \text{ V} = \boxed{0.73 \text{ V}}$$

7

4

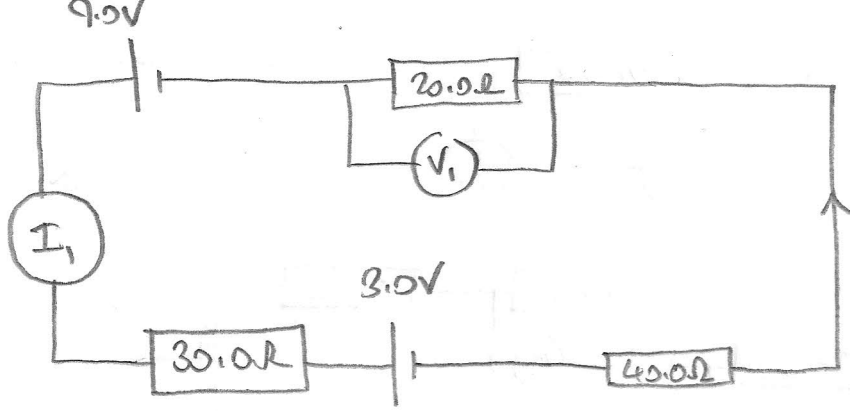


KVL: $9.0 - 3.0 = I_1 \times 30.0 + I_1 \times 40.0 + I_1 \times 20.0$
 Net EMF for loop

$\Rightarrow I_1 = \frac{6.0}{30 + 40 + 20} = 0.067 \text{ A} = \boxed{66.7 \text{ mA}}$

$V_1 = I_1 \times 20.0 = \boxed{1.33 \text{ Volts}}$

5

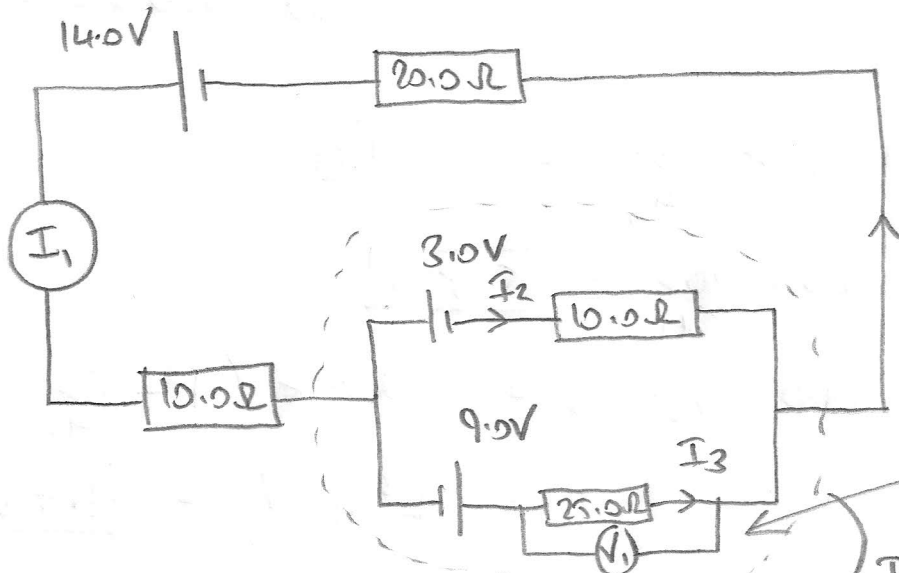

KVL: $I_1 = I_2 + I_3$

KVL: $3.0 + 9.0 = I_3 \times 25 - I_2 \times 10$
 $\Rightarrow 25I_3 - 10I_2 = 12$ (1)

{ Take care to follow direction of || as you go upside down in a loop }

KVL: (lower loop) $\Rightarrow 14 + 9 = I_1 \times 10 + I_3 \times 25 + I_1 \times 20$
 $\Rightarrow 23 = 30I_1 + 25I_3$ (2)

! oops. In question, V1 is across 9.0V bat...
 This loop
 will sweep at the end.

So using $I_1 = I_2 + I_3$: $23 = 30I_2 + 55I_3$ (2)

8

$$\therefore 75I_3 - 10I_2 = 12 \quad (1)$$

$$30I_2 + 55I_3 = 23 \quad (2)$$

$$3(1) + (2): 75I_3 + 55I_3 = 36 + 23$$

$$I_3 = \frac{59}{130} = \boxed{0.45A}$$

$$\text{In } (2): I_2 = \frac{23 - 55 \times \left(\frac{59}{130}\right)}{30} \quad \leftarrow I_3$$

$$= \boxed{-0.065A}$$

(So I_2 is in the opposite direction as shown in the diagram)

$$\therefore I_1 = I_2 + I_3 = \boxed{0.39A}$$

Now V_1^* is actually $-I_3 \times 25.0 + 9.0$ to match the question.

$$\text{ie } 9.0 - \frac{59}{130} \times 25 = \boxed{-2.35V}$$

(Sign doesn't really matter, it depends which way the voltmeter (V_1) is connected. If the 'red' end is on the right, the result is $-2.35V$).

* In the diagram here, $V_1 = I_3 \times 25.0$ Volts.

6/ Power cable carries power $P = VI$

$$\text{loss is } kP = I^2 R$$

$$k = 0.009$$

$$V = 750 \times b^3 \text{ volts}$$


$$P = 2000 \times b^6 \text{ W.}$$

$$l = 1600 \times b^3 \text{ m}$$

$$\rho = 2.8 \times b^{-8} \text{ km}$$

$$R = \frac{\rho l}{\pi r^2}$$

$$r = \sqrt{\frac{\rho l}{\pi R}}$$

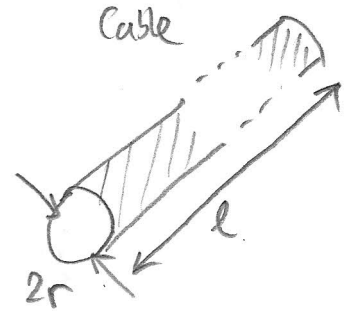

$$\text{so } I = \frac{P}{V}$$

$$\therefore kP = \frac{P^2}{V^2} R$$

$$\therefore \frac{kV^2}{P} = R$$


$$\therefore r = \sqrt{\frac{\rho l}{\pi kV^2/P}}$$

$$\therefore r = \sqrt{\frac{\rho \rho l}{\pi kV^2}}$$

$$\therefore r = \sqrt{\frac{2000 \times b^6 \times 2.8 \times b^{-8} \times 1600 \times b^3}{\pi \times 0.009 \times (750 \times b^3)^2}}$$

$$= 0.075 \text{ m} = \boxed{75.1 \text{ mm}}$$


(so a 15 cm diameter cable).

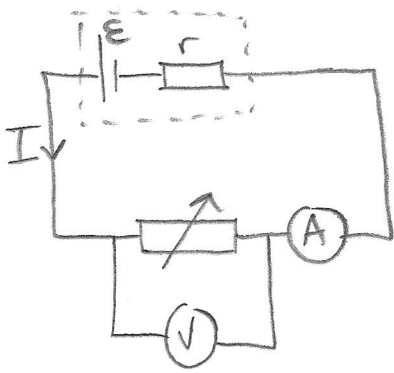

Power dissipated in variable resistor R is $P = I^2 R$

$$I = \frac{\varepsilon}{r+R}$$
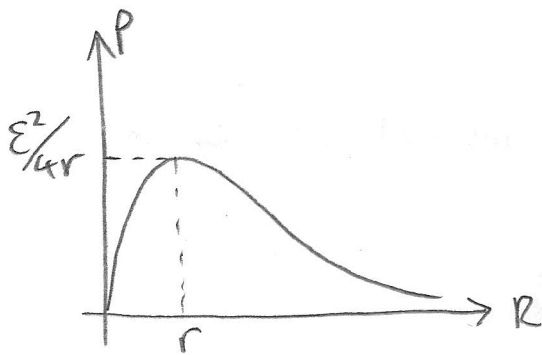
$$\therefore P = \frac{\varepsilon^2 R}{(r+R)^2}$$



when $R=0$, $P=0$
 $R \rightarrow \infty$, $P \rightarrow 0$

Stationary point when $\frac{dP}{dR} = 0$

$$\frac{dP}{dR} = \frac{(r+R)^2(1) - R(2(r+R)(1))}{(r+R)^4} \times \varepsilon^2$$

so $\frac{dP}{dR} = 0$ when $(r+R)^2 - 2R(r+R) = 0$

$$(r+R)(r+R-2R) = 0$$

$$(r+R)(r-R) = 0$$


and \therefore since $r, R > 0 \Rightarrow \boxed{r=R}$

when $r=R$, $P = \frac{\varepsilon^2 r}{(2r)^2} = \boxed{\frac{\varepsilon^2}{4r}}$ i.e. Maximum power dissipated.

See spreadsheet for $\varepsilon = 5V$ vs $\varepsilon = 7V$
 $r = 4\Omega$ vs $r = 2\Omega$

Max power: $\frac{5^2}{4 \times 4} = \boxed{1.56W}$



$\frac{7^2}{4 \times 2} = \boxed{6.13W}$

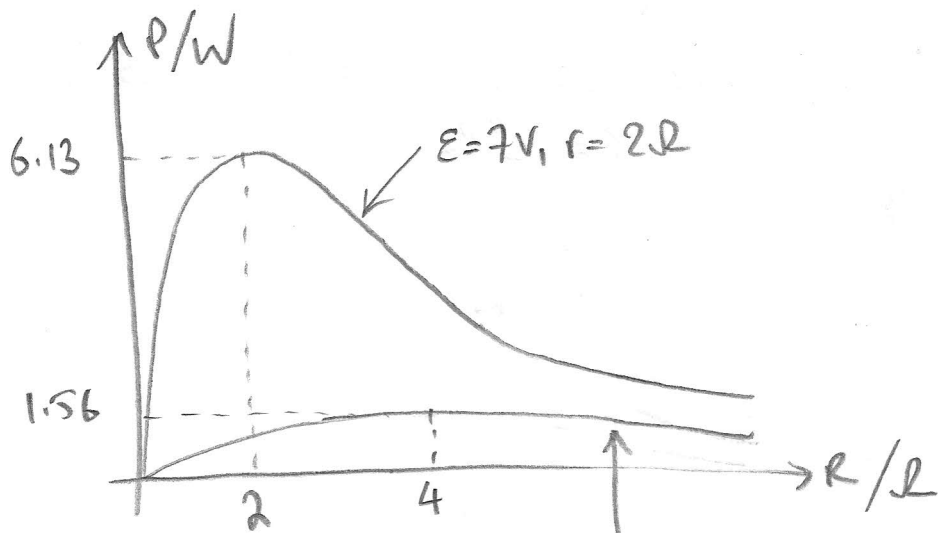

$E = 7V, r = 2R$


$E = 5V, r = 4R$

2/

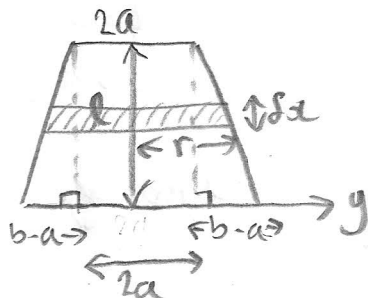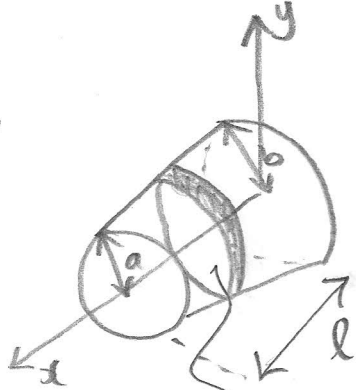

Truncated cone cross section

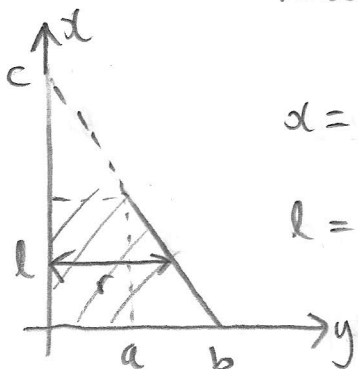resistance of cylinder is $\delta R = \frac{\rho \delta x}{\pi r^2}$



$x = c - \frac{l}{b-a} y$

$l = c - \frac{l}{b-a} a$

$\therefore c = l \left(1 + \frac{a}{b-a} \right)$

$\therefore c = \frac{l(b-a+a)}{b-a}$

$c = \frac{lb}{b-a}$

So $x = \frac{l(b-y)}{b-a}$

in our case $r=y$

So $\frac{(b-a)x}{l} = b-y$

$\therefore y = r = b - \frac{(b-a)x}{l}$

$\therefore \delta R = \frac{\rho \delta x}{\pi \left(b - \frac{(b-a)x}{l} \right)^2}$

(2)

Since resistors add in series, total resistance of the truncated cone is

$$R = \int_0^l \rho R \Rightarrow R = \int_{x=0}^l \frac{\rho dx}{\left(b - \frac{(b-a)x}{l}\right)^2}$$

$$R = \frac{\rho}{\pi} \int_0^l \frac{dx}{\left(b - \frac{(b-a)x}{l}\right)^2}$$

Now $\frac{d}{dx} \left(\frac{1}{A-Bx} \right) = \frac{-1}{(A-Bx)^2} (-B) = \frac{B}{(A-Bx)^2}$

$$\therefore \int \frac{1}{(A-Bx)^2} dx = \frac{1}{B} \frac{1}{A-Bx} + C$$

$$\therefore R = \frac{\rho}{\pi} \frac{1}{(b-a)/l} \left[\frac{1}{b - \frac{(b-a)x}{l}} \right]_0^l$$

$$\therefore R = \frac{\rho}{\pi} \frac{l}{b-a} \left[\frac{1}{b - (b-a)} - \frac{1}{b} \right]$$


$$\therefore R = \frac{\rho}{\pi} \frac{l}{b-a} \left(\frac{1}{a} - \frac{1}{b} \right)$$

$$\therefore R = \frac{\rho}{\pi} \frac{l}{b-a} \left(\frac{b-a}{ab} \right)$$



$$\therefore \boxed{R = \frac{\rho l}{\pi ab}} \quad \text{as required.}$$

Does it make sense? well let $a=b \Rightarrow R = \frac{\rho l}{\pi a^2}$
 i.e. resistance of a cylinder ✓

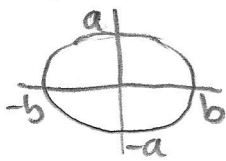[Note since πab is the cross sectional area of an ellipse, this means an elliptical resistor has the same resistance of a truncated cone!]



9/

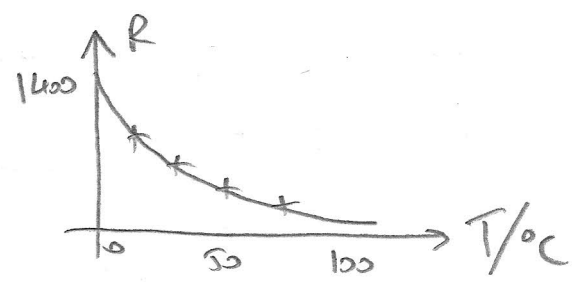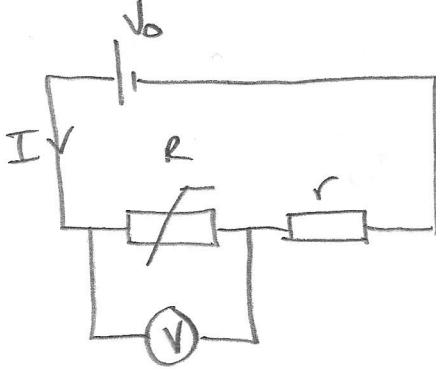

let R for thermistor be
 $R = R_0 e^{-kT}$

(example: $k = 0.0271$, $R_0 = 1183 \Omega$)
 $0^\circ\text{C} < T < 90^\circ\text{C}$
 \uparrow \uparrow
 T_{\min} T_{\max}

$$V = V_0 \times \frac{R}{R+r}$$

$$V = \frac{V_0 R_0 e^{-kT}}{R_0 e^{-kT} + r}$$

$$V = \frac{V_0 R_0}{R_0 + r e^{kT}}$$

$$\Delta V = V(T_{\min}) - V(T_{\max})$$

$$\therefore \Delta V(r) = V_0 R_0 \left(\frac{1}{R_0 + r e^{kT_{\min}}} - \frac{1}{R_0 + r e^{kT_{\max}}} \right)$$

$$\frac{d\Delta V}{dr} = V_0 R_0 \left(\frac{-e^{kT_{\min}}}{(R_0 + r e^{kT_{\min}})^2} + \frac{e^{kT_{\max}}}{(R_0 + r e^{kT_{\max}})^2} \right)$$

so $\frac{d\Delta V}{dr} = 0$ when $\frac{e^{kT_{\min}}}{(R_0 + r e^{kT_{\min}})^2} = \frac{e^{kT_{\max}}}{(R_0 + r e^{kT_{\max}})^2}$

$$\Rightarrow \frac{R_0 + r e^{kT_{\max}}}{e^{\frac{1}{2}kT_{\max}}} = \frac{R_0 + r e^{kT_{\min}}}{e^{\frac{1}{2}kT_{\min}}}$$

$$\therefore r \left(e^{\frac{1}{2}kT_{\max}} - e^{\frac{1}{2}kT_{\min}} \right) = R_0 \left(e^{-\frac{1}{2}kT_{\min}} - e^{-\frac{1}{2}kT_{\max}} \right)$$


$$r = R_0 \frac{\left(e^{-\frac{1}{2}kT_{\min}} - e^{-\frac{1}{2}kT_{\max}} \right)}{e^{\frac{1}{2}kT_{\max}} - e^{\frac{1}{2}kT_{\min}}}$$

← This is the optimum r which maximizes ΔV .

So for our numbers: $r = 1183 \Omega \times \frac{\left(1 - e^{-\frac{1}{2} \cdot 0.0271 \times 90} \right)}{e^{\frac{+0.0271 \times 90}{2}} - 1}$

$$= \boxed{349 \Omega}$$

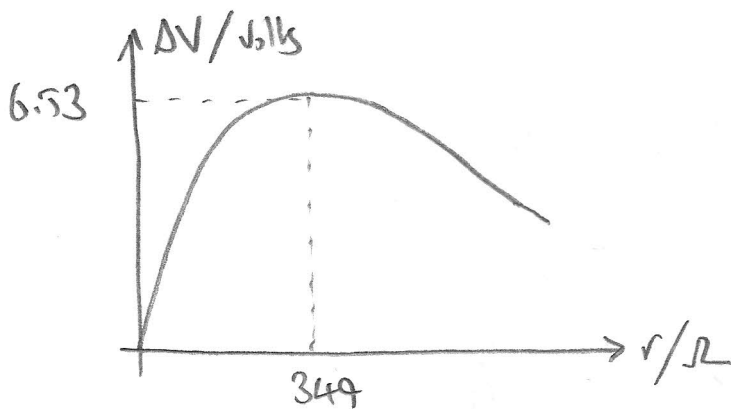See spreadsheet for a plot of $\Delta V(r)$.




(if $V_0 = 12$ Volts).

Q10/

Resistance of the first circuit is:

$$R_{TOT} = R + \frac{1}{\frac{1}{R} + \frac{1}{R + \frac{1}{\frac{1}{R} + \frac{1}{R + \dots}}}}$$
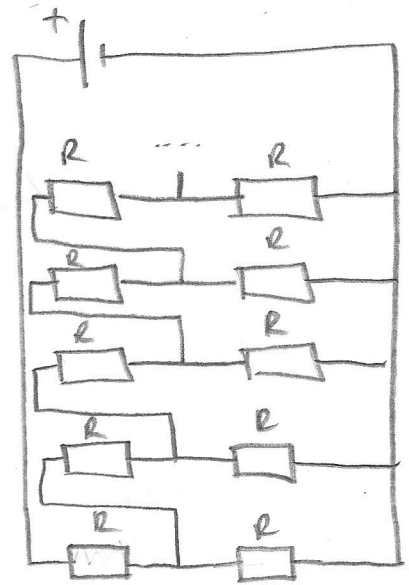
$$= R \left(1 + \frac{1}{1 + \frac{1}{1 + \frac{1}{1 + \frac{1}{1 + \dots}}}} \right)$$



A "continued fraction"

Now if $\phi = (\dots)$

$$\phi = 1 + \frac{1}{\phi}$$

$$\therefore \phi^2 = \phi + 1$$

$$\therefore \phi^2 - \phi - 1 = 0$$

$$\left(\phi - \frac{1}{2}\right)^2 - \frac{1}{4} - 1 = 0$$

$$\left(\phi - \frac{1}{2}\right)^2 = \frac{5}{4}$$


$$\phi = \frac{1}{2} \pm \frac{\sqrt{5}}{2}$$

Now clearly $\phi > 0$

$$\phi = \frac{1 + \sqrt{5}}{2}$$

The Golden Ratio!

$$\approx 1.618$$

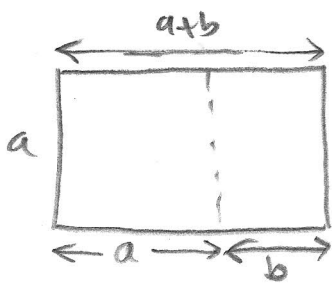

(a > b)

Golden ratio when $\frac{a+b}{a} = \frac{a}{b} = \phi$

$$\therefore 1 + \frac{1}{\phi} = \phi$$

which is the same as above.

$$\therefore \phi = \frac{1 + \sqrt{5}}{2}$$

Resistance of the second circuit is:

$$R_{\text{tot}} = R \left(3 + \frac{1}{7 + \frac{1}{15 + \frac{1}{292 + \frac{1}{1 + \frac{1}{2 + \frac{1}{3 + \dots}}}}} \right)$$

$$\approx 3.14151 R$$

$$\approx \boxed{\pi R} \quad (\pi = 3.14159265359\dots)$$

Resistance of the third circuit is:

$$R_{\text{tot}} = R \left(6 + \frac{1}{2 + \frac{1}{12 + \frac{1}{2 + \frac{1}{12 + \dots}}} \right)$$

$$\text{let } \alpha = 12 + \frac{1}{2 + \frac{1}{12 + \frac{1}{2 + \dots}}}$$

$$\therefore (\dots) = \alpha - 6 = 12 + \frac{1}{2 + \frac{1}{\alpha}} - 6$$

$$\therefore \alpha = 12 + \frac{1}{2 + \frac{1}{\alpha}}$$

$$\alpha = 12 + \frac{\alpha}{2\alpha + 1}$$

$$(2\alpha + 1)\alpha = 12(2\alpha + 1) + \alpha$$

$$2\alpha^2 - 24\alpha - 12 = 0$$

$$\alpha^2 - 12\alpha - 6 = 0$$


$$(\alpha - 6)^2 - 42 = 0$$

$$\therefore \alpha - 6 = \pm \sqrt{42}$$

$$\alpha > 0 \text{ so } \alpha - 6 = \boxed{\sqrt{42}}$$


In "Mitch Hiker's Guide to the Galaxy" "42" is the answer to the "Ultimate Question", pondered by the mega-computer "Deep Thought". So the circuit "at the bottom of Deep Thought" should have a resistance of $\sqrt{42} R$!

Q11

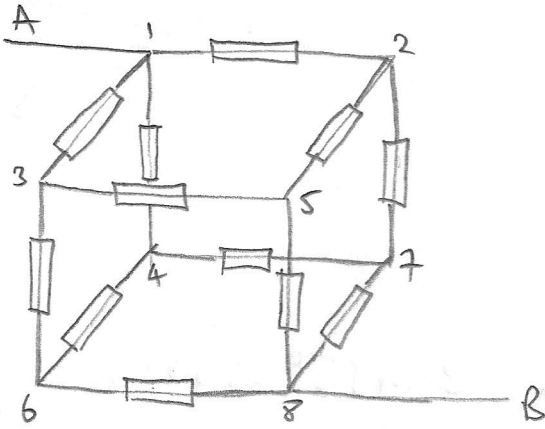

Consider a cube of identical resistors. Each has a resistance of $1R$.

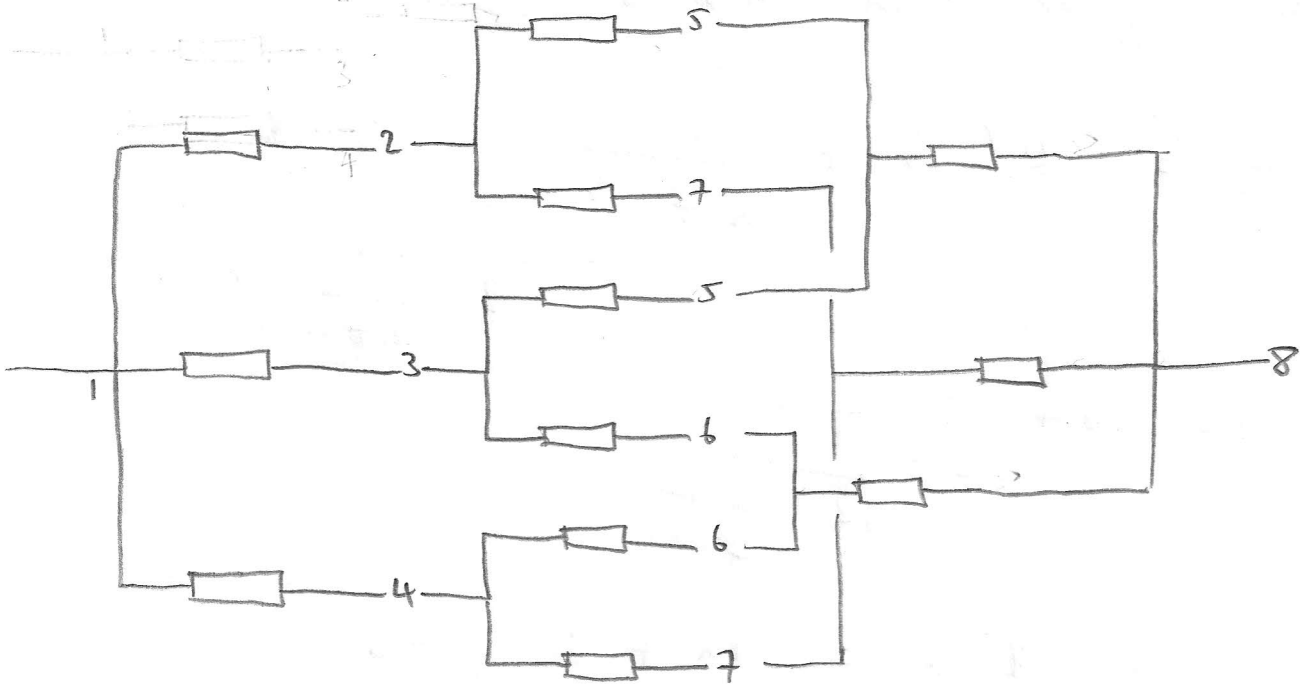To find the resistance between A and B we need to redraw the circuit in 2D!




Now this is tricky to consider as a connection of parallel circuits because of the way the second set of vertices cross-link.

And so a trick is needed! (Note this only works because all the resistors are the same, without this you would have to solve a set of simultaneous equations for currents in each wire, using kI and kII).

The trick is, by symmetry, voltages at 2,3,4 ARE THE SAME. Ditto for 6,7,5.

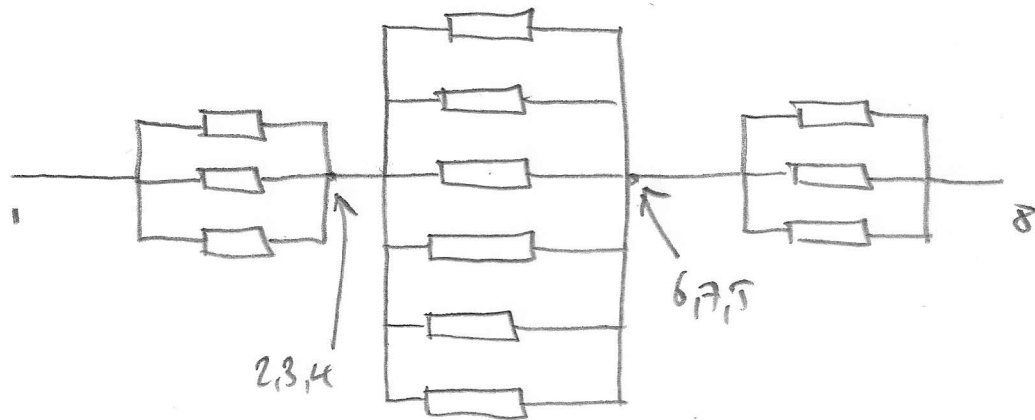∴ we can consider the following equivalent circuit:



The total resistance is therefore:

$$\frac{1}{3} + \frac{1}{6} + \frac{1}{3} = \boxed{\frac{5}{6}} \quad (2)$$

Extension: Write a computer program to solve the 12 equations (simultaneous) for currents I_i through a set of n resistors wired like this, given a PD V_{AB} between A and B. Use this information to find the total current I_{AB} and hence find $R_{AB} = V_{AB}/I_{AB}$.

AF 22/7/20