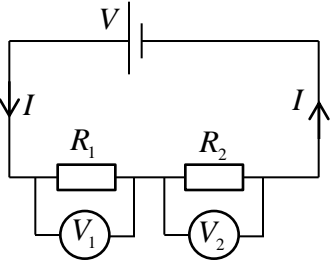


Series & Parallel circuits

Electronic systems consist of networks of basic components which modify the rate of flow of charge (*current*) and energy per unit charge (*voltage*) between two points in the network. In order to model the behaviour of a system, it is useful to understand the basic mathematical features. We shall consider *resistive* components (i.e. those which obey *Ohm's Law*) and the difference between *series* and *parallel* arrangements of resistors.

Series circuits



The *same* current must flow through every component in the loop, otherwise charge would be created or lost.

$$V_1 = IR_1 \quad \text{Apply Ohm's law to each resistor in turn}$$

$$V_2 = IR_2$$

$$V = IR \quad \text{Apply Ohm's law to entire series loop. } R \text{ is the total resistance}$$

$$V = V_1 + V_2 \quad \text{The applied voltage } V \text{ must be divided across the resistors}$$

Hence:

$$IR = IR_1 + IR_2$$

$$\therefore \boxed{R = R_1 + R_2} \quad \text{so series resistors add}$$

We can use this result to show that resistances in series can act as *potential dividers*

$$I = \frac{V_1}{R_1} = \frac{V}{R_1 + R_2} \quad \therefore \frac{V_1}{R_1} = \frac{V}{R_1 + R_2}$$

$$\boxed{V_1 = \frac{R_1}{R_1 + R_2} V} \quad \text{i.e. the voltage across a resistor is the same fraction of the applied voltage as the ratio of resistance to the total resistance.}$$

Ohm's Law

$$V = IR$$

Voltage / volts
Energy per unit charge lost across a conductor of resistance R

Resistance / ohms (Ω)


Current / amps
Rate of flow of charge through resistor R

Note due to a quirk of history, **conventional current is the 'flow of positive charge'**. Unfortunately **electrons** were discovered after many of the electrical conventions were fixed. Since it is the *electrons which are mobile in a conductor*, current can be thought of as the flow of 'holes' of net positive charge left when an electron has been moved via an electric field.



Georg Ohm
1789-1854

Parallel circuits

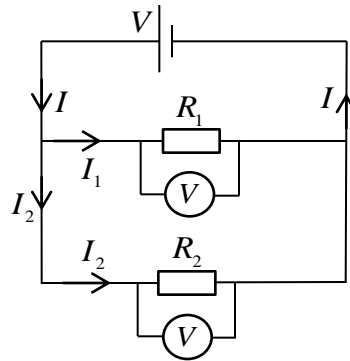

$$V = IR \quad \text{Apply Ohm's law to entire circuit. } R \text{ is the total resistance}$$

$$V = I_1 R_1 \quad \text{Apply Ohm's law to each resistor in turn. Same electric field across each loop, so the same voltage is dropped across the resistors}$$

$$V = I_2 R_2$$

Current is assumed to be contained within the circuit, hence:


$$I = I_1 + I_2 \quad \leftarrow \text{This is Kirchhoff's law}$$

Therefore:

$$V / R = V / R_1 + V / R_2$$

$$\therefore \boxed{\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}} \quad \text{so parallel resistor loop resistance reciprocals add}$$

Series circuit example

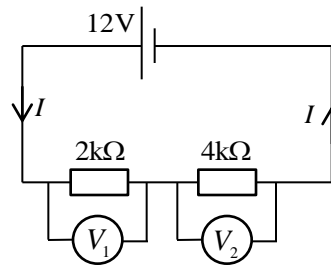


$$I = \frac{12}{2 + 4} \text{ mA}$$

$$I = 2 \text{ mA}$$

$$V_1 = \frac{2}{2 + 4} \times 12 = \boxed{4\text{V}}$$

$$V_2 = \frac{4}{2 + 4} \times 12 = \boxed{8\text{V}}$$

Parallel circuit example

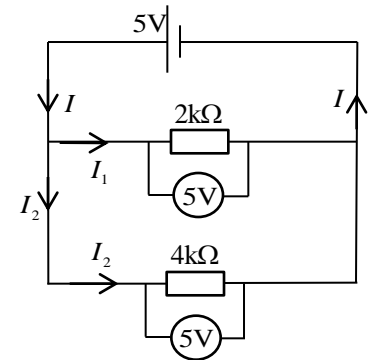

$$I_1 = 5 / 2 = 2.5 \text{ mA}$$

$$I_2 = 5 / 4 = 1.25 \text{ mA}$$

$$I = I_1 + I_2 = \boxed{3.75 \text{ mA}}$$


Ohm's Law then add currents

Or alternatively ...

$$R = \frac{1}{\frac{1}{2} + \frac{1}{4}} = \frac{4}{3} \text{ k}\Omega$$

$$I = 5 / \frac{4}{3} = \frac{15}{4} \text{ mA} = \boxed{3.75 \text{ mA}}$$

Use reciprocal resistance addition rule

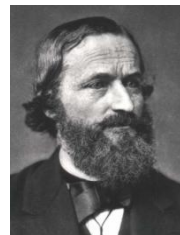

Gustav Kirchhoff
1824-1887