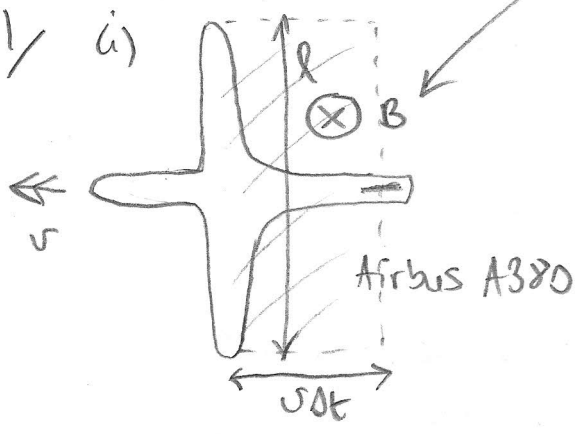


ELECTROMAGNETISM

Earth's magnetic field




In dt seconds, the wings sweep out area $v dt l$.

The magnetic flux linked is $\therefore B v dt l$ and \therefore the rate of change of magnetic flux linked is $\frac{d\Phi}{dt} = B v l$.

By Faraday's law, this is the EMF induced across the wings.

$$V = B v l = 65 \times 10^{-6} \text{ T} \times 1050 \times \frac{1000 \text{ m}}{3600 \text{ s}} \times 79.8 \text{ m}$$

$$= \boxed{1.51 \text{ V}}$$

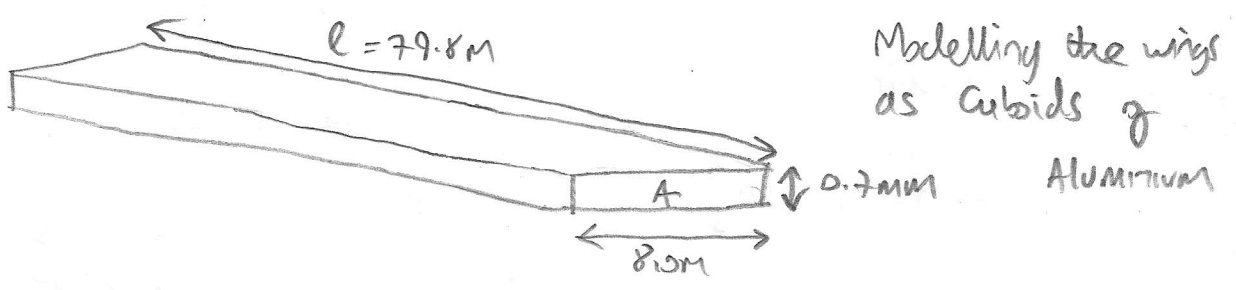

$$I = \frac{V}{R} \quad R = \frac{\rho l}{A}$$


$$\therefore I = \frac{V A}{\rho l} = \frac{1.51 \times 8.0 \times 0.7 \times 10^{-3}}{2.7 \times 10^{-8} \times 79.8}$$

$$= \boxed{3920 \text{ A}}$$

This seems rather large, so one hopes the wings can either (i) harness this current or (ii) increase the resistance of the wings via insulating material.

However, the power of 5.9 kW (VI) is likely to be relatively minor in terms of the jet engine power.

Although, with a thrust of $\times 65.1 \text{ kW}$ (Boeing 747 \rightarrow the A380 will probably be larger) the induced currents and resulting EM braking effect might actually be significant.

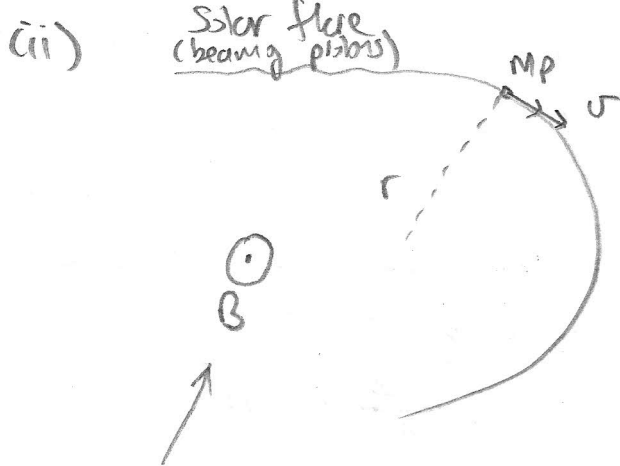

Newton II:

$$\frac{m_p v^2}{r} = B e v$$

$$\frac{m_p v}{B e} = r$$

$$r = \frac{1.67 \times 10^{-27} \times 4.90 \times 10^3}{4.17 \times 10^{-6} \times 1.60 \times 10^{19}}$$


$$r = 12.3 \text{ m}$$

which on the scale of Jupiter is tiny. So expect a visible aurora effect at the poles.

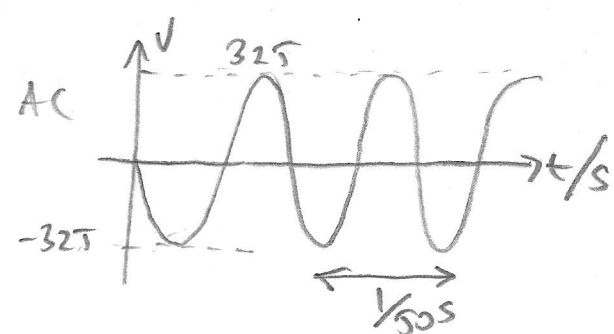
(iii) Diesel generator produces mains AC

$$e = -N B A \omega \sin \omega t$$


So $N = \frac{V_{\text{max}}}{B A \omega}$ # windings in generator


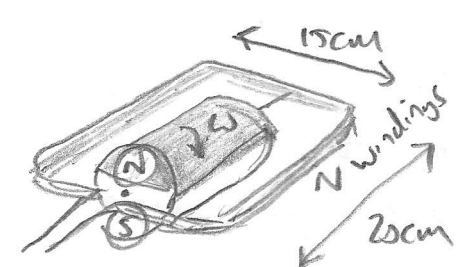
$$\therefore N = \frac{325}{0.05 \times (20 \times 10^{-2} \times 15 \times 10^{-2}) \times 2\pi \times 50} = 690$$



AC generator

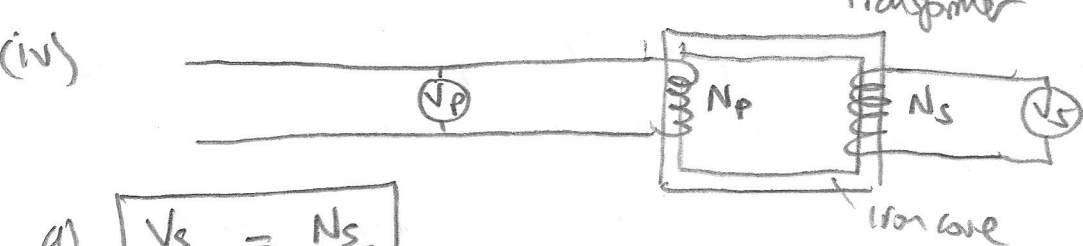

$$\frac{V_s}{V_p} = \frac{N_s}{N_p}$$


$$\therefore N_p = \frac{V_p}{V_s} N_s = \frac{500 \text{ kV}}{4 \text{ kV}} \times 50 = 6250$$

b) $I_s V_s = 0.95 \underbrace{I_p V_p}_{660 \text{ MW}}$ if transformer is 95% efficient.

So $I_p = \frac{660 \times 10^6}{500 \times 10^3} = \boxed{1320 \text{ A}}$

$\therefore I_s = \frac{0.95 \times 660 \times 10^6}{4000} = \boxed{1.57 \times 10^5 \text{ A}}$

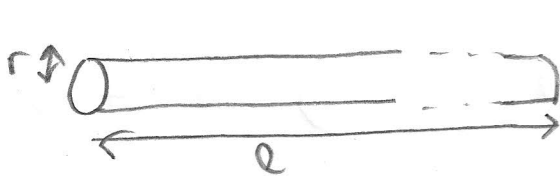c) Assume pair wire suffers a 1% loss over $100 \text{ km} = l$



$$R = \frac{\rho l}{\pi r^2}$$

$$\underbrace{0.01 \times 660 \times 10^6}_{P_{\text{loss}}} = I_p^2 R$$

$$\frac{\rho l}{\pi r^2} = \frac{P_{\text{loss}}}{I_p^2}$$

$$\frac{\pi r^2}{\rho l} = \frac{I_p^2}{P_{\text{loss}}}$$

$$\therefore r = \sqrt{\frac{\rho l I_p^2}{\pi P_{\text{loss}}}}$$

$$r = \sqrt{\frac{2.7 \times 10^{-8} \times 100 \times 10^3 \times 1320^2}{\pi \times 0.01 \times 660 \times 10^6}} \quad (\text{m})$$

$$= \boxed{15.1 \text{ mm}}$$


d) Compute the skin depth $\left(\frac{\delta}{\text{mm}}\right) \approx 5.03 \times 10^5 \sqrt{\frac{\rho}{f}}$

$$= 5.03 \times 10^5 \sqrt{\frac{2.7 \times 10^{-8}}{50}} = \boxed{11.7 \text{ mm}}$$

↑ only for AC signals of frequency f .

So skin current is AC, might get away with slightly thinner cables (which will be lighter).

(vi)

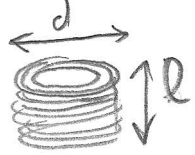

Inductor of inductance

$$L = \frac{\mu_0 N^2 \pi (d/2)^2}{l}$$

∴ # of turns


$$N = \sqrt{\frac{4lL}{\mu_0 \pi d^2}}$$

$$(L = \mu_0 N^2 A / l)$$

$$N = \sqrt{\frac{4 \times 5.0 \times 5^2 \times 1.0}{4\pi \times 10^{-7} \times \pi \times (9.0 \times 10^{-2})^2}}$$


$$N = 2501$$

(vi)

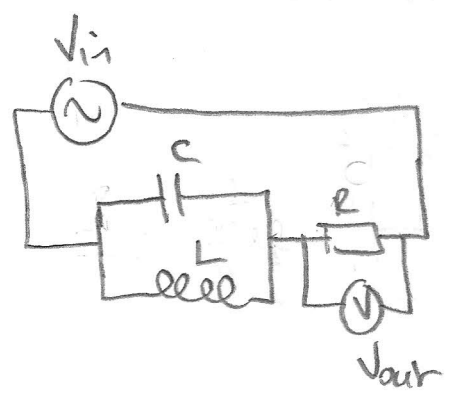

Resonance frequency
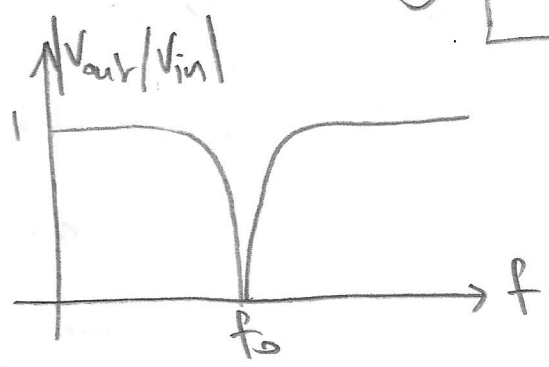
$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$$




$$4\pi^2 f_0^2 = \frac{1}{LC}$$

$$C = \frac{1}{4\pi^2 f_0^2 L}$$

$$C = \frac{1}{4\pi^2 \times 50^2 \times 0.2} = 50.7 \mu F$$

(vii)

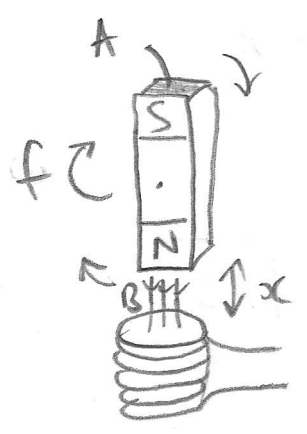

Rate of magnetic flux linked by

$$\text{Solenoid is } BAN_0 f_0 = E_0, \text{ etc}$$

EMF induced.

$$\text{If } l \rightarrow 2l, \text{ expect } B_1 = \frac{B_0}{23}$$

$$E_1 = B_1 A N_1 f_1 \times$$

$$\text{so } \frac{E_1}{E_0} = \frac{B_1 N_1 f_1}{B_0 N_0 f_0}$$

[for frequency f]

(4)

$$\varepsilon_1 = 12.6 \text{ mV} \times \left(\frac{1}{2}\right) \left(\frac{1200}{2400}\right) \left(\frac{5000}{1000}\right)$$


$$\boxed{\varepsilon_1 = 3.9 \text{ mV}}$$

Now $A = (0.5 + b^{-2})^2 \text{ m}^2$

$$\therefore B_0 = \frac{12.6 \times b^{-3}}{(0.5 + b^{-2})^2 \times 2400 \times 1000 \times 2\pi/60}$$

$$\boxed{B_0 = 2.01 \text{ mT}}$$

(viii)

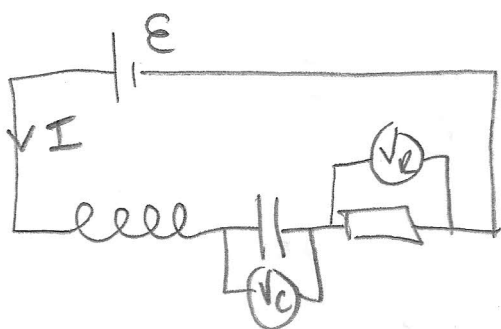

ohm's law:

$$\varepsilon - L \frac{dI}{dt} = V_c + V_R$$

"Back EMF"

$$V_R = IR$$

$$CV_c = \int I dt \quad "Q = CV"$$

$$\therefore I = \frac{C dV_c}{dt} \quad \text{let } V = V_c \text{ for brevity.}$$

Now input power to capacitor is IV (dibs for other components)

From energy conservation $\Rightarrow CV \frac{dV}{dt} = I\varepsilon - I^2 R - LI \frac{dI}{dt}$

$$\boxed{I\varepsilon = I^2 R + LI \frac{dI}{dt} + CV \frac{dV}{dt}}$$

Now $LI \frac{dI}{dt} = \frac{d}{dt} \left(\frac{1}{2} LI^2 \right) \quad CV \frac{dV}{dt} = \frac{d}{dt} \left(\frac{1}{2} CV^2 \right)$

So $I\varepsilon = I^2 R + \frac{d}{dt} \left(\frac{1}{2} CV^2 + \frac{1}{2} LI^2 \right)$


↑
input power

↑
power dissipated in resistor

← Energy stored in C and L

∴ Stored energy in Capacitor is $\frac{1}{2} CV^2$
 and stored energy in Inductor is $\frac{1}{2} LI^2$

2

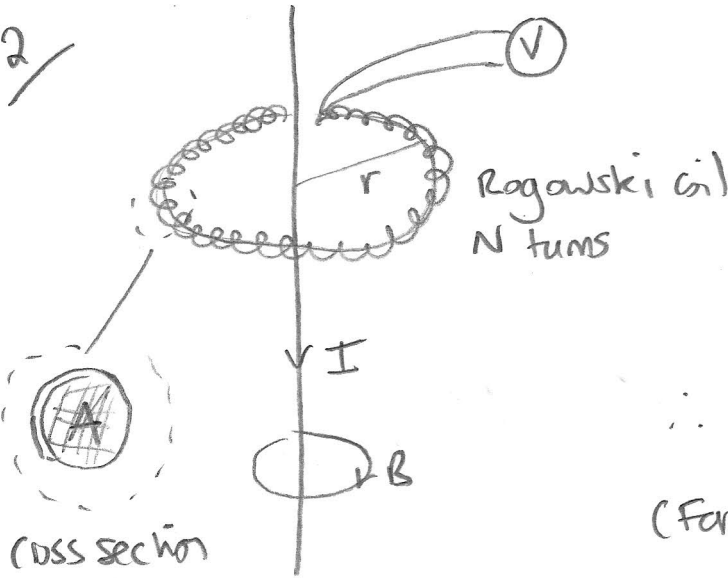

Flux linked by coil is


$$NBA = \Phi$$

$$\Phi = NA \times \frac{\mu_0 I}{2\pi r}$$

∴ EMF induced $V = -\frac{d\Phi}{dt}$
 (Faraday's law)

$$\Rightarrow V = -\frac{NA\mu_0}{2\pi r} \frac{dI}{dt}$$

If $I = I_0 \cos \omega t$

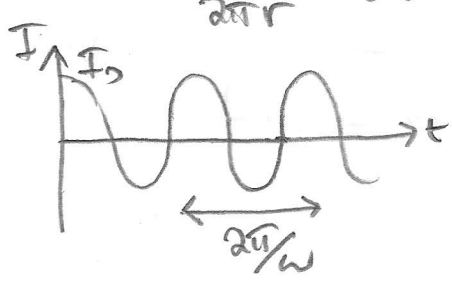

$$\omega = \frac{2\pi}{T}$$

$$T = \frac{2\pi}{\omega}$$

$$\therefore V = -\frac{NA\mu_0}{2\pi r} (-I_0 \omega \sin \omega t)$$

$$\boxed{V = \frac{\omega NA\mu_0 I_0 \sin \omega t}{2\pi r}}$$

[let's try sensible numbers $N = 50$; $A = \pi \times (5 \times 10^{-3})^2 \text{ m}^2$

$$\omega = 2\pi \times 50 \text{ Hz}, \quad r = 2.0 \times 10^{-2} \text{ m}$$


$$\therefore V = \left(\frac{f}{50 \text{ Hz}}\right) \left(\frac{I_0}{A}\right) \sin(2\pi ft) \left(\frac{N}{50}\right) \times \boxed{2.46 \times 10^{-7} \text{ V}}$$

So ideally want quite high frequency AC at around 1-6 A, with a few 100 coils to get a reasonable CRO reading for V.


6

3

MAGNETRON


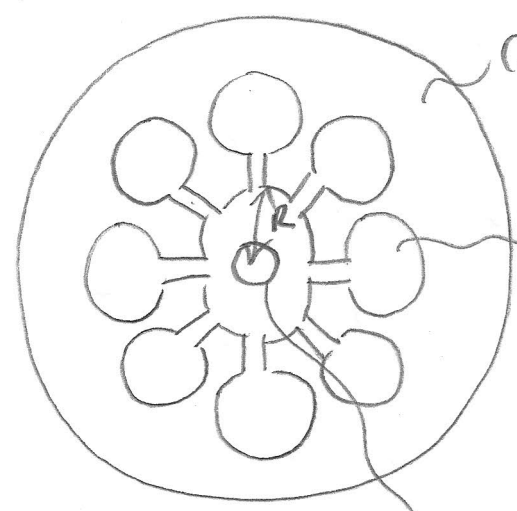


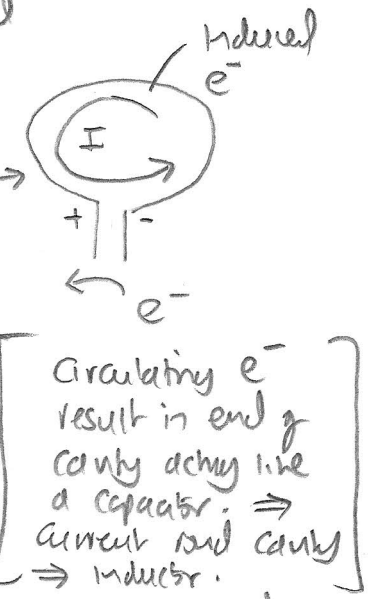Oscillating E and B fields result in EM radiation
17 Microwave spectrum




Cathode, radius r (same of electrons)

Simple model:

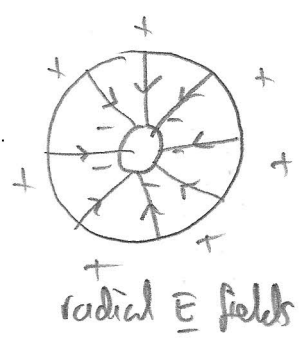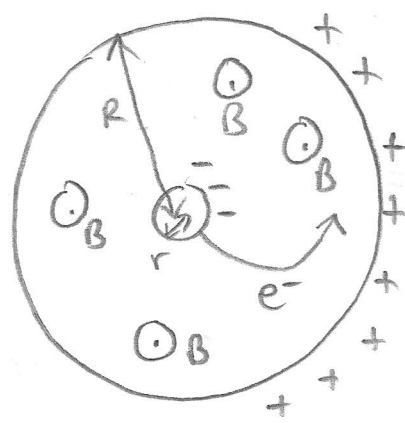

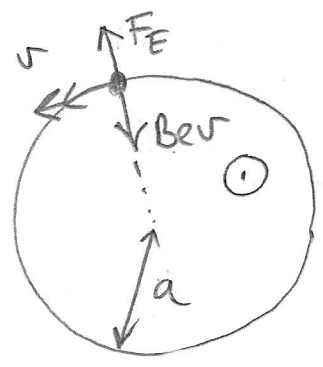If stable circular orbits at radius a (of electrons)



$$NI: \frac{Mv^2}{a} = Bevr - F_E$$

↑ MASS M

Now $F_E = \frac{e\lambda}{2\pi\epsilon_0 a}$ ← Electric field strength

where λ is the charge / unit length along the cathode

Voltage V between anode and cathode is $V = \frac{\lambda}{2\pi\epsilon_0} \ln\left(\frac{R}{r}\right)$

$(V = \int_r^R E dr)$

$$\therefore \lambda = \frac{2\pi\epsilon_0 V}{\ln(R/r)}$$

$-\frac{dV}{dr} = E$

$$\therefore \frac{Mv^2}{a} = Bevr - \frac{e}{2\pi\epsilon_0 a} \frac{2\pi\epsilon_0 V}{\ln(R/r)}$$

(7)

$$\frac{mv^2}{a} = Bev - \frac{eV}{a \ln(R/r)}$$

Now since the magnetic force always acts \perp to the electron velocity, it does no work.

\therefore By conservation of energy: $eV = \frac{1}{2}mv^2$

$$\Rightarrow v = \sqrt{\frac{2eV}{m}} \quad \begin{array}{l} \text{Work done by electric field} \\ \text{This is when } a = R. \end{array}$$

$$\text{so } \frac{2eV}{R} = Be \sqrt{\frac{2eV}{m}} - \frac{eV}{R \ln(R/r)}$$

$$B = \frac{eV}{R} \left(1 + \frac{1}{\ln(R/r)} \right) \sqrt{\frac{m}{2eV}} \frac{1}{e}$$

$$B = \left(1 + \frac{1}{\ln(R/r)} \right) \sqrt{\frac{mV^2}{2eVR^2}}$$

$$B = \left(1 + \frac{1}{\ln(R/r)} \right) \sqrt{\frac{mV}{2eR^2}}$$

$$\text{let } r = 2 \text{ mm} \quad R = 15 \text{ mm} \quad V = 1 \text{ kV}$$

$$m = 9.109 \times 10^{-31} \text{ kg}$$

$$\Rightarrow B = \left(1 + \frac{1}{\ln\left(\frac{15}{2}\right)} \right) \sqrt{\frac{9.109 \times 10^{-31} \times 1000}{2 \times 1.602 \times 10^{-19} \times (15 \times 10^{-3})^2}}$$

$$= \boxed{0.011 \text{ T}}$$

which is quite achievable.

Frequency of circulating electrons is $f = \frac{\omega}{2\pi}$


$$v = R\omega \quad \text{so } f = \frac{v}{R} \frac{1}{2\pi} = \frac{1}{2\pi R} \sqrt{\frac{2eV}{m}}$$

$$= \boxed{0.2 \text{ GHz}}$$




(8)

4/

$\mu g = 9.81 \text{ N/kg}$

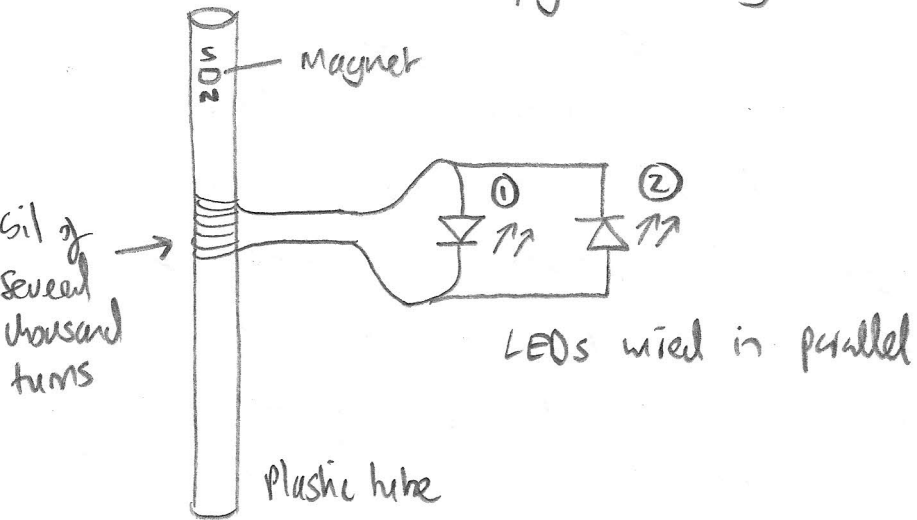

coil of several thousand turns

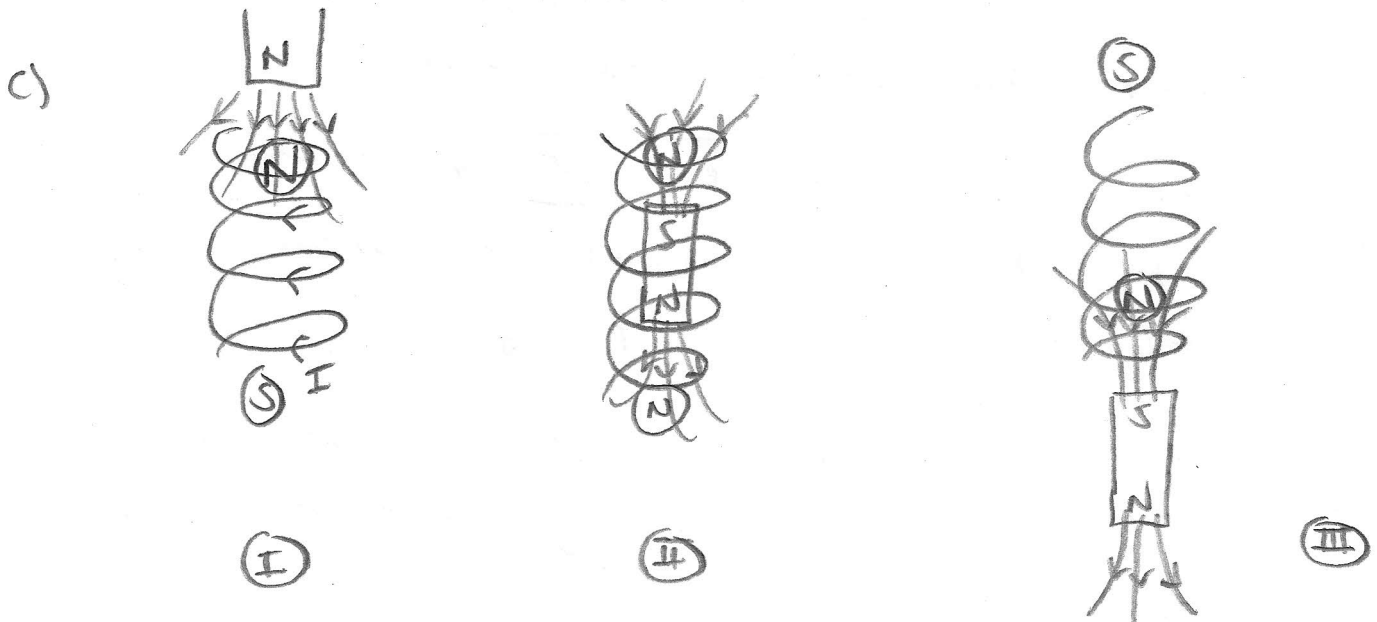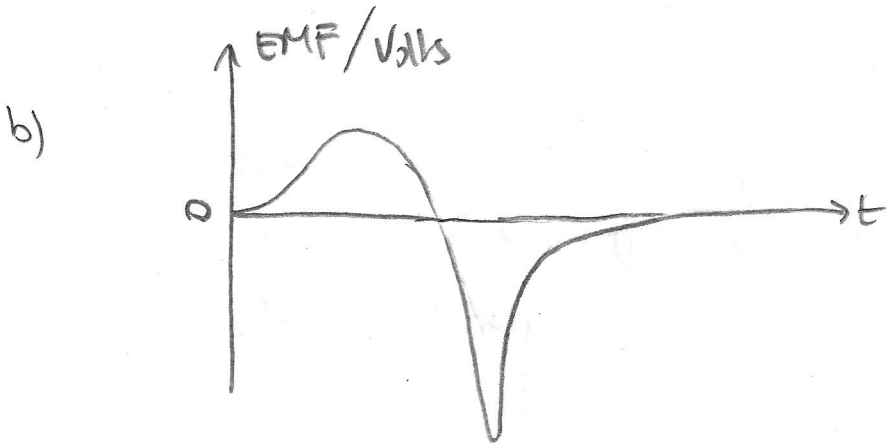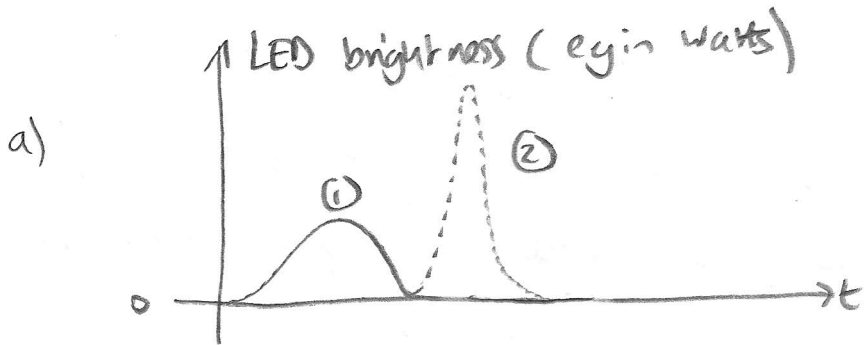

9

(I) Magnet accelerates towards coil.

Coil experiences a rate of change of magnetic flux linked
∴ EMF induced across the coil. LENZ'S law means
an opposing (N) pole is induced in the top of the solenoid.
This means the magnet will experience a resistive (ie
upwards acting) force. However, if the coil is
short, we might not expect the effect of this force
to slow the magnet very much.

Since magnet is accelerating, expect EMF \uparrow

(II)

As magnet passes through the coil it will induce
an EMF of opposing sign to the top half. When the
magnet gets half way there will cancel out
 \Rightarrow zero EMF.

(III)


As the magnet leaves the coil, the -ve EMF
will dominate, as a (N) pole is induced in the
lower half of the coil. (opposite to (I)).

Now the magnet is still accelerating, so
we would expect the maximum EMF to be
larger (and more -ve) than before.

It will also take less time to rise and fall
Since the time to traverse the bottom half of
the coil is $<$ the top half.

once the magnet leaves the coil, the flux
linkage drops by $\approx \frac{1}{r^3}$ since the magnet
 \propto dipole.

(10)

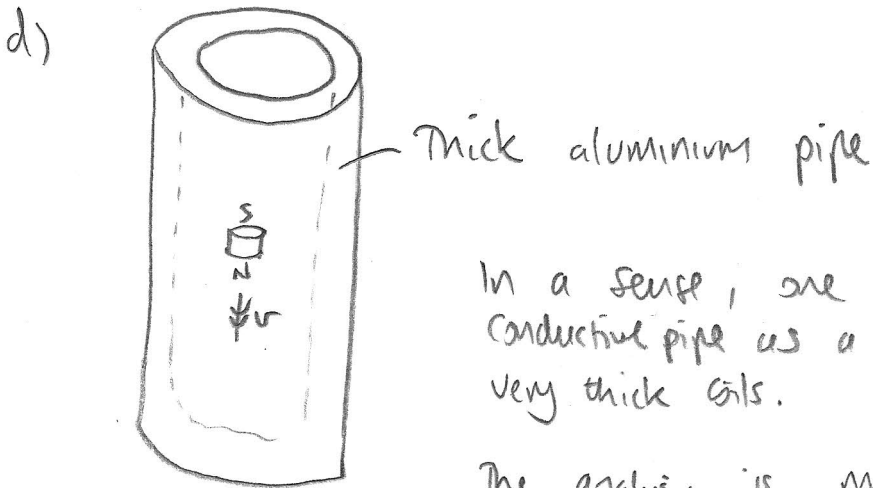

In a sense, one could imagine a thick conducting pipe as a very long solenoid comprising very thick coils.

The analysis is more complex though as currents can swirl in eddies throughout the volume of the pipe - they are not confined to tangentially biled wires.

However, by Fleming's rules, expect tangential currents

Experimentally one observes a significant drag force on the falling magnet, and models predict this is \propto speed.

\therefore expect the magnet to attain a


terminal velocity where the weight of the magnet is balanced by the force of interaction between the falling magnet and the magnetic field set up by the eddy currents induced in the cylinder. $\{$ ignore air resistance \rightarrow use a heavy magnet $\}$.


one way of doing this is to work out the force on a ring element of the pipe:

$$F = B_r \times I \times 2\pi a \quad \text{By Newton III}$$

this is also the upward force on the magnet. But you have to consider the effect of the South pole too!

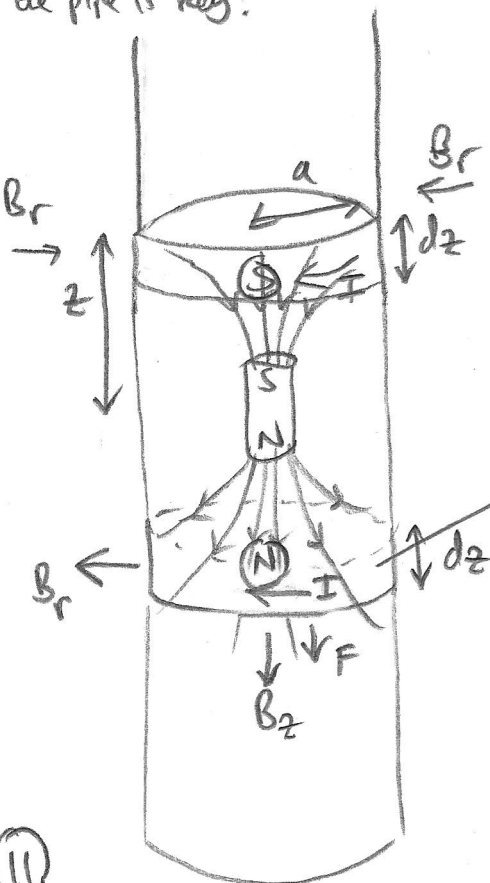It looks like the effects might cancel each other out mid pipe... So perhaps the **START** of the pipe is key?



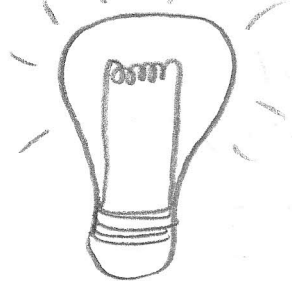

Filament bulb

$N = 50$ coils in length
 $l = 2.0 \text{ cm}$. Wire diameter is
 $d = 0.046 \text{ mm}$.

uncoiled length of wire is
 $l_0 = 580 \text{ mm}$.

wire is made from Tungsten with resistivity $\rho = 5.60 \times 10^{-8} \Omega \cdot \text{m}$.

5/

$$a) i) R = \frac{\rho L}{\pi \left(\frac{d}{2}\right)^2} = \frac{5.60 \times 10^{-8} \times 580 \times 10^{-3}}{\pi \left(0.046 \times 10^{-3} / 2\right)^2} = \boxed{19.5 \Omega}$$

b) ii) Treating the filament as a solenoid (air core)
inductance $L = \frac{\mu_0 N^2 A}{l}$



N loops of coil of length l_0
 $2\pi R N = l_0$

\therefore radius of loop R is given by


$$\therefore R = \frac{l_0}{2\pi N}$$

$$\therefore A = \pi R^2 = \frac{\pi l_0^2}{4\pi^2 N^2} = \frac{l_0^2}{4\pi N^2}$$

$$\therefore L = \frac{\mu_0 N^2}{l} \frac{l_0^2}{4\pi N^2} \Rightarrow \boxed{L = \frac{\mu_0 l_0^2}{4\pi l}}$$

$$\therefore L = \frac{4\pi \times 10^{-7} \times (580 \times 10^{-3})^2}{4\pi \times 2.0 \times 10^{-2}} = \boxed{1.68 \times 10^{-6} \text{ H}}$$

b)

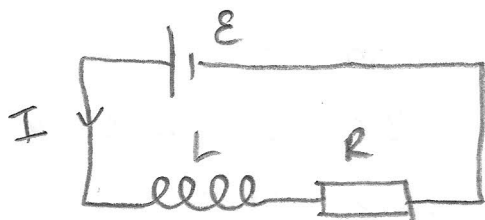

$$\varepsilon = 230\text{V}$$

$$L = 1.68 \times 10^{-6}\text{H}$$

$$R = 19.5\Omega$$

$$\varepsilon - L \frac{dI}{dt} = IR$$

Applied EMF Back EMF due to inductor Ohm's law

$$\Rightarrow \boxed{\varepsilon = L \frac{dI}{dt} + IR}$$

let
$$\boxed{I = \frac{\varepsilon}{R} (1 - e^{-tR/L})}$$

$$\frac{dI}{dt} = \frac{\varepsilon}{R} \frac{R}{L} e^{-tR/L} = \frac{\varepsilon}{L} e^{-tR/L}$$

$$\therefore L \frac{dI}{dt} + IR = \varepsilon e^{-tR/L} + \varepsilon - \varepsilon e^{-tR/L} = \varepsilon \checkmark$$

[let $I = \frac{\varepsilon}{R} - z$ $\therefore \frac{dI}{dt} = -\frac{dz}{dt}$

$$\therefore \varepsilon = -L \frac{dz}{dt} + \left(\frac{\varepsilon}{R} - z\right) R$$

$$\varepsilon = -L \frac{dz}{dt} + \varepsilon - Rz$$

$$L \frac{dz}{dt} = -Rz$$

$$\int_{z_0}^z \frac{1}{z'} dz' = -\frac{R}{L} t$$

when $t=0$, $I=0$

$$\text{so } z_0 = \frac{\varepsilon}{R}$$


$$\therefore \int_{\varepsilon/R}^z \frac{1}{z} dz = -\frac{R}{L} t$$

$$\therefore \left[\ln z \right]_{\varepsilon/R}^z = -\frac{Rt}{L}$$

$$\ln\left(\frac{z}{\varepsilon/R}\right) = -\frac{Rt}{L}$$

$$z = \frac{\varepsilon}{R} e^{-Rt/L}$$
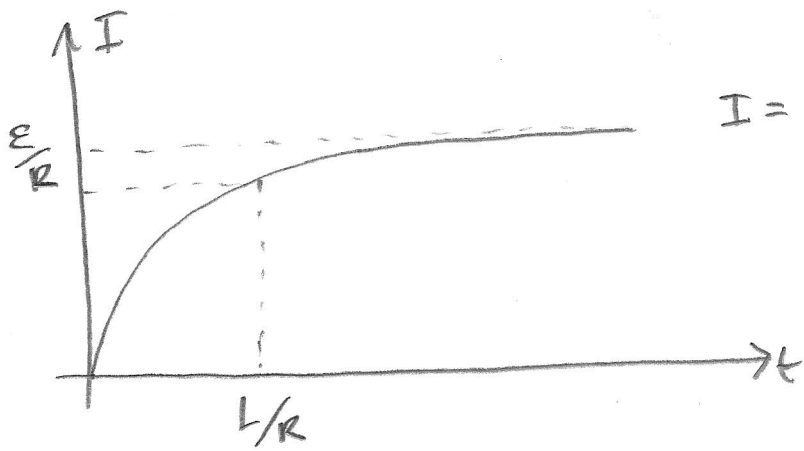
$$\therefore \text{So } I = \frac{\varepsilon}{R} - z \Rightarrow \boxed{I = \frac{\varepsilon}{R} (1 - e^{-tR/L})}$$




$$I = \frac{\varepsilon}{R}(1 - e^{-tR/L})$$

For our filament bulb: $\frac{L}{R} \approx \boxed{8.6 \times 10^{-8} \text{ s}}$

when $t = L/R$: $I = \frac{\varepsilon}{R}(1 - e^{-1}) \approx 0.632 \frac{\varepsilon}{R}$

$$\frac{\varepsilon}{R} = \frac{230}{19.5} = \boxed{11.8 \text{ A}}$$

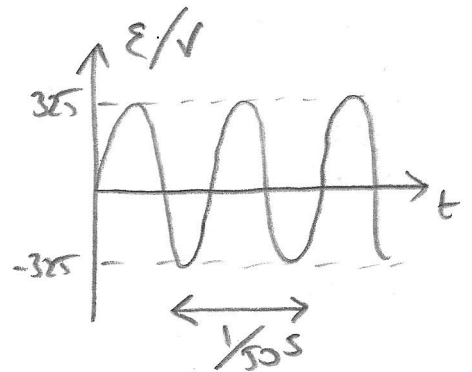c) Mains AC: $\varepsilon = 325 \sin(2\pi \times 50t)$





The current establishment time $\approx 8.6 \times 10^{-8} \text{ s}$
 is \ll than the period of the AC ($2.0 \times 10^{-2} \text{ s}$)

(a factor of about 4.3×10^6). So \therefore we can largely ignore the induction effects on the timescales of mains AC.

Conversely, the assumption of constant ε in $I = \frac{\varepsilon}{R}(1 - e^{-tR/L})$ is valid. over a 10^{-7} s time period, the mains voltage \approx constant.

6/

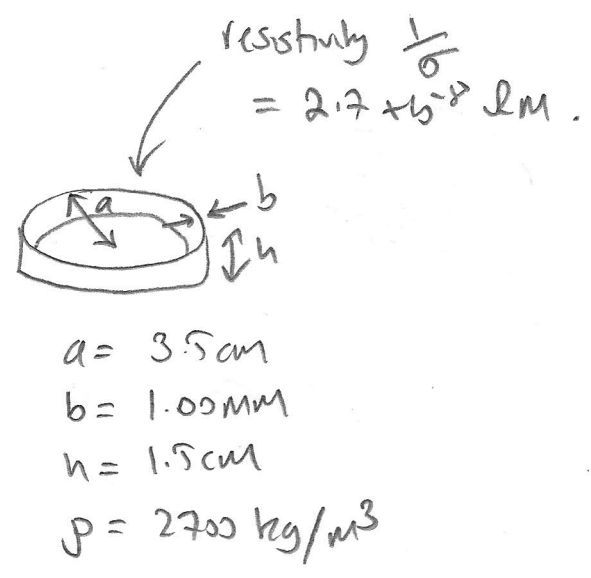
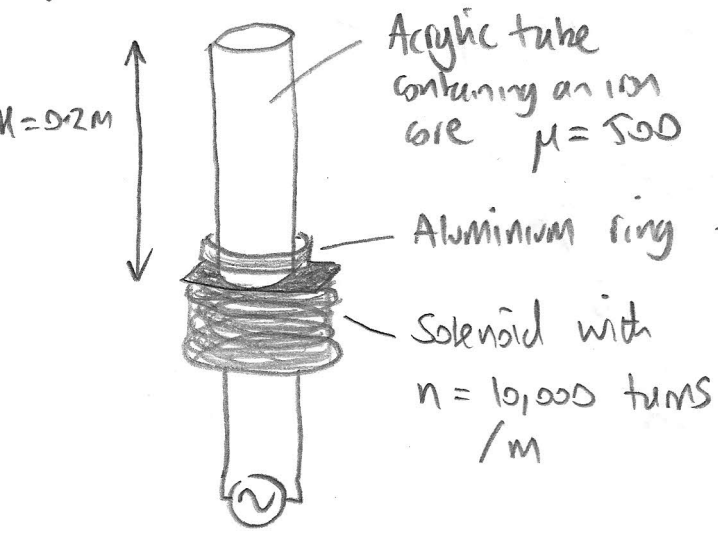


main AC

$$I = I_0 \sin \omega t$$

$$I_0 = 0.2$$
 A

$$\omega = 2\pi \times 50$$
 Hz

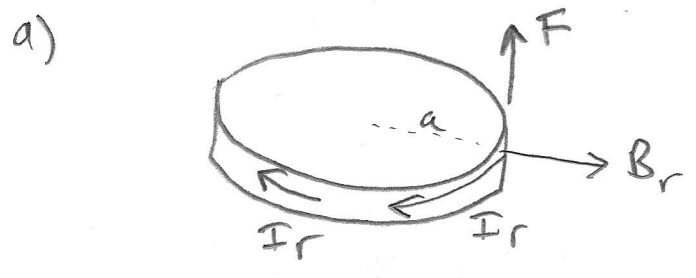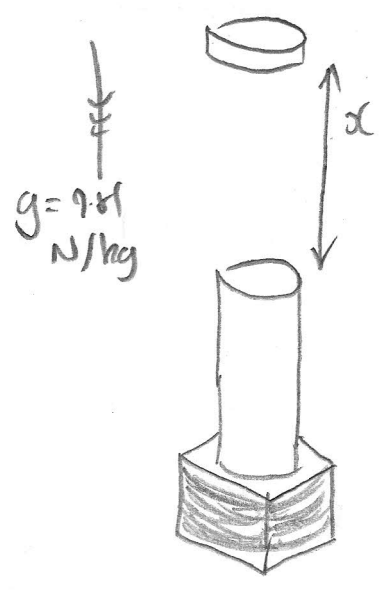


By Fleming's left hand rule, for an upward force on the ring, magnetic field must be radial and induced current tangential as shown.

\therefore using "F = BIL"

$$F = 2\pi a B_r I_r$$

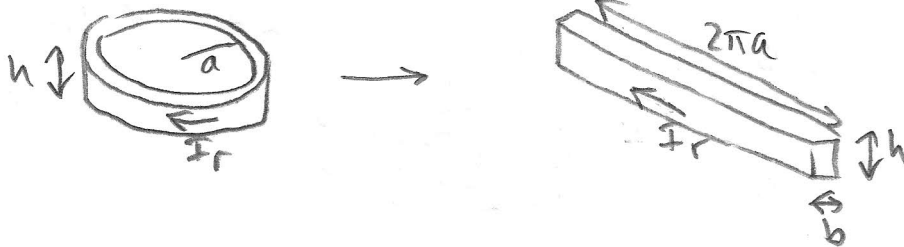b) Since $b \ll a$, ring is $2\pi a$ long and with a cross section of bh .



$$\therefore \text{resistance } R = \frac{1}{\sigma} \frac{2\pi a}{bh}$$

$$R = \frac{2\pi a}{\sigma bh}$$

$$\therefore R = \frac{2\pi \times 3.5 \times 10^{-2} \text{ m}}{2.7 \times 10^8 \text{ S/m} \times 1.00 \times 10^{-3} \text{ m} \times 1.5 \times 10^{-2} \text{ m}} = 4.0 \times 10^{-4} \Omega$$

c) Flux linked by ring is $\Phi = \mu\mu_0 n I \pi a^2$
 So EMF induced (if ignore "Back EMF" due to inductance of ring) is: $\mathcal{E} = -\frac{d\Phi}{dt} = \pi a^2 \mu\mu_0 n \frac{dI}{dt}$
 If $I = I_0 \sin \omega t$
 $\therefore \frac{dI}{dt} = \omega I_0 \cos \omega t$.

$$\therefore \text{Max EMF induced is: } \mathcal{E} = \pi a^2 \mu\mu_0 n \omega I_0$$

$$\approx \pi \times (3.5 \times 10^{-2})^2 \times 500 \times 4\pi \times 10^7 \times 10^4 \times 2\pi \times 50 \times 0.2 \text{ (V)}$$

$$\approx 1.5 \text{ V}$$

Hence max current in the ring is $\approx \frac{1.5 \text{ V}}{4.0 \times 10^{-4} \Omega}$

$$= 3840 \text{ A} \quad (\text{if don't use rounded results})$$


1.8 I_r is really large! If ring is 'held down' expect significant heating.

d) let $B_r = 5 \times 10^{-4} B$


$$\therefore F = 2\pi a I_r B_r \quad B = \mu_0 n I$$

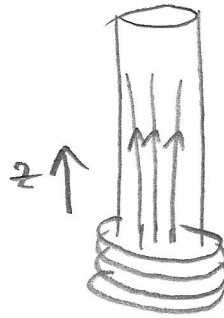1.8 don't expect much radial deviation of magnetic field in iron core

so $F = 2\pi \times 3.5 \times 10^{-2} \times 38400$
 $\times 500 \times 4\pi \times 10^{-7} \times 10^4 \times 0.2$
 $\times 5 \times 10^{-4}$
 $= \boxed{0.53 \text{ N}}$



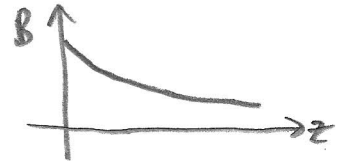Might expect B (and $\therefore B_r$) \downarrow above solenoid though also.



[Compare to mg

$$m = \rho \times 2\pi a \times b \times h = 2700 \times 2\pi \times 3.5 \times 10^{-2} \times 1 \times 10^{-3} \times 1.5 \times 10^{-2}$$

$$= 8.91 \times 10^{-3} \text{ kg}$$

$\therefore mg = 0.087 \text{ N}$ is 16% of 'magnetic upthrust']

\uparrow
 so probably can't ignore.

so net work done in rising α above top of iron column is $FH - mgH$


Let this turn into GPE $mg\alpha$, is total energy at apogee, if GPE zero taken at top of column.

$$\therefore \alpha = \frac{FH - mgH}{mg}$$

$$\alpha = \left(\frac{F}{mg} - 1 \right) H$$

$$\alpha = \left(\frac{0.53}{0.087} - 1 \right) \times 0.2 \approx \boxed{1.01 \text{ m}}$$

7/a)

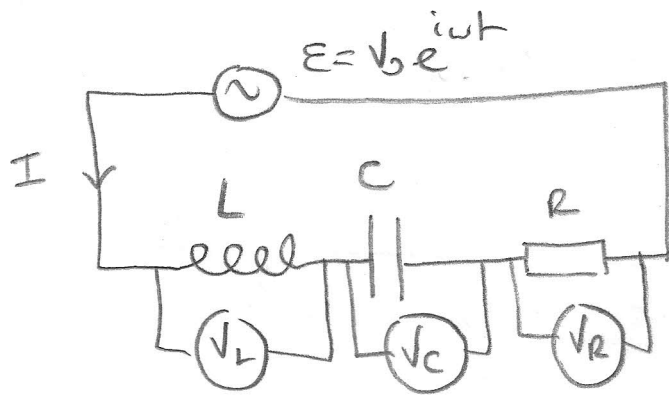

Ohm's law generalized to 'complex impedances'

$$V_C = I z_C$$

$$\mathcal{E} = I(z_L + z_C + z_R)$$

$$\frac{V_C}{\mathcal{E}} = \frac{z_C}{z_L + z_C + z_R}$$

$$z_C = \frac{1}{i\omega C}$$

$$\therefore V_C = \frac{V_0 e^{i\omega t} \frac{1}{i\omega C}}{i\omega L + \frac{1}{i\omega C} + R}$$

$$z_L = i\omega L$$

$$z_R = R$$

Kirchoff II: $\mathcal{E} = V_L + V_C + V_R$
 $\mathcal{E} = +L \frac{dI}{dt} + \frac{1}{C} \int I dt + IR$
 $C V_C = \int I dt$

let $I = I_0 e^{i\omega t - i\phi} \therefore \mathcal{E} = +L i\omega I + \frac{1}{i\omega C} I + IR$

$$\mathcal{E} = I \left(i\omega L + \frac{1}{i\omega C} + R \right)$$

$$\mathcal{E} = I z$$


$$\therefore V_C = \frac{V_0 e^{i\omega t}}{-\omega^2 LC + 1 + i\omega RC}$$

$$V_C = \frac{V_0 e^{i\omega t} (1 - \omega^2 LC - i\omega RC)}{(1 - \omega^2 LC)^2 + \omega^2 R^2 C^2}$$

$$\left[\frac{1}{a+ib} = \frac{a-ib}{(a+ib)(a-ib)} = \frac{a-ib}{a^2 - i^2 b^2} = \frac{a-ib}{a^2 + b^2} \right]$$

$$V_c = A e^{i(\omega t - \phi)} V_0$$
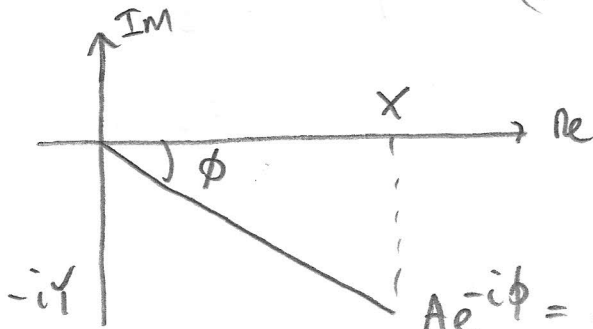
$$\therefore A e^{-i\phi} = \frac{(1 - \omega^2 LC - i\omega RC)}{(1 - \omega^2 LC)^2 + \omega^2 R^2 C^2}$$




$$x = \frac{1 - \omega^2 LC}{(1 - \omega^2 LC)^2 + \omega^2 R^2 C^2}$$


$$y = \frac{\omega RC}{(1 - \omega^2 LC)^2 + \omega^2 R^2 C^2}$$

$$\phi = \tan^{-1} \left(\frac{\omega RC}{1 - \omega^2 LC} \right)$$
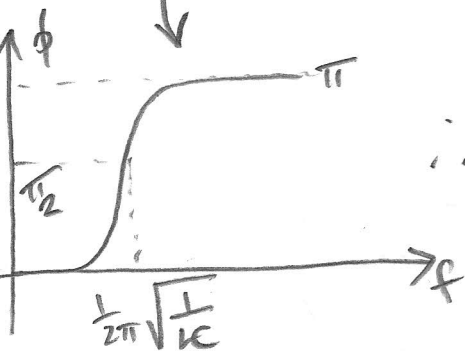
$$A = \sqrt{x^2 + y^2} = \sqrt{\frac{(1 - \omega^2 LC)^2 + \omega^2 R^2 C^2}{[(1 - \omega^2 LC)^2 + \omega^2 R^2 C^2]^2}}$$


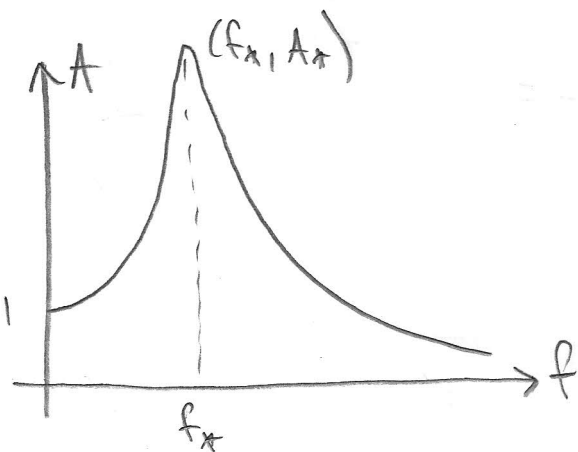
$$A = \frac{1}{\sqrt{(1 - \omega^2 LC)^2 + \omega^2 R^2 C^2}}$$



$$\frac{dA}{d\omega} = -\frac{1}{2} \left((1 - \omega^2 LC)^2 + \omega^2 R^2 C^2 \right)^{-3/2} \times [2(1 - \omega^2 LC)(-2\omega LC) + 2\omega R^2 C^2]$$

$$\text{so } \frac{dA}{d\omega} = 0 \text{ when}$$

$$\omega = 2\pi f$$

$$2\omega LC(1 - \omega^2 LC) = \omega R^2 C^2$$

$$1 - \omega^2 LC = \frac{1}{2} R^2 C^2 / LC$$

$$\frac{1 - \frac{1}{2} R^2 C^2 / LC}{LC} = \omega^2$$

$$\omega_* = \sqrt{\frac{1}{LC} - \frac{R^2 C^2}{2L^2 C^2}}$$

$$\omega_* = \sqrt{\frac{1}{LC} - \frac{1}{LC} \left(\frac{R^2 C^2}{2LC} \right)}$$

$$\omega_* = \sqrt{\frac{1}{LC}} \left(1 - \frac{R^2 C^2}{2LC} \right)^{\frac{1}{2}}$$

$$f_* = \frac{1}{2\pi} \sqrt{\frac{1}{LC}} \left(1 - \frac{R^2 C^2}{2LC} \right)^{\frac{1}{2}}$$

Now: $1 - \omega_*^2 LC = \frac{1}{2} \frac{R^2 C^2}{LC}$

$$\omega_*^2 R^2 C^2 = \left(\frac{1}{LC} - \frac{R^2 C^2}{2LC^2} \right) R^2 C^2$$

$$= \frac{R^2 C^2}{LC} - \frac{R^4 C^4}{2LC^2}$$

$$= \frac{R^2 C^2}{LC} \left(1 - \frac{R^2 C^2}{2LC} \right)$$

$$\therefore (1 - \omega_*^2 LC)^2 = \frac{1}{4} \frac{R^2 C^2}{LC} \frac{R^2 C^2}{LC}$$

$$\therefore (1 - \omega_*^2 LC)^2 + \omega_*^2 RC = \frac{R^2 C^2}{LC} \left(\frac{1}{4} \frac{R^2 C^2}{LC} + 1 - \frac{R^2 C^2}{2LC} \right)$$

$$= \frac{R^2 C^2}{LC} \left(1 - \frac{1}{4} \frac{R^2 C^2}{LC} \right)$$

$$\therefore A_* = \frac{\sqrt{LC}}{RC} \left(1 - \frac{1}{4} \frac{R^2 C^2}{LC} \right)^{-\frac{1}{2}}$$



Now clearly a natural frequency of the system is

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$$

so period $T = \frac{1}{f_0} = \boxed{2\pi\sqrt{LC}}$

RC is a characteristic decay time for capacitor charge and discharge.

Capacitor charge

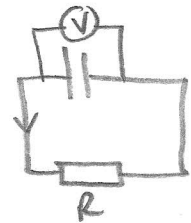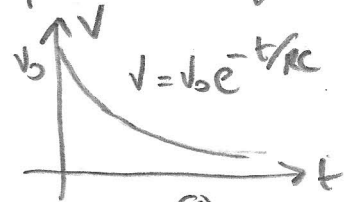

Define: $\tau_c = RC$
 $\tau_L = \sqrt{LC}$

$$f_x = f_0 \left(1 - \frac{1}{2} \left(\frac{\tau_c}{\tau_L} \right)^2 \right)^{\frac{1}{2}}$$

and

$$A_x = \frac{\tau_L}{\tau_c} \left(1 - \frac{1}{4} \left(\frac{\tau_c}{\tau_L} \right)^2 \right)^{-\frac{1}{2}}$$

if $\tau_L \gg \tau_c$

$$f_x \approx f_0$$

$$A_x \approx \frac{\sqrt{L}}{R\sqrt{C}}$$

$$\Rightarrow f_x \approx \frac{1}{2\pi\sqrt{LC}}$$


so $L \uparrow \Rightarrow f_x \downarrow$ as $f_x \propto \frac{1}{\sqrt{L}}$

$A_x \uparrow$ as $A_x \propto \sqrt{L}$

$C \uparrow \Rightarrow f_x \downarrow$ as $f_x \propto \frac{1}{\sqrt{C}}$

$A_x \downarrow$ as $A_x \propto \frac{1}{\sqrt{C}}$

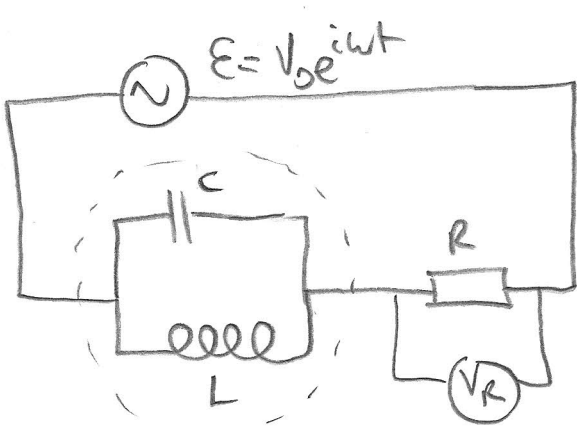$R \uparrow \Rightarrow A_x \downarrow$ as $A_x \propto \frac{1}{R}$



$$V_R = \frac{\epsilon R}{Z + R}$$

$$V_R = \frac{\epsilon R}{\frac{i\omega L}{1 - \omega^2 LC} + R}$$

impedance $Z = \frac{1}{\frac{1}{Z_C} + \frac{1}{Z_L}}$

$$V_R = \frac{\epsilon R (1 - \omega^2 LC)}{i\omega L + R(1 - \omega^2 LC)}$$


$$= \frac{1}{i\omega C + \frac{1}{i\omega L}}$$

$$V_R = \frac{\epsilon R (1 - \omega^2 LC) (R(1 - \omega^2 LC) - i\omega L)}{\omega^2 L^2 + R^2 (1 - \omega^2 LC)^2}$$

$$= \frac{i\omega L}{-\omega^2 LC + 1}$$

$$V_R = A V_0 e^{-i\phi} e^{i\omega t}$$

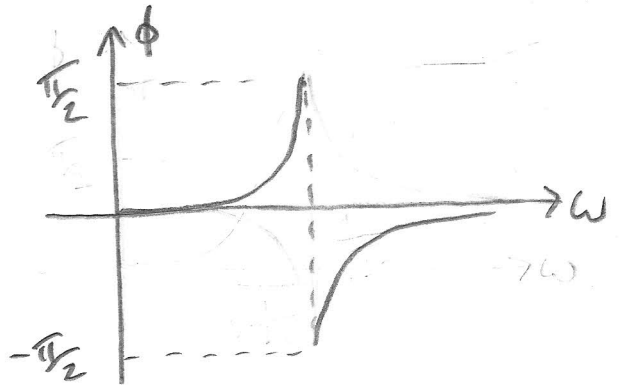
$$\phi = \tan^{-1} \left(\frac{\omega L / R}{1 - \omega^2 LC} \right)$$



$$(1 - \omega^2 LC < 0 \Rightarrow \omega^2 > \frac{1}{LC} \Rightarrow \omega > \frac{1}{\sqrt{LC}})$$

$$A = \frac{R^2 (1 - \omega^2 LC)^2 + \omega^2 L^2}{(\omega^2 L^2 + R^2 (1 - \omega^2 LC)^2)^{1/2}} \times |R(1 - \omega^2 LC)| \leftarrow \text{is } \sqrt{(R(1 - \omega^2 LC))^2}$$

$$A = \frac{|R(1 - \omega^2 LC)|}{\sqrt{\omega^2 L^2 + R^2 (1 - \omega^2 LC)^2}}$$

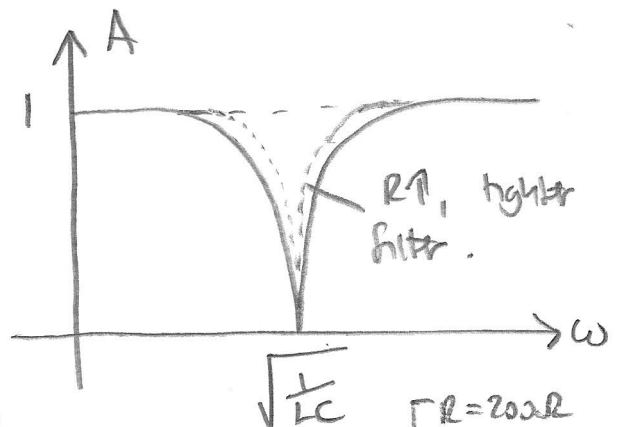

This could be used as a filter
eg remove 'mans hum' if $\frac{1}{2\pi} \sqrt{\frac{1}{LC}} = 50 \text{ Hz}$.

$$\begin{cases} R = 200 \Omega \\ C = 203 \mu\text{F} \\ L = 0.05 \text{ H} \\ \Rightarrow f_0 = 70 \text{ Hz} \end{cases}$$