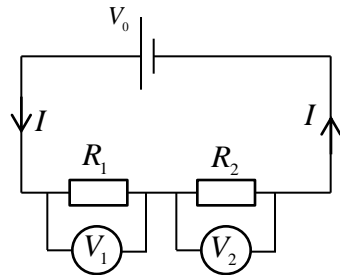


Maximum power theorem

Consider a series electrical circuit consisting of two resistors.

$$R_1 = xR$$

$$R_2 = R$$



What value of x results in the *maximum* power dissipated by resistor R_1 ?

$$P_1 = V_1 I$$

$$P_1 = I^2 xR$$

$$I = \frac{V_0}{xR + R}$$


$$\therefore P_1 = \frac{V_0^2}{R^2 (x+1)^2} xR$$

$$\therefore P_1 = \frac{V_0^2}{R} \frac{x}{(x+1)^2}$$

Note since the resistances must be positive $x > 0$

Define: $P_1 = \frac{V_0^2}{R} y$

$$y = \frac{x}{(x+1)^2}$$

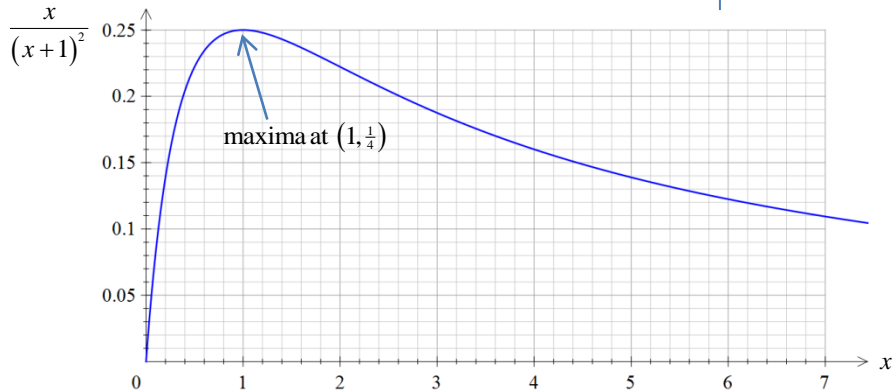

$$y = \frac{x}{(x+1)^2}$$

$$\frac{dy}{dx} = \frac{(x+1)^2(1) - x(2)(x+1)}{(x+1)^4}$$

$$\frac{dy}{dx} = \frac{(x+1)(x+1-2x)}{(x+1)^4}$$

$$\frac{dy}{dx} = \frac{1-x}{(x+1)^3}$$

$$\frac{dy}{dx} = 0 \Rightarrow \frac{1-x}{(x+1)^3} = 0$$

$$\therefore x = 1$$

$$y(1) = \frac{1}{(1+1)^2} = \frac{1}{4}$$

$$\therefore \text{maxima at } \left(1, \frac{1}{4}\right)$$

Therefore **maximum power** dissipated in resistor R_1 is

$$P_1 = \frac{V_0^2}{4R}$$

i.e. when **both resistors have the same value**

$$R_1 = R_2 = R$$

The total power dissipated by *both* resistors is


$$P = P_1 + P_2$$

$$P = I^2 (R_1 + R_2)$$

$$I = \frac{V_0}{xR + R}, \quad R_1 = xR, \quad R_2 = R$$

$$\therefore P_1 = \frac{V_0^2}{R^2 (x+1)^2} R(x+1)$$

$$P = \frac{V_0^2}{R} \frac{1}{x+1}$$

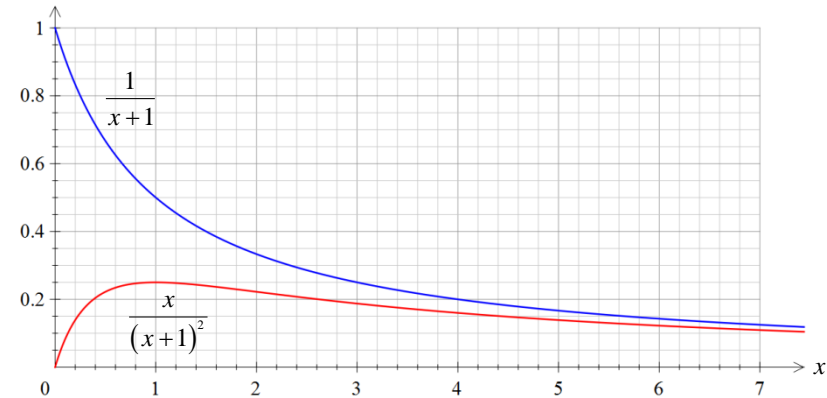

The graphs above describe the situation. The total power dissipated decays *hyperbolically* with x . The power in R_1 increases until $x = 1$. At this point both resistors dissipate the same power.

When $x > 1$, the fraction of total power dissipated in R_1 increases, but the total power dissipated by R_1 decreases, since the total power dissipated is also decreasing.