
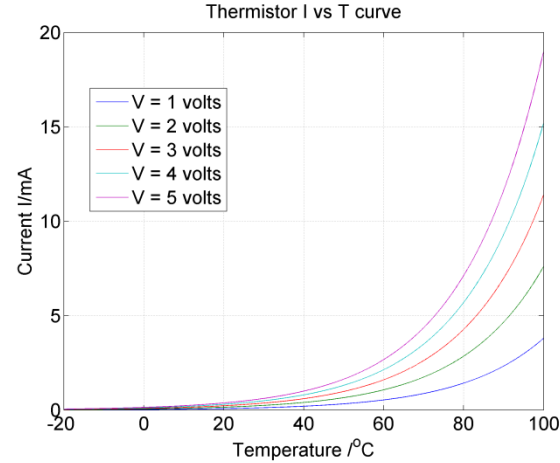
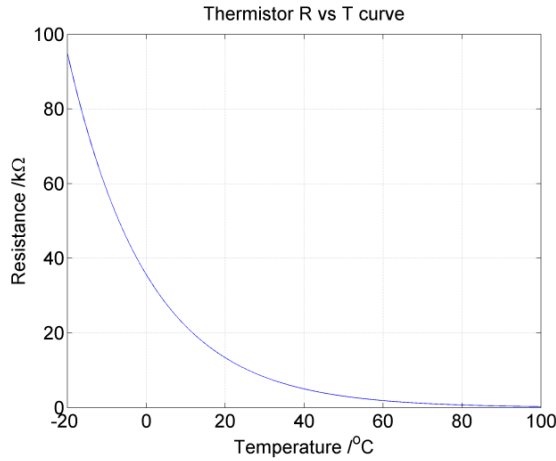




A simple electrical circuit can be used as a **sensor** if the resistance of one of the components in the circuit varies *significantly* with a change in the parameter being measured. For example, the resistance of a *thermistor* will change with temperature, and the consequential change in current drawn through a circuit can be used to measure the temperature, assuming a *calibration process* has occurred to relate the current measured to temperature.

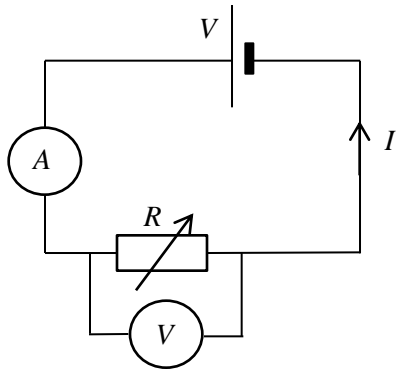

So apply a fixed voltage to the circuit, measure current using a sensitive ammeter and then use the graph to determine the temperature measurement.

Note a typical thermistor is has a *highly non-linear* resistance vs temperature relationship.

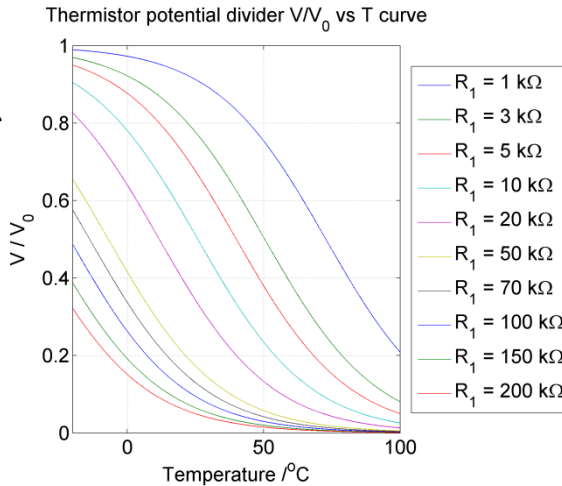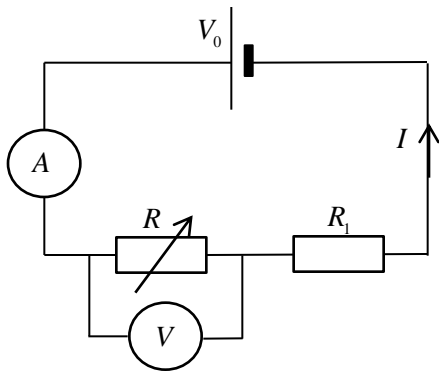
An alternative electrical measurement scheme is to use *voltage* rather than current. This may be preferable if the resistance of the sensor is very low, which means there may be a risk of drawing dangerously large currents through the sensor circuit. To vary voltage as resistance of the sensor changes, we use a **potential divider**.



The sensor can be said to **sensitive** if the electrical measurement (voltage in this case) variation is *large* given a variation in the parameter being measured. i.e. in our case the (T, V) graph varies significantly (i.e. a large % change) over the temperature range -20°C to 100°C .

But what happens if $R = R_0 + \delta R$ where the resistance change $\delta R \ll R_0$?
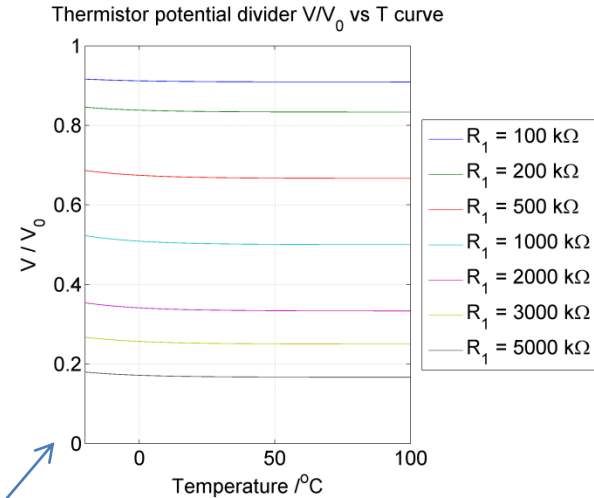
$$\frac{V}{V_0} = \frac{R_0 + \delta R}{R_0 + \delta R + R_1}$$



In the above example $R_0 = 1000\text{k}\Omega$ i.e. much higher than the variation of the thermistor resistance with temperature (about $100\text{k}\Omega$). Clearly the sensor is *not* vary sensitive in this case as the voltage barely changes over the temperature range.

To correct for this problem we need to make a *differential measurement*. In other words, a voltage response which is **zero** when $R = R_0$, $\delta R = 0$

$$V_0 = I(R + R_1) \quad \text{Ohm's Law}$$

$$V = IR$$

$$\therefore \frac{V}{V_0} = \frac{R}{R + R_1}$$

A **Wheatstone Bridge** circuit can be used to measure *small changes* in the resistance of a variable resistor R_2 . This is an effective way of constructing a **sensor system with high sensitivity**. The sensor (e.g. light-dependant-resistor, thermistor etc) operates by changing its resistance R_2 via a known curve in response to an environmental variable such as light intensity or temperature. Small changes in R_2 can be transformed into measurable voltages, with zero being the default setting. If the 'default' value of the variable resistor (R) is much larger than typical deviations δR , the Wheatstone Bridge gives rise to a voltage proportional to the fractional change $\delta R/R$, rather than the sum $R_2 = R + \delta R$. *This is the justification for the increase in sensitivity.*

Applying *Ohm's law* to the bridge circuit:

$$I_A = \frac{V_0}{R_1 + R_0 + \delta R}$$

$$I_C = \frac{V_0}{R_3 + R_4}$$

$$V_A = I_A (R_0 + \delta R)$$

$$V_C = I_C R_4$$

$$V_A = V_0 \left(\frac{R_0 + \delta R}{R_1 + R_0 + \delta R} \right)$$

$$V_C = V_0 \left(\frac{R_4}{R_3 + R_4} \right)$$

$$V_B = V_A - V_C$$

$$V_B = V_0 \left(\frac{R_0 + \delta R}{R_1 + R_0 + \delta R} - \frac{R_4}{R_3 + R_4} \right)$$

$$V_B = 0, \quad \delta R = 0$$

To enable a 'zero-offset' when $\delta R = 0$ we must *balance* the bridge.

$$\frac{R_0}{R_1 + R_0} = \frac{R_4}{R_3 + R_4}$$

$$R_0 (R_3 + R_4) = R_4 (R_1 + R_0)$$

$$R_0 R_3 + R R_4 = R_4 R_1 + R_0 R_4$$

$$R_0 = \frac{R_4 R_1}{R_3}$$

← This is called the *Bridge Equation*

Now define *sensitivity* by the gradient of the $V_B, \delta R$ curve.

$$\frac{\partial V_B}{\partial \delta R} = V_0 \left(\frac{(R_1 + R_0 + \delta R) - (R_0 + \delta R)}{(R_1 + R_0 + \delta R)^2} \right) = \frac{V_0 R_1}{(R_1 + R_0 + \delta R)^2}$$

Let us choose R_1 such that sensitivity is maximized:

$$\frac{\partial}{\partial R_1} \left(\frac{\partial V_B}{\partial \delta R} \right) = V_0 \frac{(R_1 + R_0 + \delta R)^2 - 2R_1 (R_1 + R_0 + \delta R)}{(R_1 + R_0 + \delta R)^4}$$

$$R_1 + R_0 + \delta R > 0$$

$$\therefore \frac{\partial}{\partial R_1} \left(\frac{\partial V_B}{\partial \delta R} \right) = 0 \Rightarrow R_1 + R_0 + \delta R = 2R_1$$

$$\therefore R_1 = R_0 + \delta R$$

Since $\delta R \ll R_0$ and δR is a variable quantity, a practical optimum R_1 is $R_1 = R_0$



To set $V_B = 0, \delta R = 0$

$$R_0 = \frac{R_4 R_1}{R_3}$$

$$R_1 = R_0 \quad \therefore R_4 = R_3$$


$$V_B = V_0 \left(\frac{R_0 + \delta R}{2R_0 + \delta R} - \frac{R_4}{R_4 + R_4} \right)$$
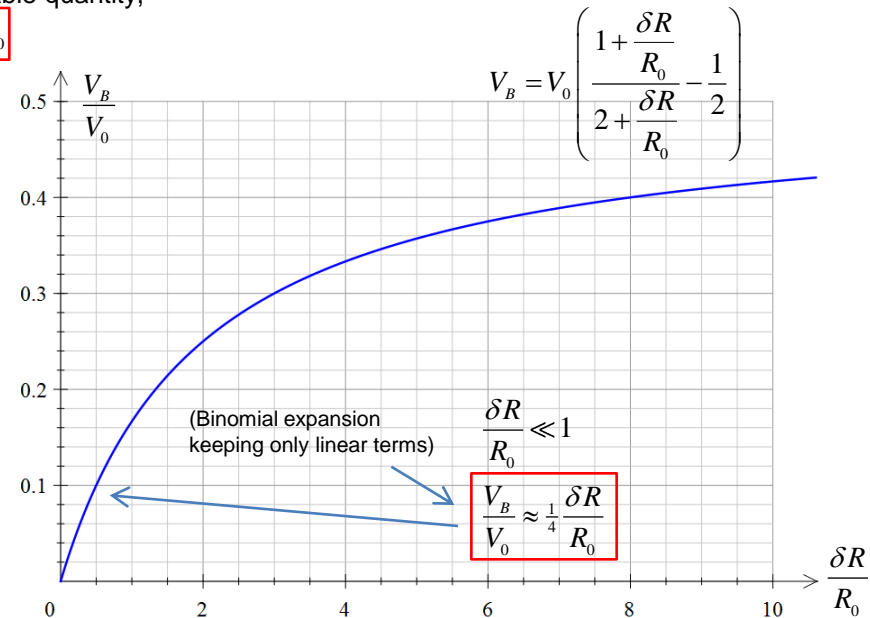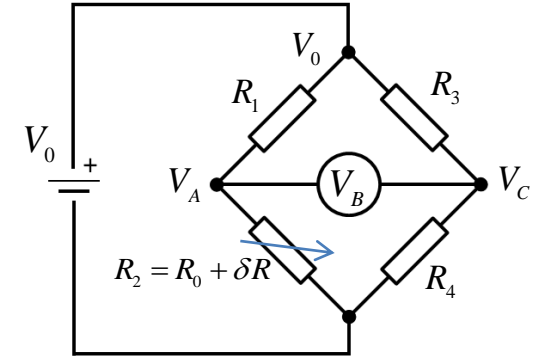
$$V_B = V_0 \left(\frac{1 + \frac{\delta R}{R_0}}{2 + \frac{\delta R}{R_0}} - \frac{1}{2} \right)$$





The **Wheatstone Bridge** can significantly improve the sensitivity of our thermistor *in series with a large fixed resistor* (which could be the internal resistance of the sensor system). This is because the voltage now changes a small amount from zero, rather than a small deviation from a fixed quantity.

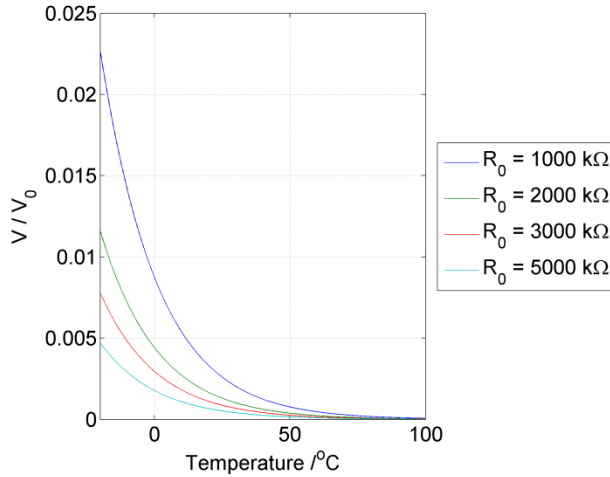Thermistor wheatstone bridge V/V_0 vs T curve



Thermistor R vs T curve

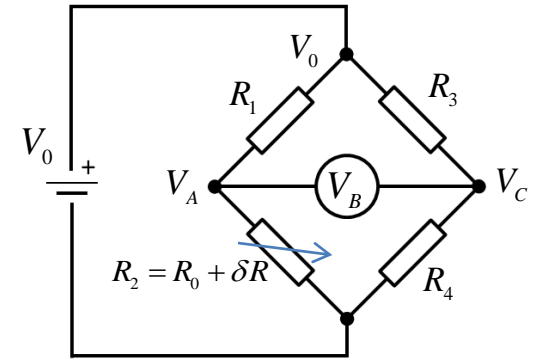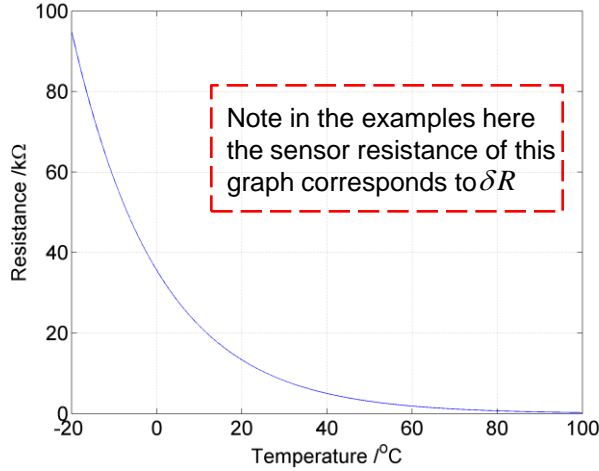


The Wheatstone Bridge circuit

$$V_B = V_0 \left(\frac{R_0 + \delta R}{R_1 + R_0 + \delta R} - \frac{R_4}{R_3 + R_4} \right)$$


$$R_1 = R_3 = R_4 = R_0$$

$$\therefore V_B = V_0 \left(\frac{1 + \frac{\delta R}{R_0}}{2 + \frac{\delta R}{R_0}} - \frac{1}{2} \right)$$

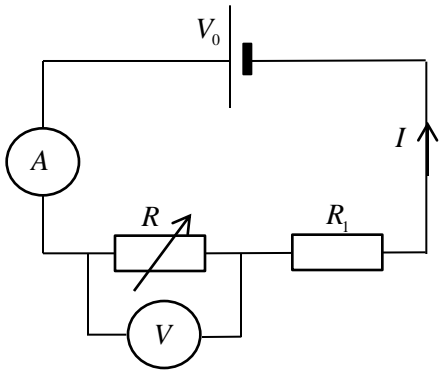The downside is the actual voltage ratio may be too small result in a measurable Wheatstone Bridge voltage. The solution here is to *increase* the applied voltage to the system.



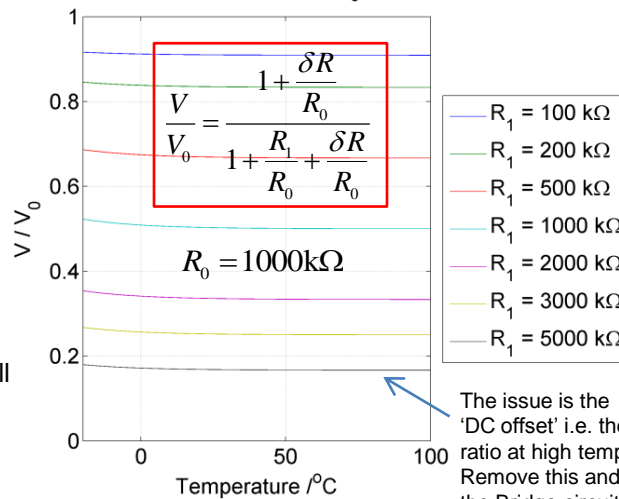Thermistor potential divider V/V_0 vs T curve



The issue is the 'DC offset' i.e. the voltage ratio at high temperatures. Remove this and we have the Bridge circuit result.

If the sensor resistor variation is small compared to the mean, the potential divider circuit is not very sensitive.

$$R = R_0 + \delta R \quad \delta R \ll R_0$$

