

[Youtube video1](#)

[Youtube video2](#)




Equipment

Terminal block with five resistors

Three multimeters


Laptop

Lots of wires!

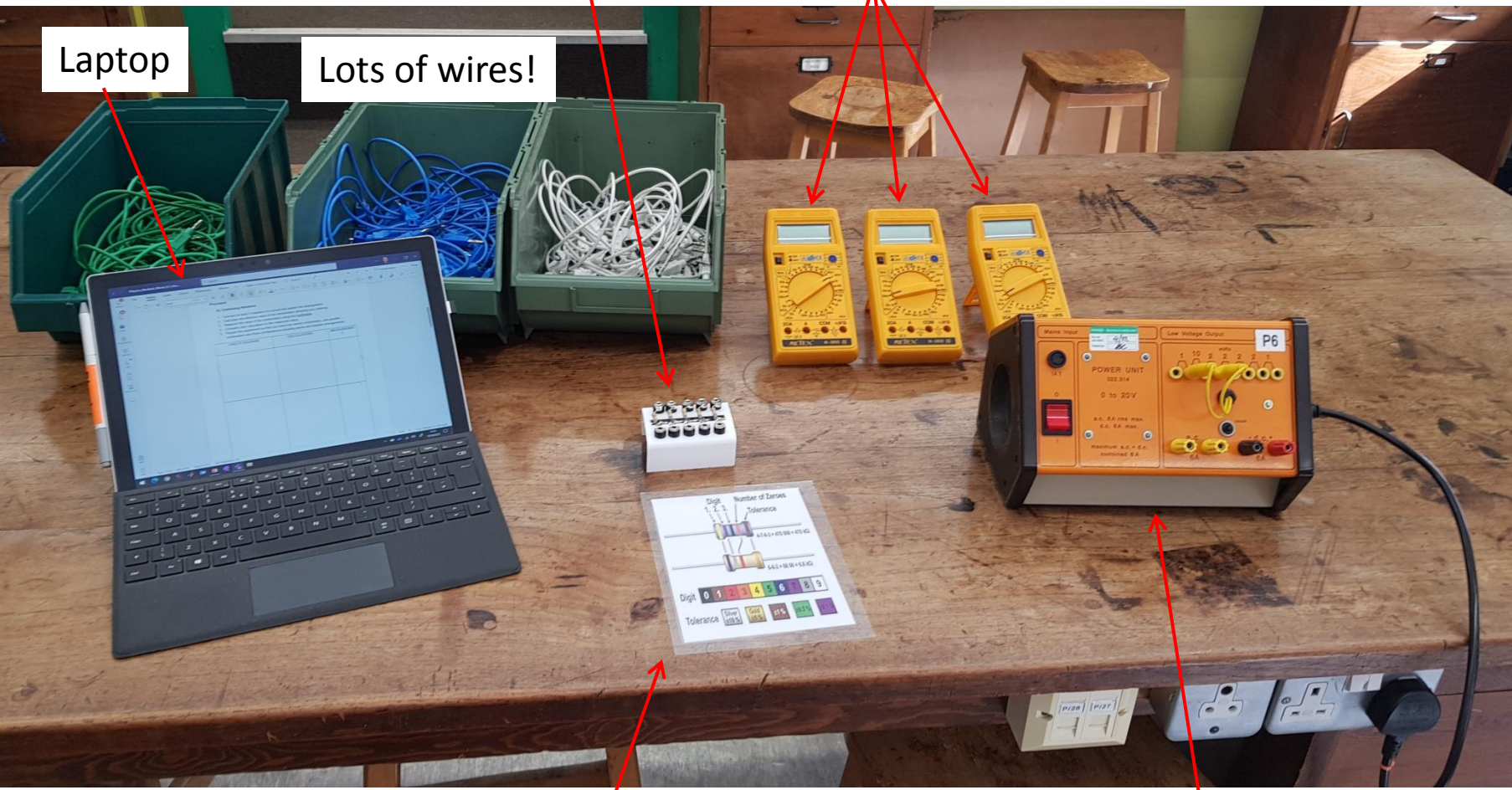

Resistor code chart

Power supply

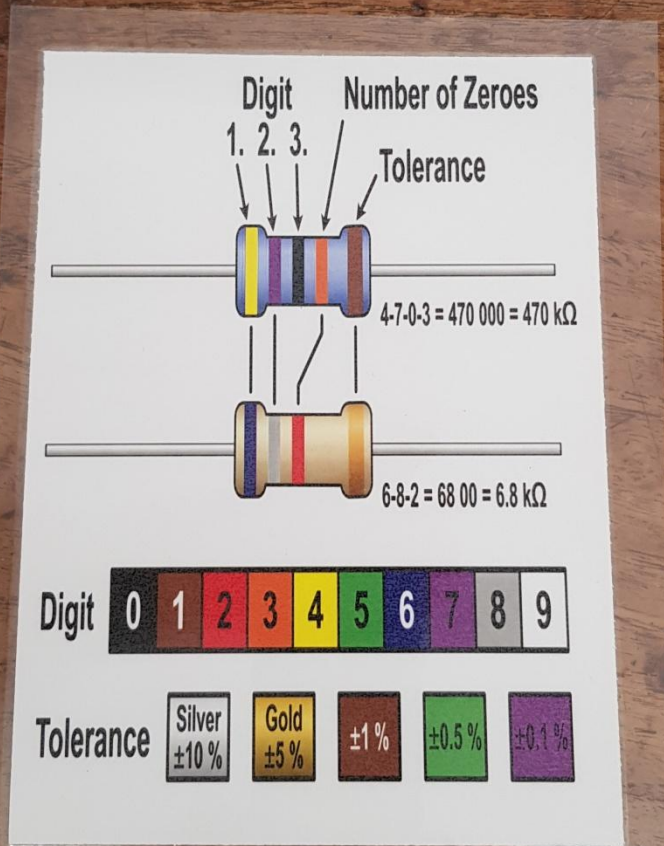

Five different resistors



TASK 1: Create a table and work out from the coloured bands the resistances.

e.g. **A:** orange, orange, brown, gold

So: 330 ohms, +/- 5%

Resistor	Digits	Zeros	Tolerance /%	Colours	Resistance /ohms	Resistance /k ohms	Measured resistance /k ohms	% error
A	33	1	5	Orange Orange Brown Gold	330	0.33	0.334	1.21%
B	15	2	5	Brown Green Red Gold	1500	1.5	1.506	0.40%
C	47	2	5	Yellow Purple Red Gold	4700	4.7	4.63	-1.49%
D	10	3	5	Brown Black Orange Gold	10000	10	9.84	-1.60%
E	56	3	5	Green Blue Orange Gold	56000	56	55.7	-0.54%

TASK 2: Use a multimeter to measure the resistances individually. Compare to nominal values based upon coloured bands.

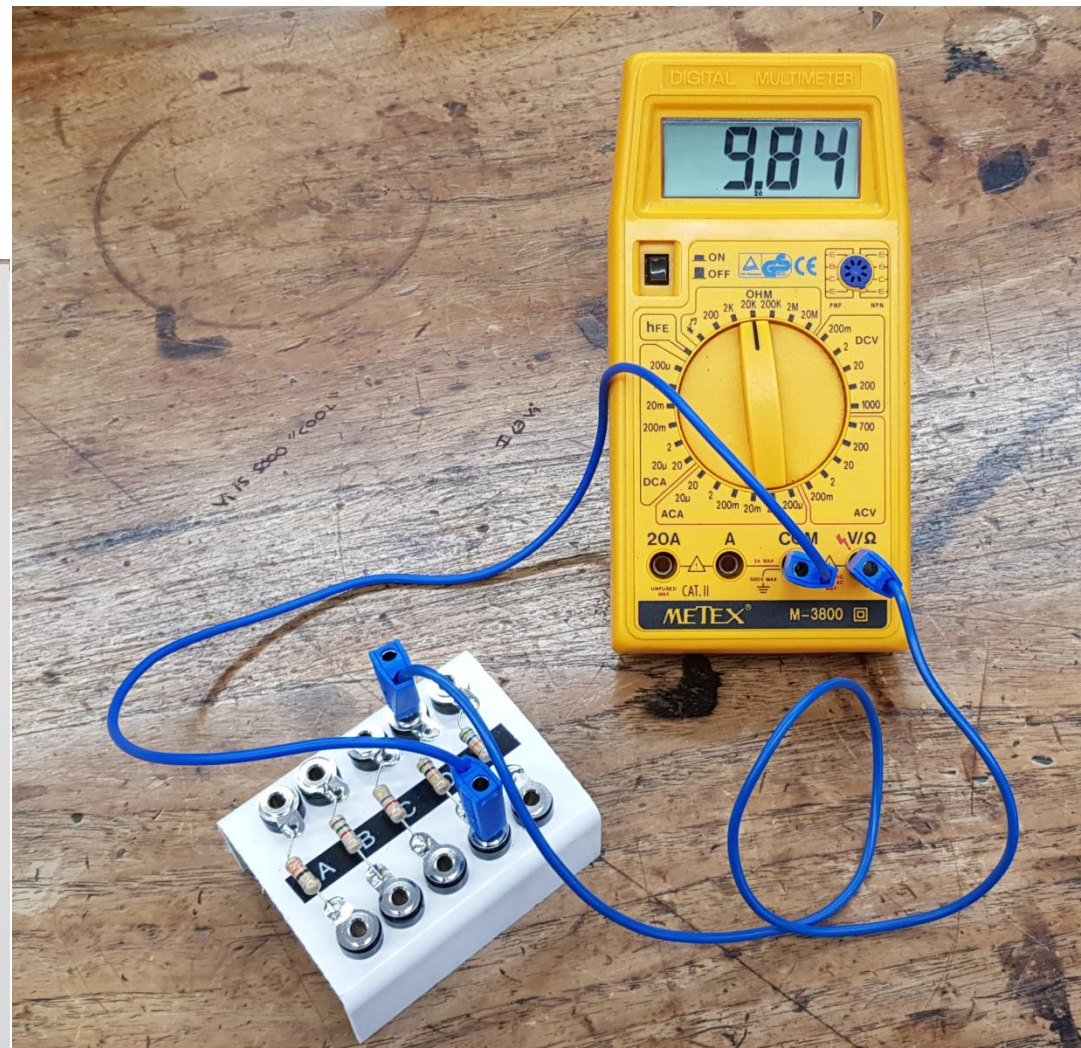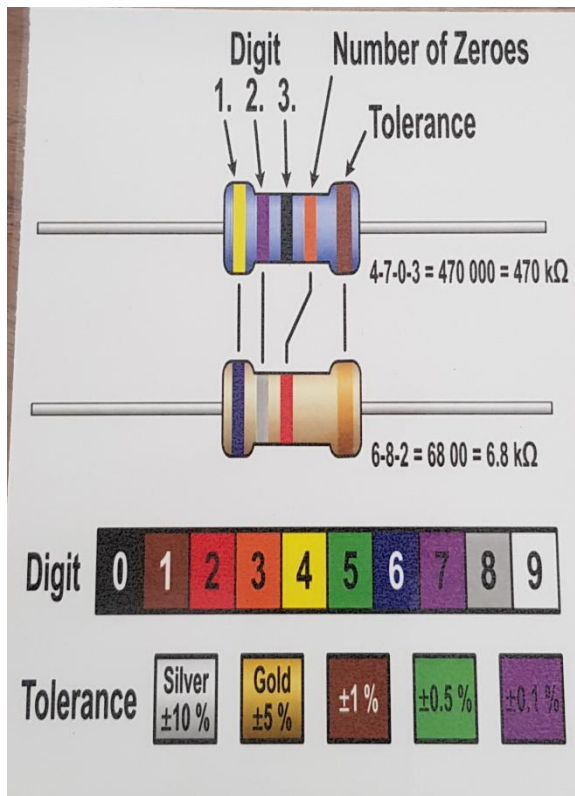


TASK3: Wire up FIVE different arrangements of three resistors. One in series, one in parallel and three in a mixture.


Predict the resistance by calculation (use either nominal resistances, or better, measured resistances) and **compare with direct measurement** using the multimeter.

For each circuit, draw a diagram first.


①

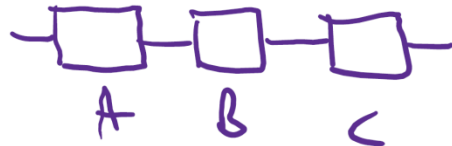


③

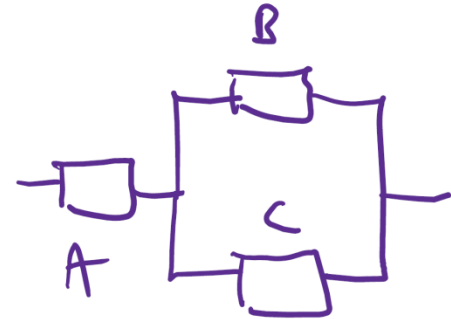


②

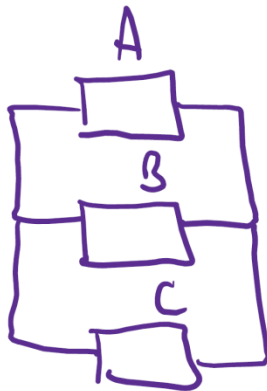


④

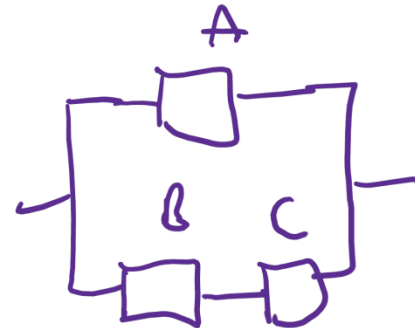

⑤

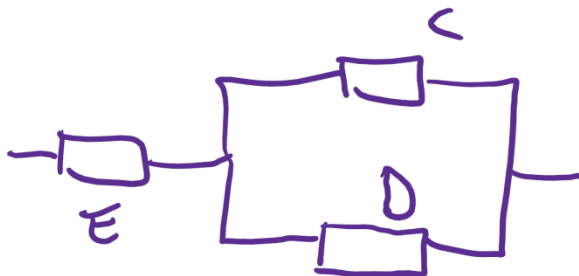


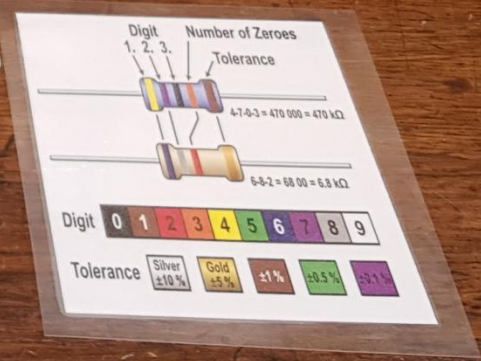
Five examples – other combinations are possible!



Resistor	Digits	Zeros	Tolerance /%	Colours	Resistance /ohms	Resistance /k ohms	Measured resistance /k ohms	% error
A	33	1	5	Orange Orange Brown Gold	330	0.33	0.334	1.21%
B	15	2	5	Brown Green Red Gold	1500	1.5	1.506	0.40%
C	47	2	5	Yellow Purple Red Gold	4700	4.7	4.63	-1.49%
D	10	3	5	Brown Black Orange Gold	10000	10	9.84	-1.60%
E	56	3	5	Green Blue Orange Gold	56000	56	55.7	-0.54%

Combination	Calculated resistance /kohms	Measured resistance /ohms	% error
1 A + B + C	6.53	6.41	-1.84%
2 $1/(1/A + 1/B + 1/C)$	0.26	0.274	7.13%
3 A + $1/(1/B + 1/C)$	1.47	1.492	1.70%
4 $1/(1/A + 1/(B+C))$	0.31	0.337	7.56%
5 E + $1/(1/C + 1/D)$	59.20	58.4	-1.35%

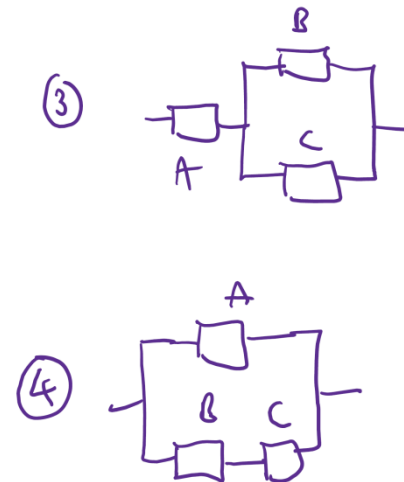
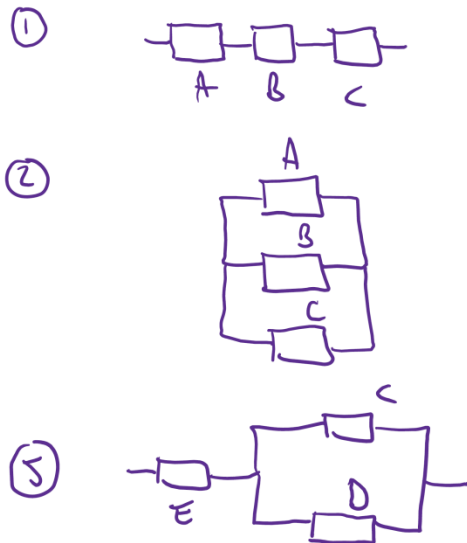
- Series resistances add
- *Parallel* resistances add in *reciprocals*



	Combination	Calculate d resistance /kohms	Measured resistance /ohms	% error
1	A + B + C	6.53	6.41	-1.84%
2	$1/(1/A + 1/B + 1/C)$	0.26	0.274	7.13%
3	$A + 1/(1/B + 1/C)$	1.47	1.492	1.70%
4	$1/(1/A + 1/(B+C))$	0.31	0.337	7.56%
5	$E + 1/(1/C + 1/D)$	59.20	58.4	-1.35%

Combination 1. A,B,C wired in series



①

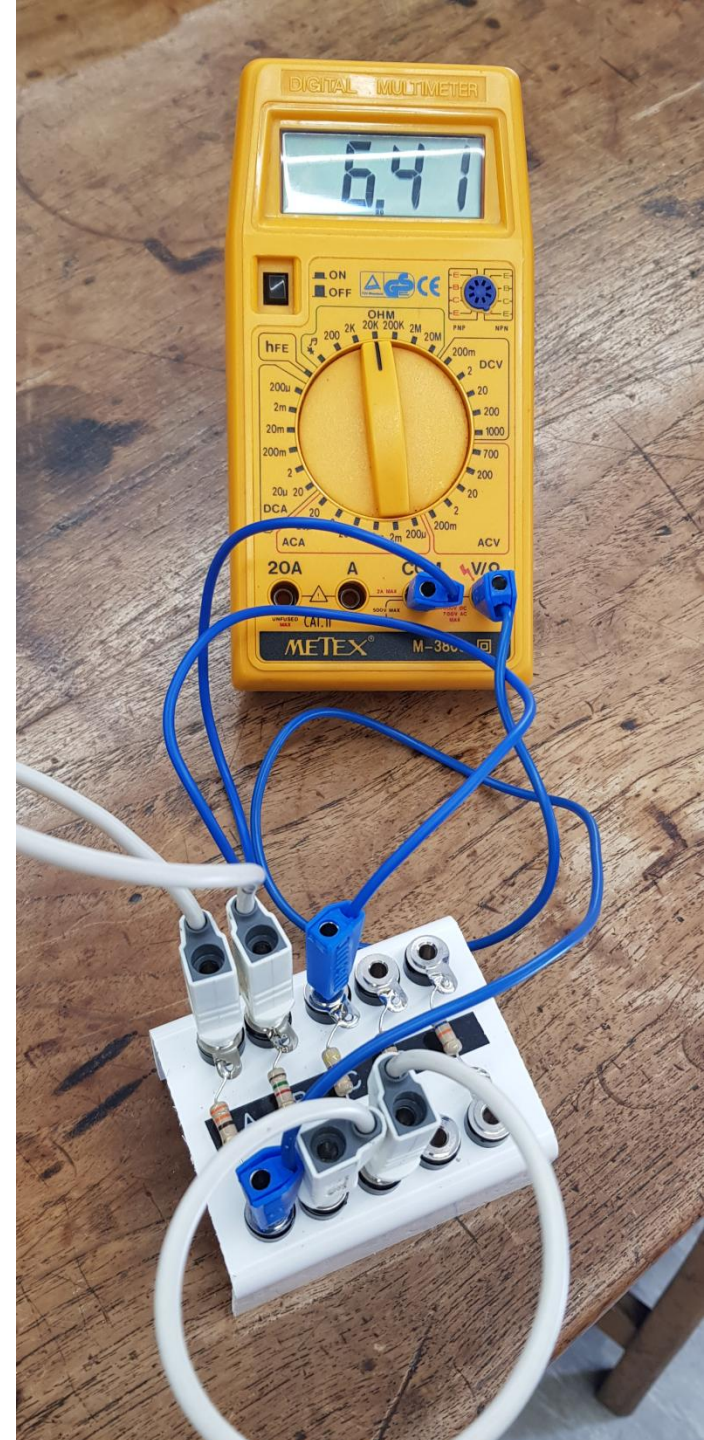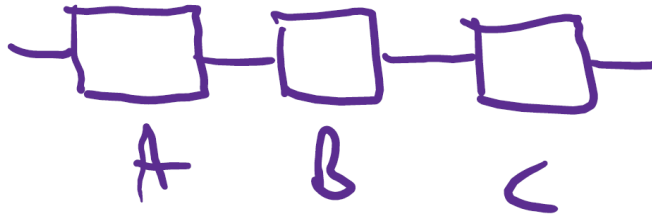

	Combination	Calculate d resistance /kohms	Measured resistance /ohms	% error
1	A + B + C	6.53	6.41	-1.84%
2	$1/(1/A + 1/B + 1/C)$	0.26	0.274	7.13%
3	$A + 1/(1/B + 1/C)$	1.47	1.492	1.70%
4	$1/(1/A + 1/(B+C))$	0.31	0.337	7.56%
5	$E + 1/(1/C + 1/D)$	59.20	58.4	-1.35%

Combination 2. A,B,C wired in parallel



②

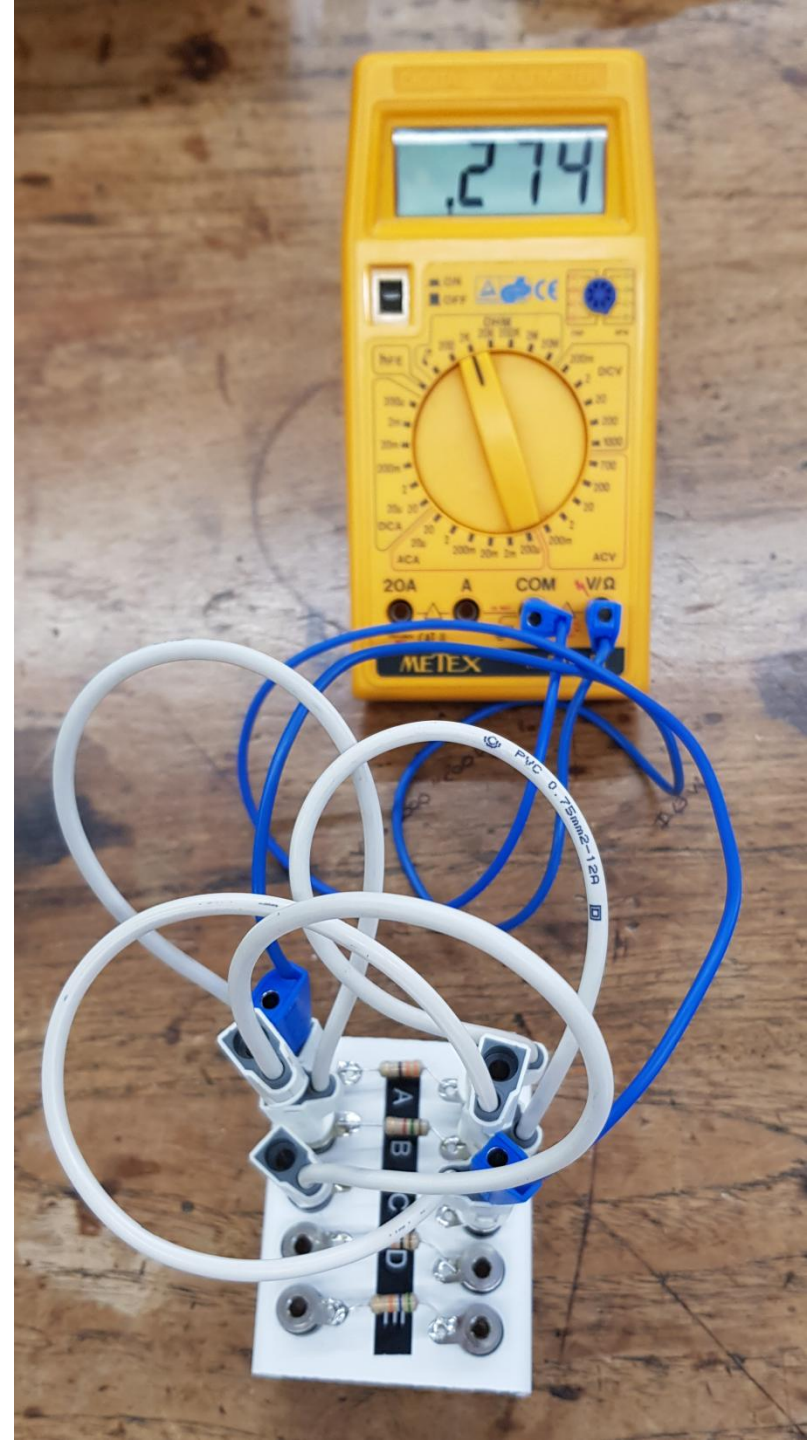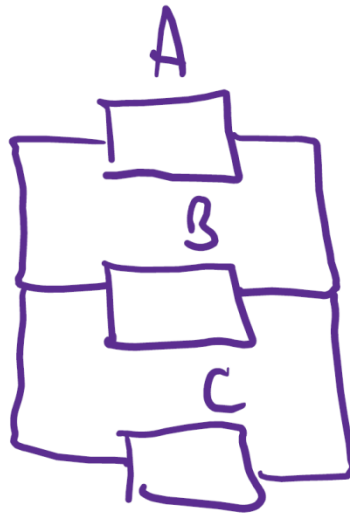

	Combination	Calculated resistance /kohms	Measured resistance /ohms	% error
1	A + B + C	6.53	6.41	-1.84%
2	$1/(1/A + 1/B + 1/C)$	0.26	0.274	7.13%
3	$A + 1/(1/B + 1/C)$	1.47	1.492	1.70%
4	$1/(1/A + 1/(B+C))$	0.31	0.337	7.56%
5	$E + 1/(1/C + 1/D)$	59.20	58.4	-1.35%

Combination 4.

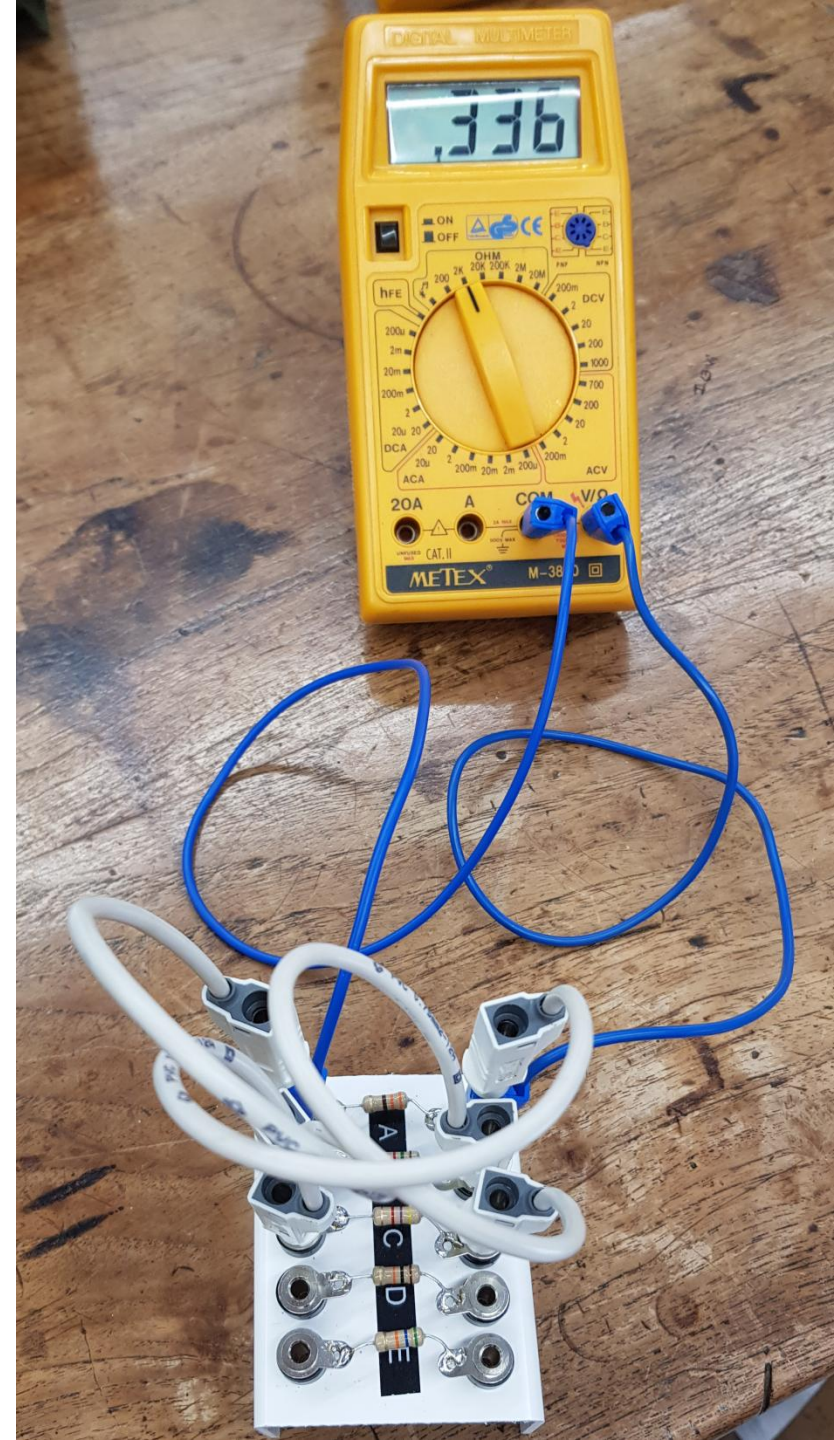
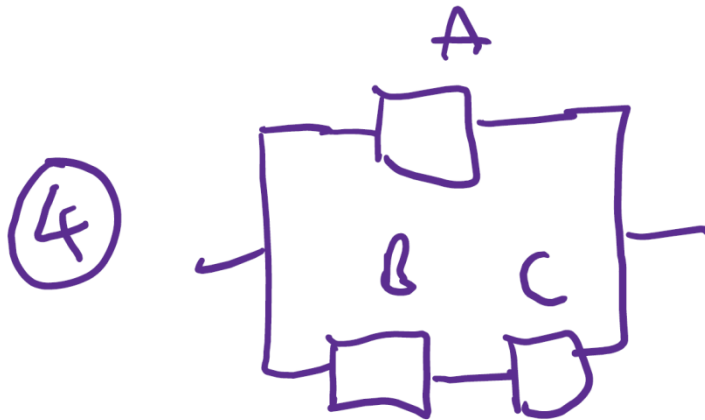
A in parallel with B and C wired in series



	Combination	Calculate d resistance /kohms	Measured resistance /ohms	% error
1	A + B + C	6.53	6.41	-1.84%
2	$1/(1/A + 1/B + 1/C)$	0.26	0.274	7.13%
3	$A + 1/(1/B + 1/C)$	1.47	1.492	1.70%
4	$1/(1/A + 1/(B+C))$	0.31	0.337	7.56%
5	$E + 1/(1/C + 1/D)$	59.20	58.4	-1.35%


Combination 5.

E in series with C and D wired in parallel

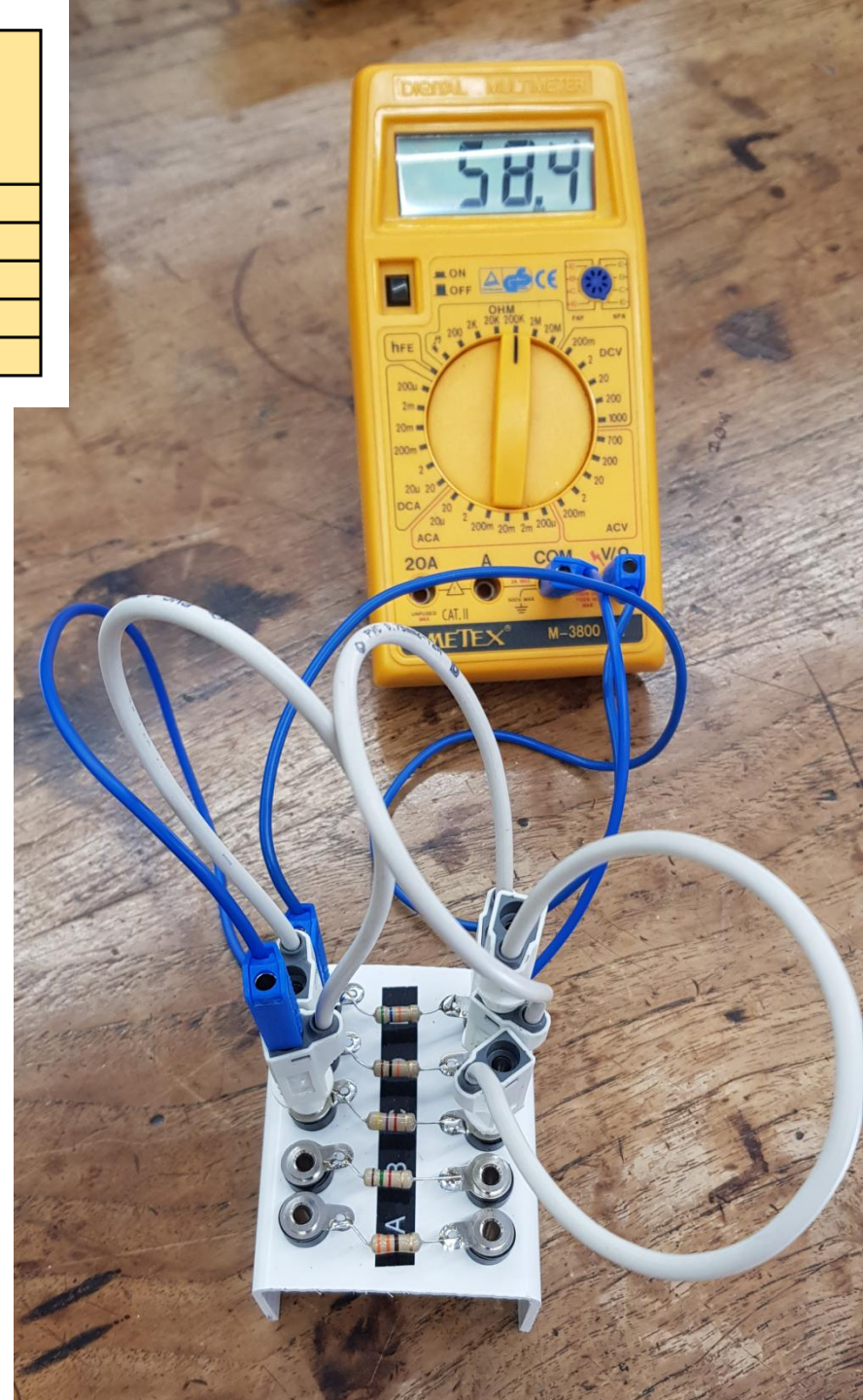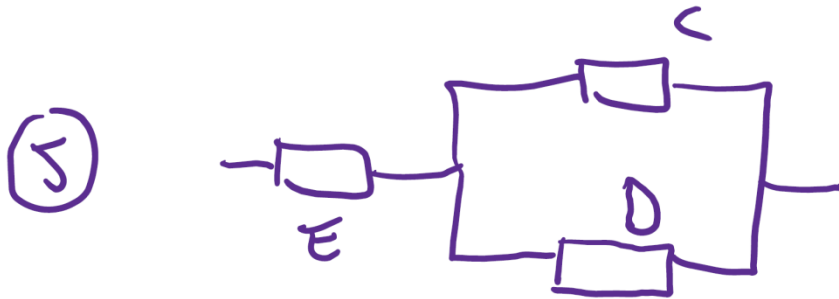

TASK4: Wire three resistors in series and connect to a 5V DC power supply.

Connect voltmeters across each resistor.

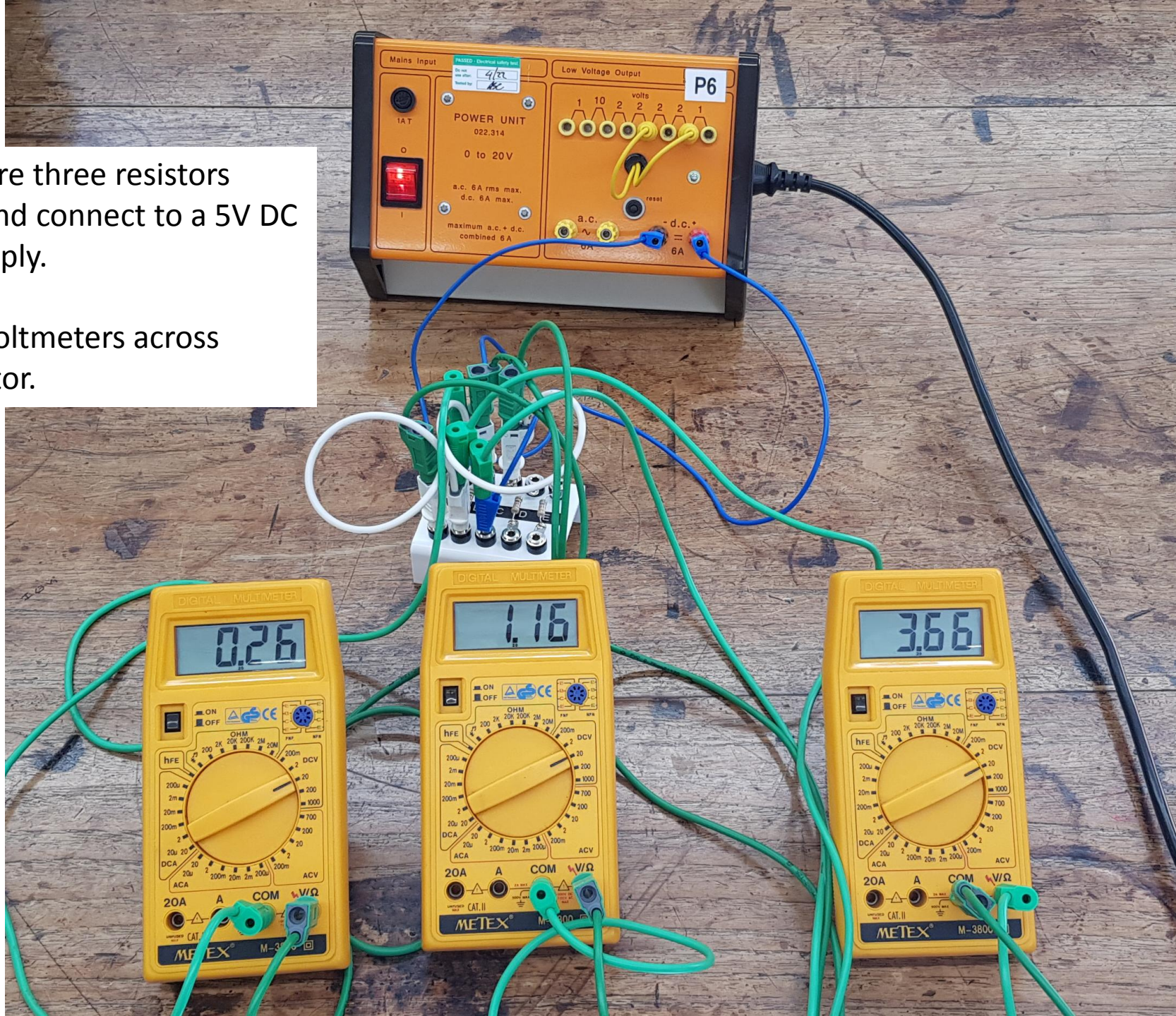

POTENTIAL DIVIDER CIRCUIT (three resistors in series)


These columns should match

Resistor	Resistance /k ohms	Fraction of total resistance	PD /volts	Fraction of total PD
A	0.334	0.052	0.26	0.051
B	1.506	0.233	1.17	0.229
C	4.63	0.716	3.68	0.720
6.47			5.11	

C	4.63	0.066	0.34	0.067
D	9.84	0.140	0.73	0.143
E	55.7	0.794	4.1	0.802
70.17			5.17	

Confirm the **potential divider** idea (since the same current flows through each resistor when wired in the same series loop).
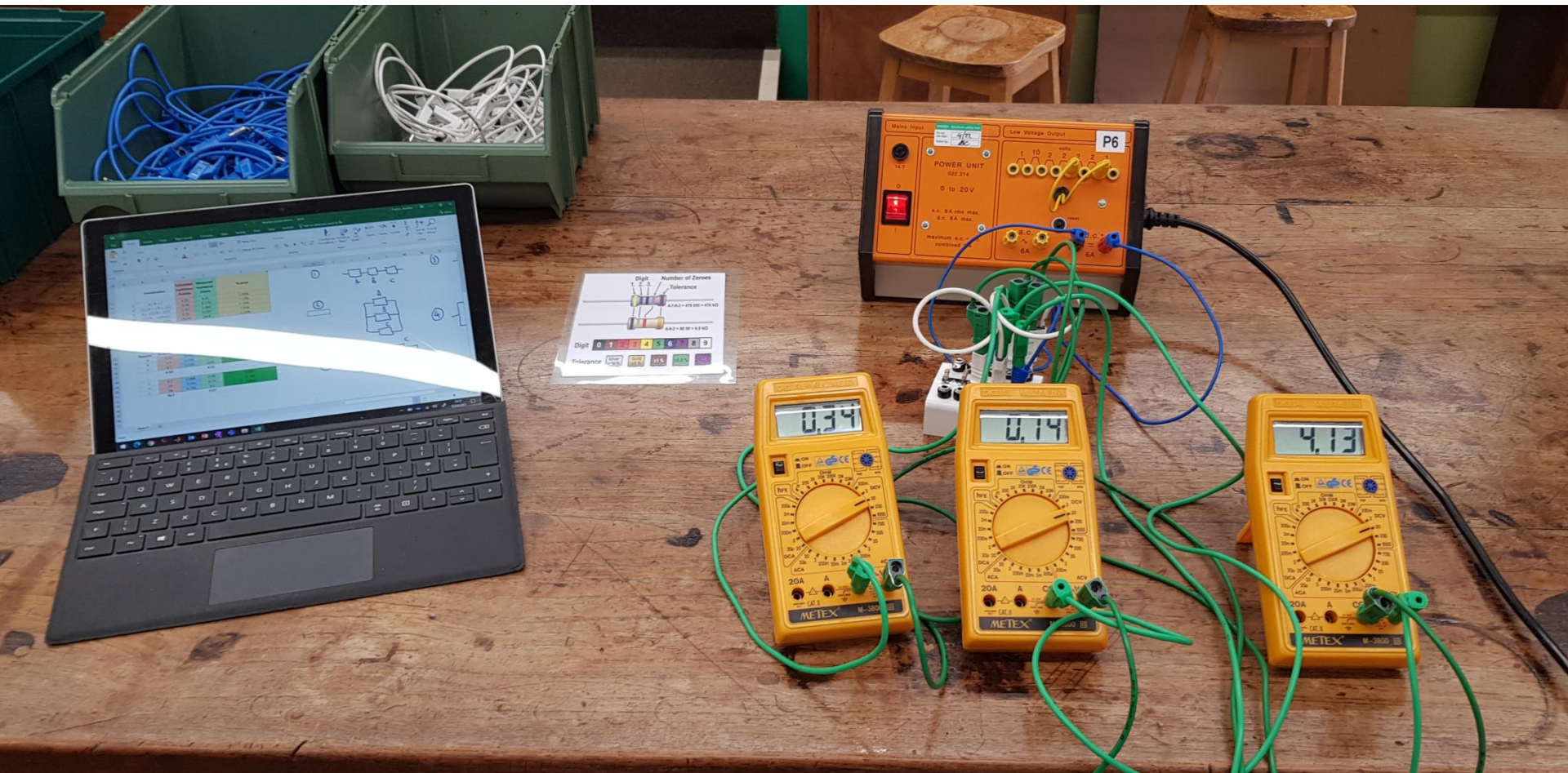
$$\frac{V_{A,B,C}}{V_A + V_B + V_C} = \frac{R_{A,B,C}}{R_A + R_B + R_C}$$



Digit	1	2	3
Number of Zeros	0	1	2
Tolerance	±1%	±2%	±5%

Digit	0	1	2	3	4	5	6	7	8	9
Tolerance	±1%	±1%	±2%	±3%	±4%	±5%	±10%	±15%	±20%	±25%

POWER UNIT
032.314
0 to 20V
K.O. 8A rms max.
6A 6A rms
MAXIMUM R.C.
CONSTANT

Low Voltage Output
1 10 2 0 2
6A 6A

P6

0.34
METEX M-3800

0.19
METEX M-3800

4.13
METEX M-3800