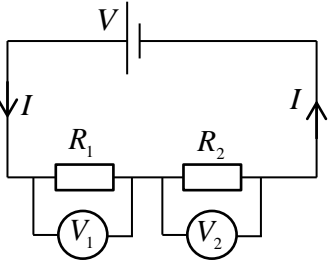


Series & Parallel circuits

Electronic systems consist of networks of basic components which modify the rate of flow of charge (*current*) and energy per unit charge (*voltage*) between two points in the network. In order to model the behaviour of a system, it is useful to understand the basic mathematical features. We shall consider *resistive* components and the difference between *series* and *parallel* arrangements of resistors. *Ohmic* components are those which have a *constant resistance*.

Series circuits



The *same* current must flow through every component in the loop, otherwise charge would be created or lost.

$$V_1 = IR_1 \quad \text{Apply 'V=IR' to each resistor in turn}$$

$$V_2 = IR_2$$

$$V = IR \quad \text{Apply 'V=IR' to entire series loop. R is the total resistance}$$

$$V = V_1 + V_2 \quad \text{The applied voltage V must be divided across the resistors}$$

Hence:

$$IR = IR_1 + IR_2$$

$$\therefore R = R_1 + R_2 \quad \text{so series resistors add}$$

We can use this result to show that resistances in series can act as *potential dividers*

$$I = \frac{V_1}{R_1} = \frac{V}{R_1 + R_2} \quad \therefore \frac{V_1}{R_1} = \frac{V}{R_1 + R_2}$$

$$V_1 = \frac{R_1}{R_1 + R_2} V \quad \text{i.e. the voltage across a resistor is the same fraction of the applied voltage as the ratio of resistance to the total resistance.}$$

Definition of resistance

$$V = IR$$

Voltage / volts
Energy per unit charge lost across a conductor of resistance R

Resistance /ohms (Ω)


Current / amps
Rate of flow of charge through resistor R

Note due to a quirk of history, **conventional current is the 'flow of positive charge'**. Unfortunately **electrons** were discovered after many of the electrical conventions were fixed. Since it is the *electrons which are mobile in a conductor*, current can be thought of as the flow of 'holes' of net positive charge left when an electron has been moved via an electric field.



Georg Ohm
1789-1854

Parallel circuits

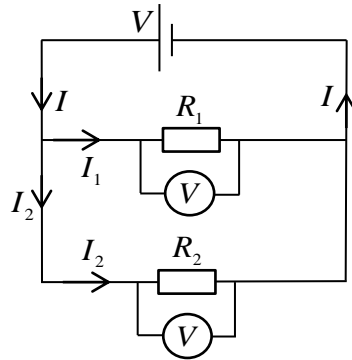

$$V = IR \quad \text{Apply 'V=IR' to entire circuit. R is the total resistance}$$

$$V = I_1 R_1 \quad \text{Apply 'V=IR' to each resistor in turn. Same electric field across each loop, so the same voltage is dropped across the resistors}$$

$$V = I_2 R_2$$

Current is assumed to be contained within the circuit, hence:


$$I = I_1 + I_2 \quad \leftarrow \text{This is Kirchhoff's law}$$

Therefore:

$$V/R = V/R_1 + V/R_2$$

$$\therefore \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} \quad \text{so parallel resistor loop resistance reciprocals add}$$

Series circuit example

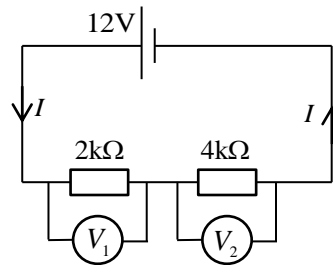


$$I = \frac{12}{2+4} \text{ mA}$$

$$I = 2 \text{ mA}$$

$$V_1 = \frac{2}{2+4} \times 12 = 4 \text{ V}$$

$$V_2 = \frac{4}{2+4} \times 12 = 8 \text{ V}$$

Parallel circuit example

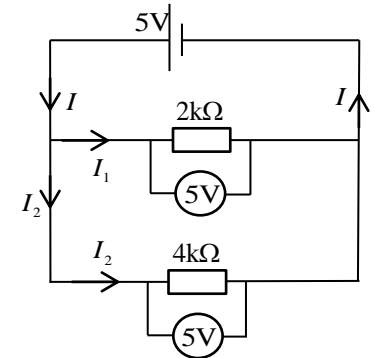

$$I_1 = 5/2 = 2.5 \text{ mA}$$

$$I_2 = 5/4 = 1.25 \text{ mA}$$

$$I = I_1 + I_2 = 3.75 \text{ mA}$$


$I = \text{voltage} / \text{resistance}$
then add currents

Or alternatively ...

$$R = \frac{1}{\frac{1}{2} + \frac{1}{4}} = \frac{4}{3} \text{ k}\Omega$$

$$I = 5 / \frac{4}{3} = \frac{15}{4} \text{ mA} = 3.75 \text{ mA}$$

Use reciprocal resistance addition rule

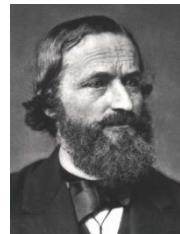

Gustav Kirchhoff
1824-1887